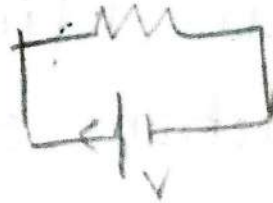


UNIT-1 Electric Circuit

Voltage: Potential difference b/w 2 points. (or) work done for moving a ^{unit} charge from one point to other point.

$$V = \frac{W}{q}$$



It is defined as the potential difference b/w any two points known as voltage.

voltage is denoted by 'V' and the unit of voltage is volts.

(or)

voltage is defined as work done in moving unit charge from one point to other point.

$$V = \frac{W}{q} = \frac{\text{Joules}}{\text{Coulomb}} \Rightarrow \text{Volts.}$$

Units of voltage is Volts & voltage is denoted by V.

$$V = \frac{dW}{dq}$$

Current: Rate of flow of charge or
Rate of flow of electrons.

'i' or 'I' is the denotation.

Unit: Ampere

It is defined as rate of flow of electrons or charge known as current and current is represented by 'I' or 'i' and the unit of current is amperes.

$$I = \frac{q}{t} = \frac{\text{coulombs}}{\text{Sec}} = \text{Amp.}$$
$$= \frac{dq}{dt}$$

Energy (W): Capacity to do the work.

Energy is nothing but capacity to do work it is represented by 'W' & unit of energy is joules.

$$W = \int P \cdot dt$$

$$W = \int P \cdot dt$$

Power: Power is nothing but energy with respect to time (or) product of voltage and current. $P = \frac{W}{t} = N$

Power is denoted by 'P' $P = VI$
Units of power is watts. $= \frac{dW}{dt}$

$$\text{Power} = \frac{\text{Work done}}{\text{Time}} = \frac{\text{Energy}}{\text{Time}} = \frac{W}{t}$$

$$\text{Power} = \frac{\text{Energy}}{\text{time}} = \text{watts} \cdot P = \frac{dW}{dt}$$

$$P = V \times I$$

$$P = \frac{dW}{dq} \times \frac{dq}{dt}$$

$$P = \frac{dW}{dt}$$

$$W = P \times t$$

Ohm's law: It states that at constant temperature current is directly proportional to voltage and inversely

proportional to resistance known as
Ohm's law

current is directly $\propto V$

$$I \propto V$$

$$I \propto V$$

$$I \propto \frac{1}{R}$$

$$I \propto \frac{1}{R}$$

$$V = IR \text{ (AV)}$$

$$I = \frac{V}{R} \text{ A}$$

$$V = IR \text{ A}$$

$$R = \frac{V}{I} \Omega$$

$$I = \frac{V}{R} \text{ V}$$

$$R = \frac{V}{I} \Omega$$

Power formulas: $P = V \times I$

$$P = V \times I$$

$$= V \times I = IR \times I$$

Energy:

$$W = \int P \cdot dt = \int V \times I \cdot dt$$

$$W = \int I^2 R \cdot dt$$

$$W = I^2 R t$$

$$W = \int P \cdot dt$$

$$= \int I^2 R \cdot dt$$

$$= I^2 R t$$

$$V = I^2 R$$

$$= V \times \frac{V}{R}$$

$$P = \frac{V^2}{R}$$

watts

limitations: Nature of the material.

- 1) Ohm's law is not applicable to non linear circuits like SCR, diodes, transistors, Ohm's law also depends on the nature of the material.
- 2) Ohm's law is also not applicable to metals.

Temperature also effects Ohm's law.

Problems:

- 1) A 12Ω resistor is connected across 6 volts battery find how much current flows through the resistor.

$$V = I R.$$

$$6 = I \times 12$$

$$I = \frac{6}{12}$$

$$I = 0.5 \text{ Amp.}$$

- 2) If 0.6 A current flows through a resistor voltage of 2 points of a resistor is 12 volts. what's the resistance of resistor.

$$R = \frac{V}{I} = \frac{12}{0.6} = 20 \Omega$$

30) If charge of a material is 30 Coulombs
we take the time 5 sec. $I = ?$

$$I = \frac{\text{charge}}{t} = \frac{30}{5} = 6 \text{ Amp.}$$

Resistor: Resistor is nothing but

Resistor opposes the very flow
of current through it

It is denoted by R .

units = ohm (Ω)

$$R = \frac{\rho l}{A}$$

ρ = Specific resistance (or)

factors effecting resistors: resistivity.

1) Resistance depends upon length of
the material

$$R \propto l$$

2) Area of Cross section

Resistance depends upon area of

cross section $R \propto \frac{l}{a}$

$$R = \frac{\rho l}{a}$$

ρ = specific resistance or resistivity.

l = length

a = cross sectional area.

Conductance: It is the reciprocal of resistance. Denoted by G .

$$G = \frac{1}{R}$$
$$= \frac{1}{R}$$

$$= \Omega^{-1} \text{ (or) mho (V)}$$

Unit of conductance is ~~mho~~ mho

Resistivity: It is defined as resistance of unit area and unit length it is denoted by ' ρ ' & the units are 'ohm-m' ($\Omega\text{-m}$)

$$R = \frac{\rho l}{A}$$

$$\rho = \frac{Ra}{l} = \text{resistance per unit area by unit length}$$

$$\rho = \frac{\text{ohm-m}^2}{\text{m}} = \text{ohm-m}$$

conductivity!

It is defined as reciprocal of resistivity it is represented by ' σ '. Unit of conductivity is $\sigma = \frac{1}{\rho}$.

Determine the resistance of 564m length of aluminium conductor whose rectangular cross section is 4cm x 2cm assume resistivity is equal to 2.826×10^{-8} ohm-m

$$2.826 \times 10^{-8} = R \times 8 \times 10^{-4}$$

$$\frac{2.826 \times 10^{-8} \times 564}{8 \times 10^{-4}} = R$$

$$= 1.413 \times 141 \times 10^{-4}$$

$$R = 1.99233 \times 10^{-2} \Omega$$

Q) Calculate the length of copper wire 1.5mm in diameter to have a resistance of 0.3 ohm the resistivity of $\mu\Omega\cdot m$.

Copper is $0.017 \mu\Omega\cdot m$

$$\begin{array}{r} 1.413 \\ \times 141 \\ \hline 1413 \\ 5652 \\ \hline 199233 \end{array}$$

$$L = 1.5 \times 10^{-3}$$

$$a = \frac{\pi d^2}{4}$$

$$R = 0.3 \Omega$$

$$\rho = 0.017 \times 10^{-6}$$

$$a = \frac{\pi d^2}{4}$$

$$= \frac{3.14 \times 1.5 \times 1.5 \times 10^{-6}}{4}$$

2)

$$2) 3.14 \times 1.5^2$$

$$\begin{array}{r} 2 \downarrow \\ 11 \\ 10 \checkmark \\ \hline 14 \end{array}$$

$$= 1.5^2 \times 0.75 \times 1.5$$

$\times 10^{-6}$

$$= 1.76625 \times 10^{-6}$$

$$E = \frac{81}{2}$$

2)

$$\lambda = 10^{-6} \text{ m} \quad 0.3 = \frac{0.017 \times 10^{-6} \times 11700}{1.76625 \times 10^{-6}}$$

1 meter = 100 cm


1 cm = 10 mm

$$\lambda = \frac{0.3 \times 1.76625 \times 10^{-6}}{0.017 \times 10^{-6}}$$

$$= 31.19 \text{ m}$$

$$\lambda = 31.19 \text{ m}$$

Inductor (L): It does not allow any sudden change of current through it. It stores energy in the form of electromagnetic field. It is denoted by 'L'. It is a storage element. When a wire is wound forms L. Unit of Inductor is Henry (H)

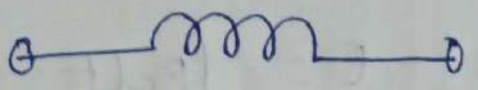Symbol : 

$V \propto I$ (from Ohm's law)
voltage across inductor

$$V \propto \frac{di}{dt}$$

$$V = L \frac{di}{dt}$$

L
Henry (H)

$$V \propto I$$

$$V \propto \frac{di}{dt}$$

$$V = L \frac{di}{dt}$$

current across the inductor!

$$\frac{di}{dt} = \frac{V}{L}$$

$$\frac{V}{L} = \frac{di}{dt}$$

$$\int di = \int \frac{V}{L} dt$$

$$di = \frac{V}{L} dt$$

$$i = \frac{1}{L} \int V dt$$

$$i = \frac{1}{L} \int V dt$$

Power across the inductor

$$P = V \times I$$

$$= L \frac{di}{dt} \times I$$

$$\boxed{P = IL \frac{di}{dt}}$$

Energy stored in inductor.

$$E = \int P dt$$

$$= \int IL \frac{di}{dt} dt$$

$$= L \int I di$$

$$\star \boxed{E = \frac{LI^2}{2}}$$

When the inductor is connected to the battery it stores its energy in the form of electromagnetic field & when the battery is removed it provides its energy to the circuit or to the capacitor.

Capacitor (C) :


It is a basic electric element.

It is based on the principle of capacitance.

Capacitor is a storage element which stores energy in the form of electrostatic field.

It is denoted by 'C'.

Unit of capacitor is Faraday (F).

Symbol:  μF
 mF

Current stored in the capacitor:

Note: It stores energy in the form of electrostatic field.

It does not allow the sudden change of voltage in the circuit.

$$V = IR \quad q = CV \quad \frac{dq}{dt} = C \frac{dV}{dt}$$
$$\frac{dV}{dt} = \frac{1}{C} \frac{dq}{dt} \quad i = \frac{d}{dt}(CV) \quad i = C \frac{dV}{dt}$$
$$V = \frac{1}{C} \int i dt$$

$$i = c \frac{dv}{dt}$$

voltage across the capacitor:

$$\frac{dv}{dt} = \frac{1}{c} i$$

$$\int dv = \int \frac{1}{c} i dt$$

$$v = \frac{1}{c} \int i dt$$

Power across the capacitor:

$$P = v \times i$$

$$= v \times c \frac{dv}{dt}$$

$$P = c v \frac{dv}{dt}$$

Energy across the capacitor:

$$E = \int P dt$$

$$= \int c v \frac{dv}{dt} dt$$

$$E = \frac{1}{2} c v^2$$

Types of Elements:

- (i) Active & passive
capable to deliver energy
not capable to provide energy but store energy
- (ii) linear & non linear.
- (iii) lumped & distributed.
- (iv) Unilateral & Bilateral.

Active & Passive elements:

Active elements: capable to provide energy for a very long time
There are nothing but energy sources like voltage and current


source & the passive elements include $\sqrt{\text{Resistor, Inductor, capacitor}}$. They are not capable of providing energy for a very long period of time.

linear & Non linear

I & V characteristics of these types of elements which passes through the origin and satisfies superposition


theorem, principle & ohm's law.
Principle known as linear elements:

Ex: R, L, C.

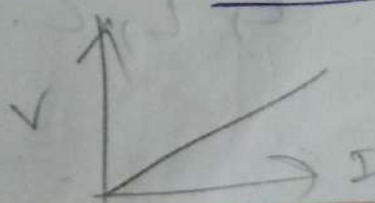

Non linear:
In current & voltage characteristics of these types of elements does not pass through origin & Does not satisfy superposition theorem, Principle called Non linear elements.

Ex: semiconductors like diodes.

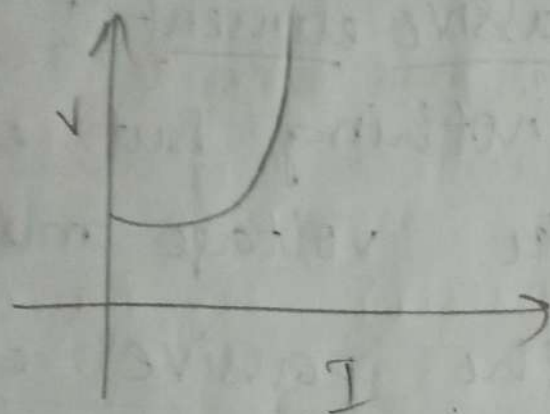

(iii) lumped & Distributed elements

↓
physically separable
small size devices.

↓ parameters
non physically
separable.

lumped elements: which are very small in size and we can separate it easily.

Ex: R, L, C .

Distributed elements:

size is very high which cannot be separated physically


Ex: Transmission lines.

(iv) Unilateral & Bilateral elements:

current passes from anode to cathode

Elements which can conduct current in only one direction known as Unilateral elements

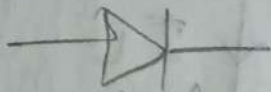Ex: Diode, SCR (Silicon control Rectifier)




anode, cathode are terminals

Elements which are having two directions or which can conduct current in both the directions known as Bilateral elements.

Ex: R, L, C.

Types of Sources:



(i) Independent

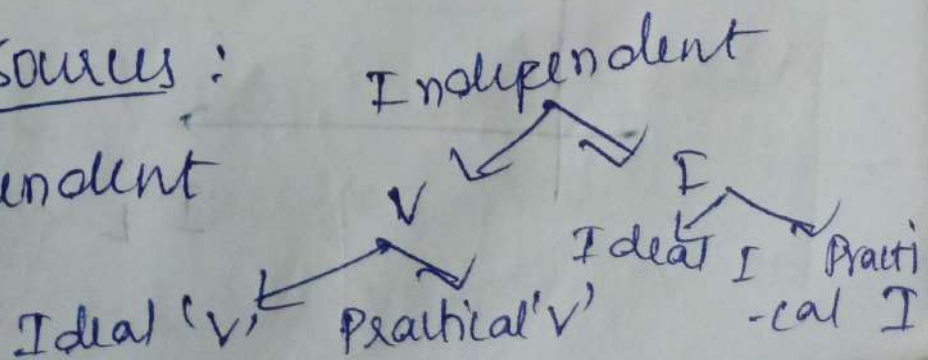



(ii) Dependent

VDVS	VDCS	CDCS	CDVS
voltage dependent voltage source	voltage dependent current source	current dependent current source	current dependent voltage source

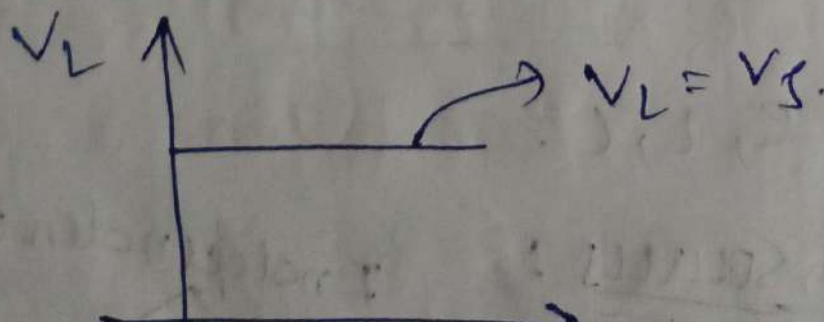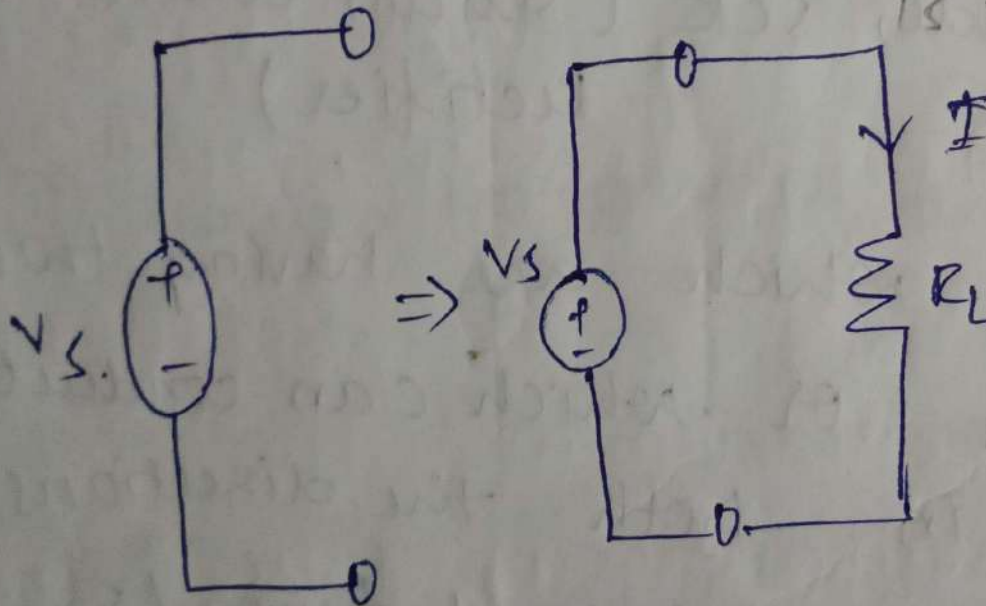① Ideal (v) source: voltage across the load & source is same irrespective of difference in current



② Practical 'V' source!

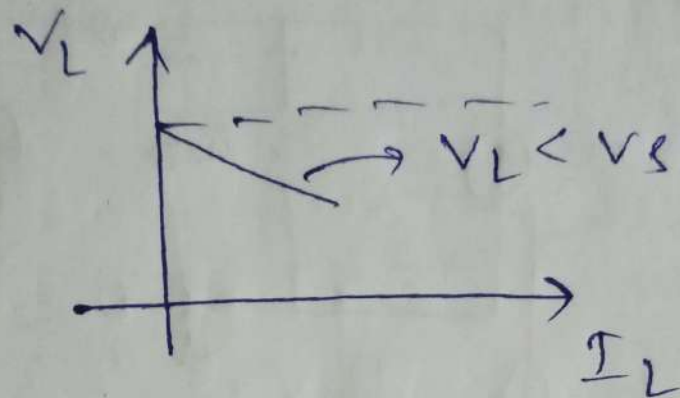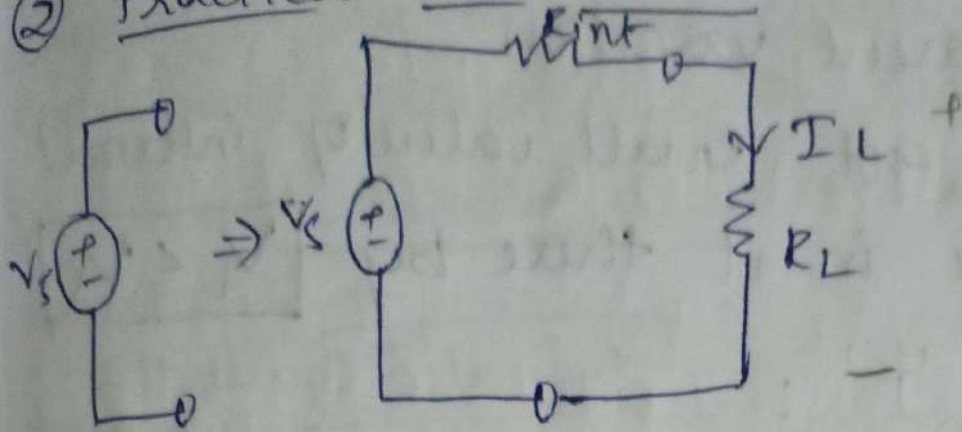

① Ideal voltage source!

It is a voltage source which gives constant to the load terminals irrespective of load current variation

$$V_L = V_s$$


② Practical voltage source!

It is the voltage source which delivers the specified value of voltage or reduced voltage to the


the load terminals with respect to load current variation.

It has got small value of internal resistance in it there by $V_L < V_S$


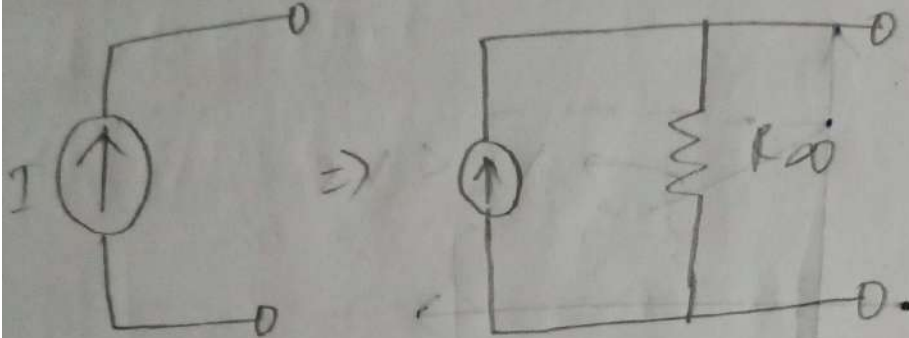
(iii) Ideal I : In Ideal 'I' source the value of



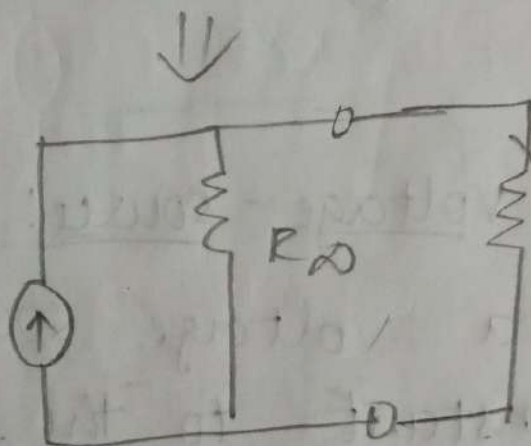R is ∞ (very high) so 'i' does not flow through it. & we remove R_{∞}






this is called load resistance R_L

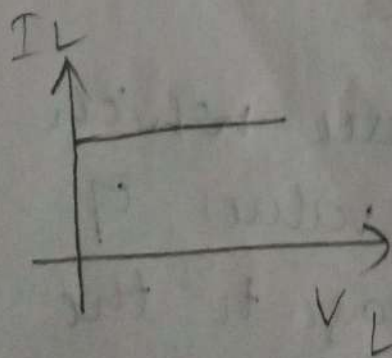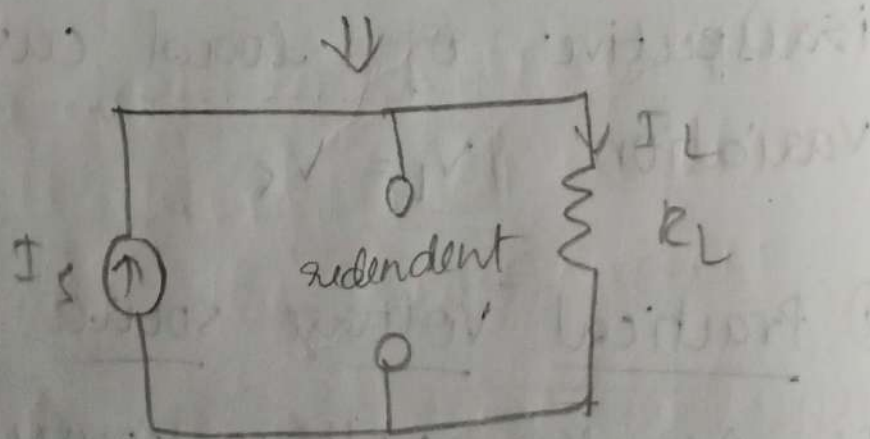

It is a current source which delivers constant value of load current to load terminals irrespective of load variations. It has infinite value of internal resistance.

$$I_L = I_S$$

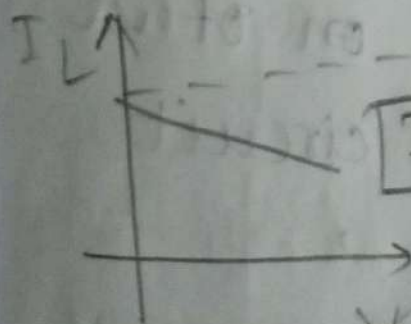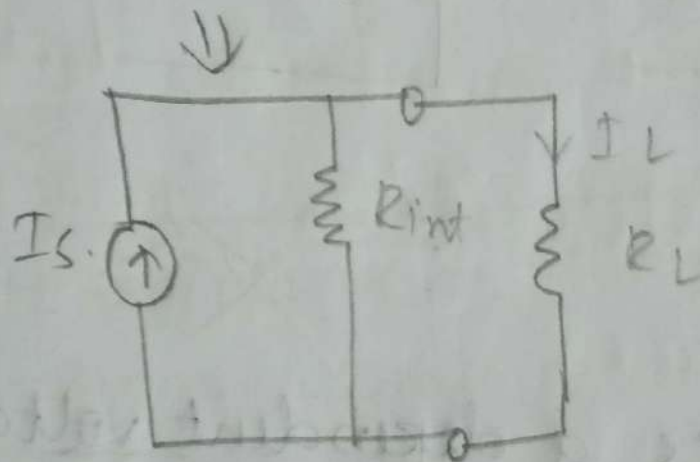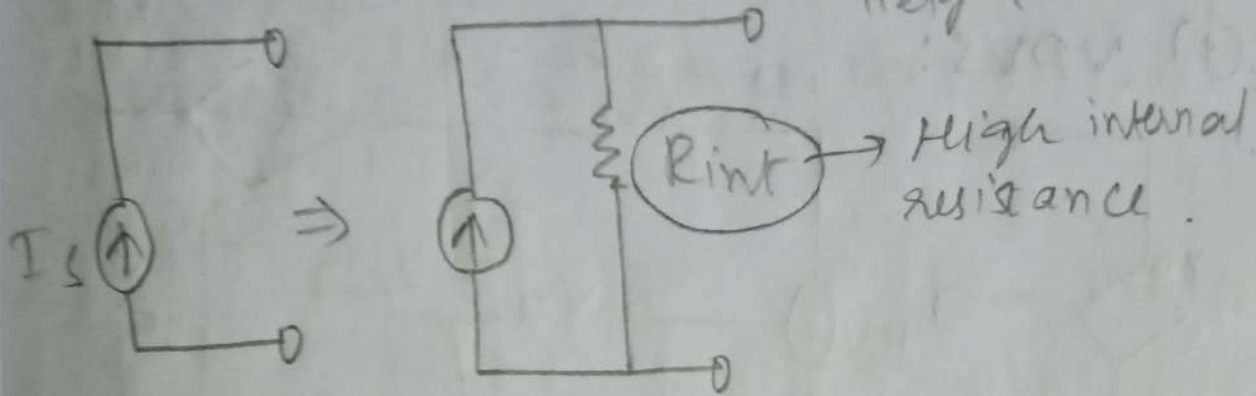(iv) Practical I : In current source int resistor is connected in parallel.



$$I_L < I_S$$


It is a current source which delivers specified value of current or

reduced value of current to load terminals w.r.t load voltage variations
 → It has got high internal resistance


$$I_L < I_S$$

(ii) Dependent :

(i) V DVS:

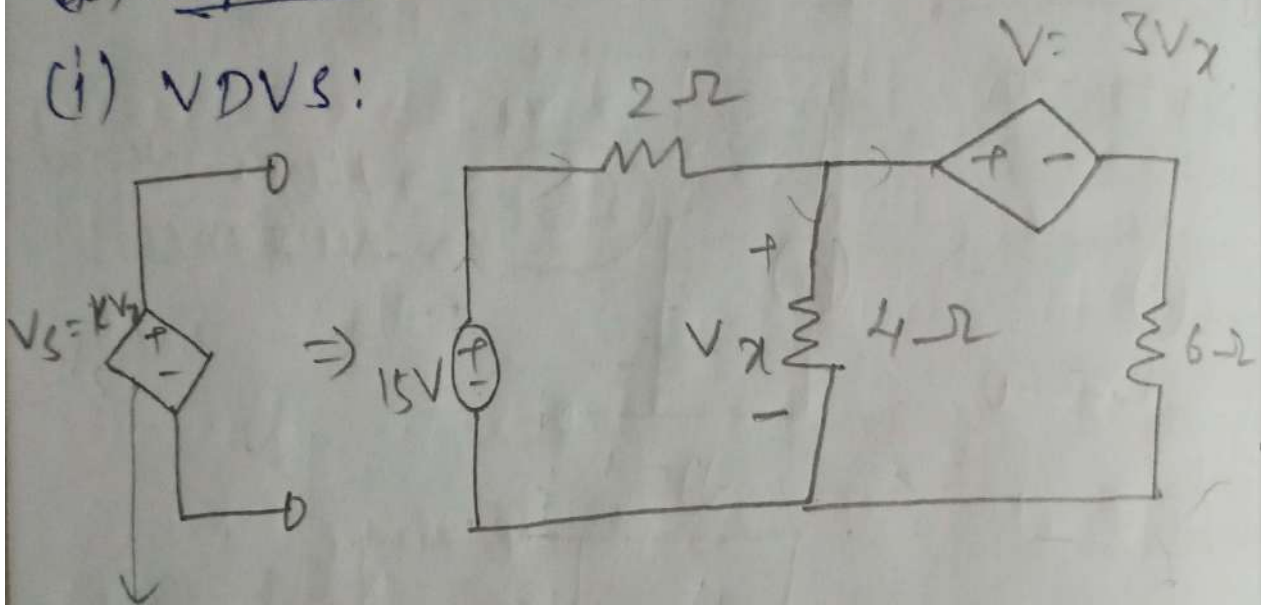

dependent voltage
source

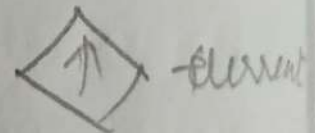


It is a dependent voltage source whose voltage depends on other element ^{voltage} in the same circuit

Dependent source




(ii) VDIS:

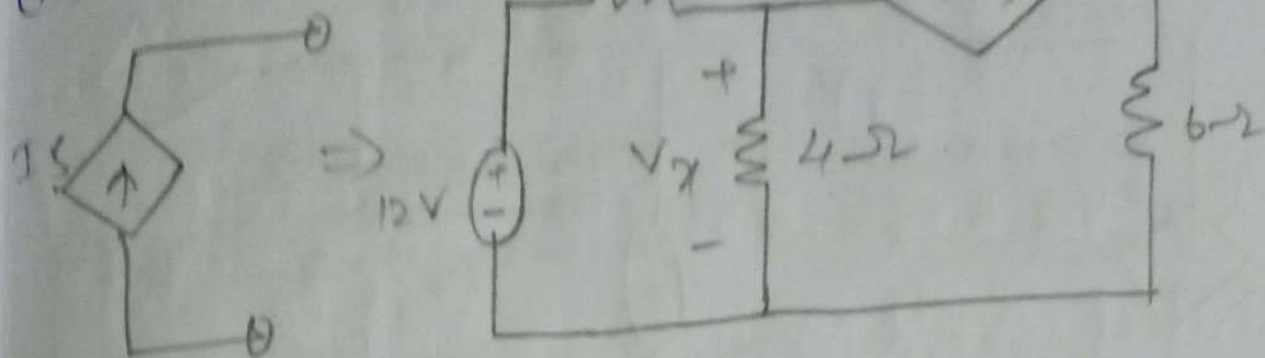

It is a dependent current source which depends on other element voltage in the same circuit.

(iii) CDCS:

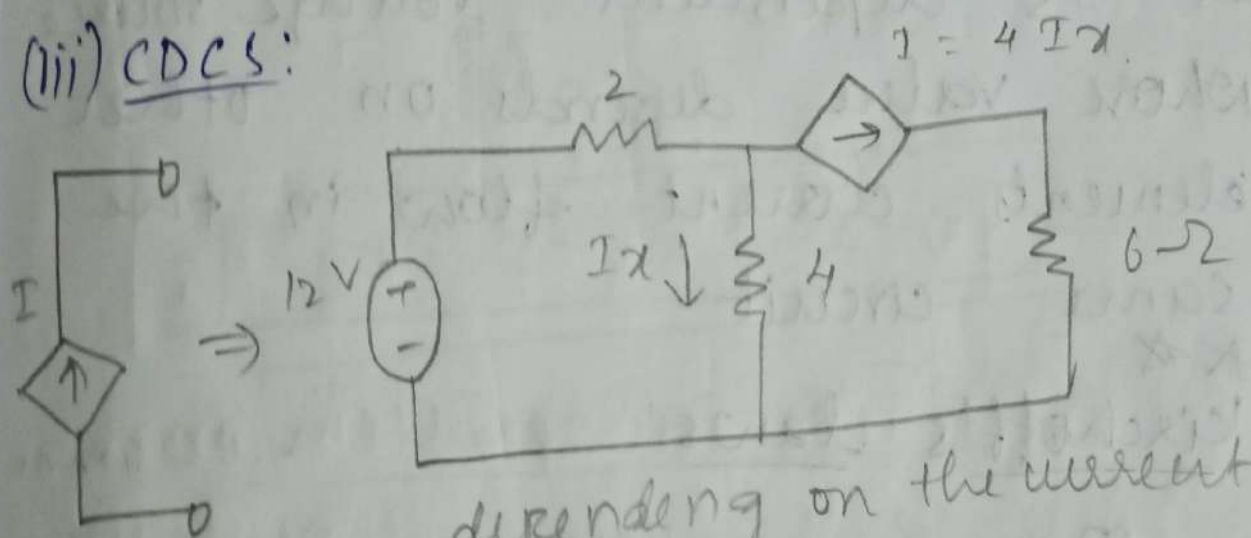


depending on the current from some element in the same circuit.

current dependent current source

It is dependent current source whose value depends on other elements in the same circuit.

4) KDVS:

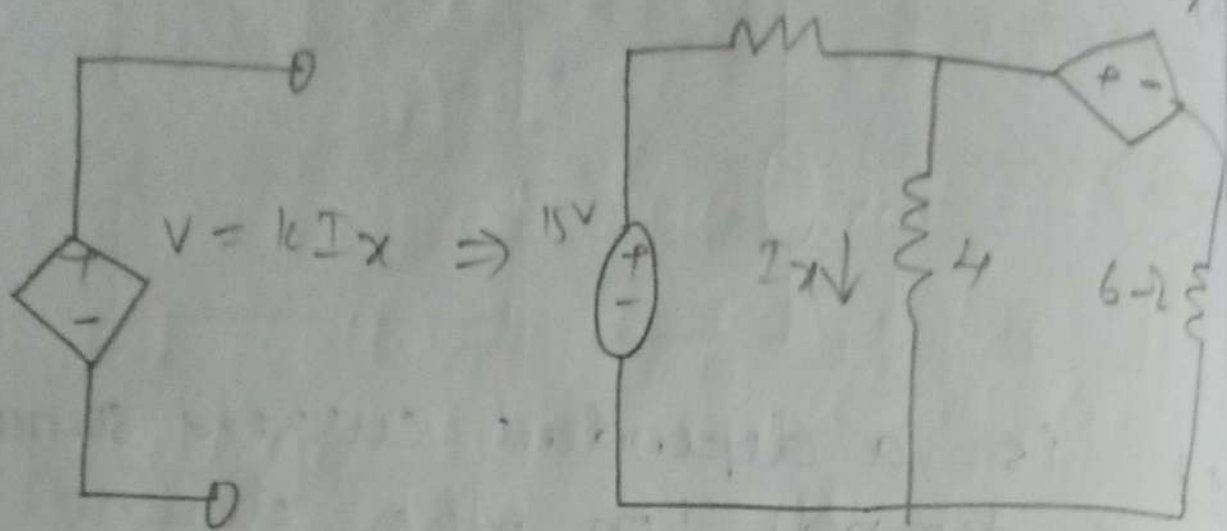

current dependent voltage source
It is dependent voltage source
whose value depends on other
elements current flow in the
same circuit.

★★
Kirchoff's laws! problem in exam


- ① KCL
- ② KVL.

1) Kirchoff's current law :

It states that algebraic sum
of all the currents meeting at
a common point or junction or

node is equal to zero
(or)

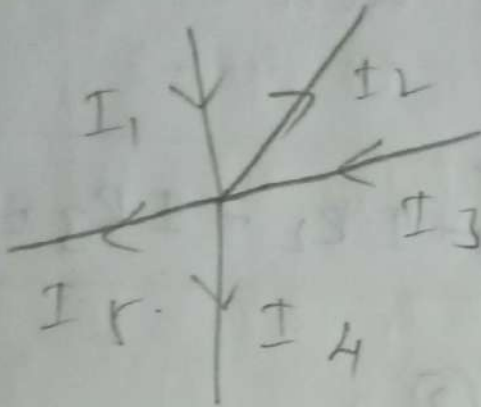
The algebraic sum of incoming currents is equal to algebraic sum of out going current.



$$I_1 + I_3 = I_2 + I_4 + I_5 \quad \text{--- (1)}$$

$$I_1 + I_3 - I_2 - I_4 - I_5 = 0 \quad \text{--- (2)}$$

(ii) Kirchoff's voltage law:

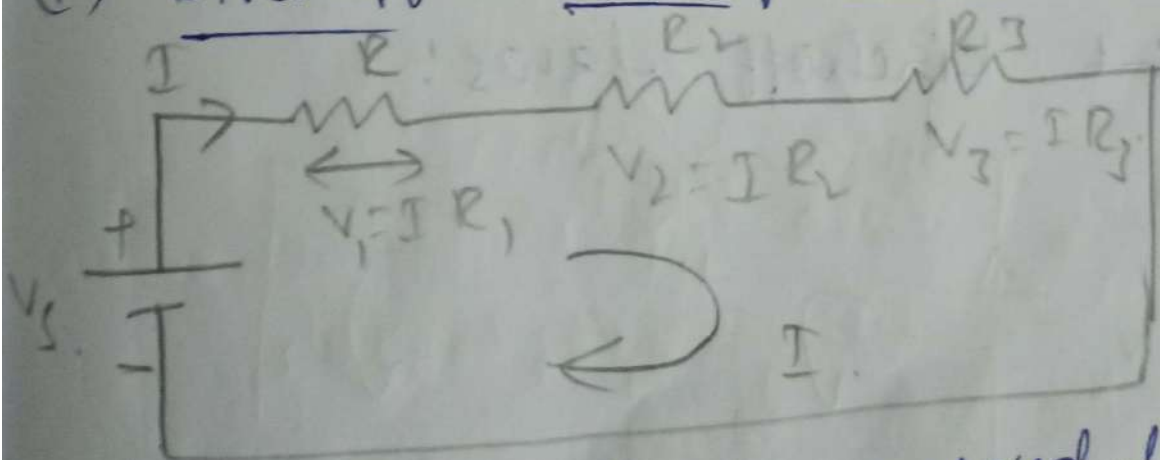

It states that in a closed loop algebraic sum of voltage drop

across the each and every element is equal to zero

(or)

In a closed loop total voltage total voltage is equal to sum of voltage drop across each & every element.


$$-V_s + IR_1 + IR_2 + IR_3 = 0.$$

①

②

$$V_s = IR_1 + IR_2 + IR_3$$

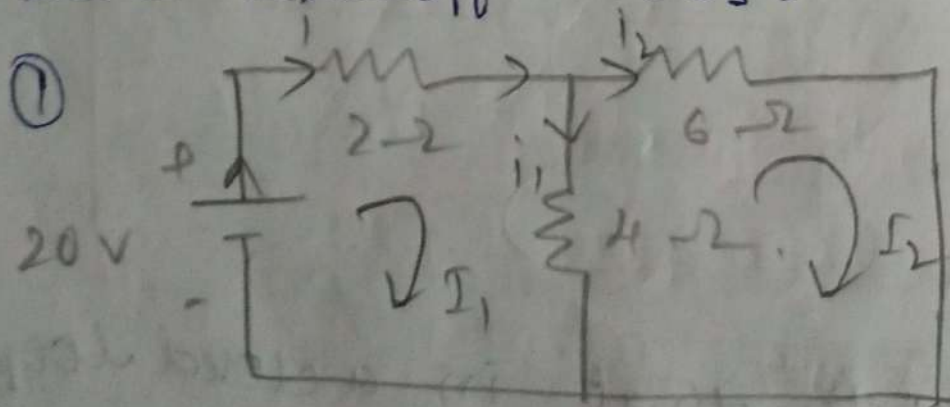Q) Determine current through each and every element using KVL kirchoff laws?



$$-20V + 2i_1 + i_2 \cdot 4 + i_3 \cdot 6$$

Applying KVL to loop 1

$$-20 + 2I_1 + 4(I_1 - I_2) = 0$$

$$2I_1 + 4I_1 - 4I_2 = 20$$

$$6I_1 - 4I_2 = 20 \quad \text{--- (1)}$$

Applying KVL to loop 2.

$$6I_2 + 4(I_2 - I_1) = 0$$

$$6I_2 + 4I_2 - 4I_1 = 0$$

$$-4I_1 + 10I_2 = 0$$

$$2(3I_1 - 2I_2 = 10)$$

$$3(-2I_1 + 5I_2 = 0)$$

$$6I_1 - 4I_2 = 20$$

$$-6I_1 + 15I_2 = 0$$

$$11I_2 = 20$$


$$I_2 = \frac{20}{11}$$

$$-4I_1 + 10\left(\frac{20}{11}\right) = 0$$

$$-44I_1 + 200 = 0$$

$$I_1 = \frac{50}{11} = 4.545 \text{ A}$$

1) determine I value from the circuit.

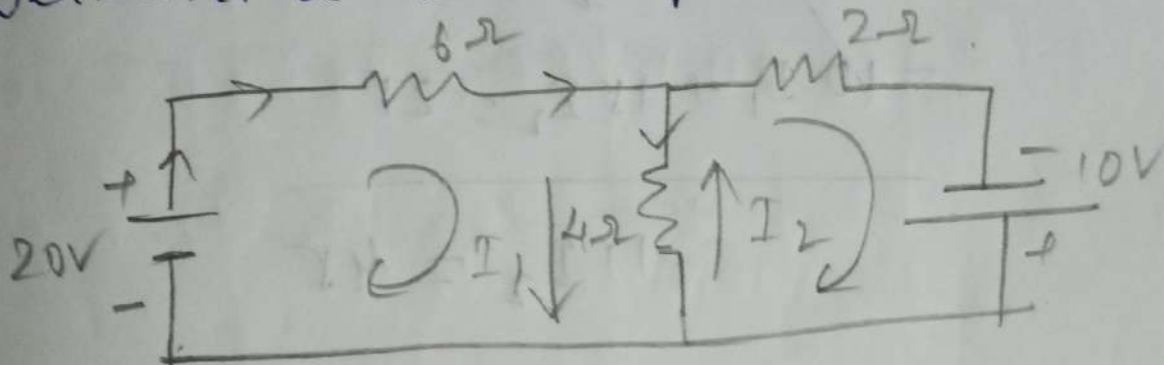

loop 1

$$-20 + 6I_1 + 4(I_1 - I_2) = 0$$

$$6I_1 + 4I_1 - 4I_2 = 20$$

$$10I_1 - 4I_2 = 20$$

$$5I_1 - 2I_2 = 10$$

loop 2

$$2I_2 - 10 + 4(I_2 - I_1) = 0$$

$$6I_2 - 4I_1 - 10 = 0$$

$$3I_2 - 2I_1 = 5$$

$$2(5I_1 - 2I_2 = 10)$$

$$5(-2I_1 + 3I_2 = 5)$$

$$10I_1 - 4I_2 = 20$$

$$-10I_1 + 15I_2 = 25$$

$$11I_2 = 45$$

$$I_2 = \frac{45}{11}$$


$$5I_1 - 2\left(\frac{45}{11}\right) = 10$$

$$55I_1 - 90 = 110$$

$$55I_1 = 200$$

$$I_1 = \frac{200}{55} = 40$$

$$I_1 = \frac{40}{11}$$

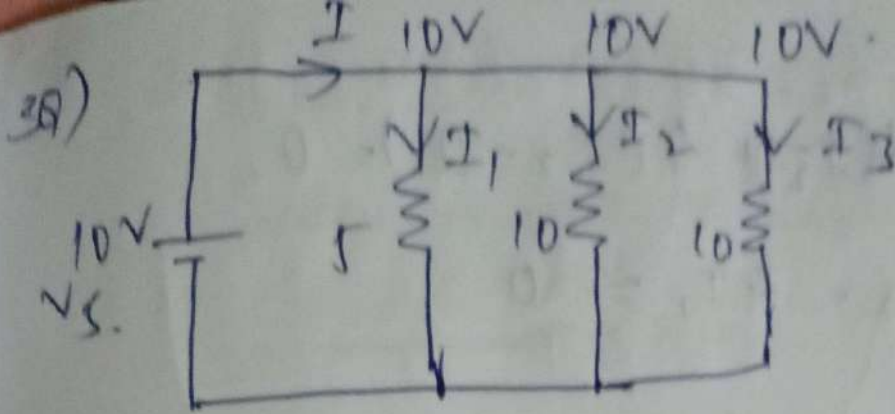

find out the value of i

→ KCL


$$\rightarrow I = I_1 + I_2 + I_3$$

$$= \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$I = \frac{10}{5} + \frac{10}{10} + \frac{10}{10}$$

$$= 2 + 1 + 1$$

$$\boxed{I = 4A}$$

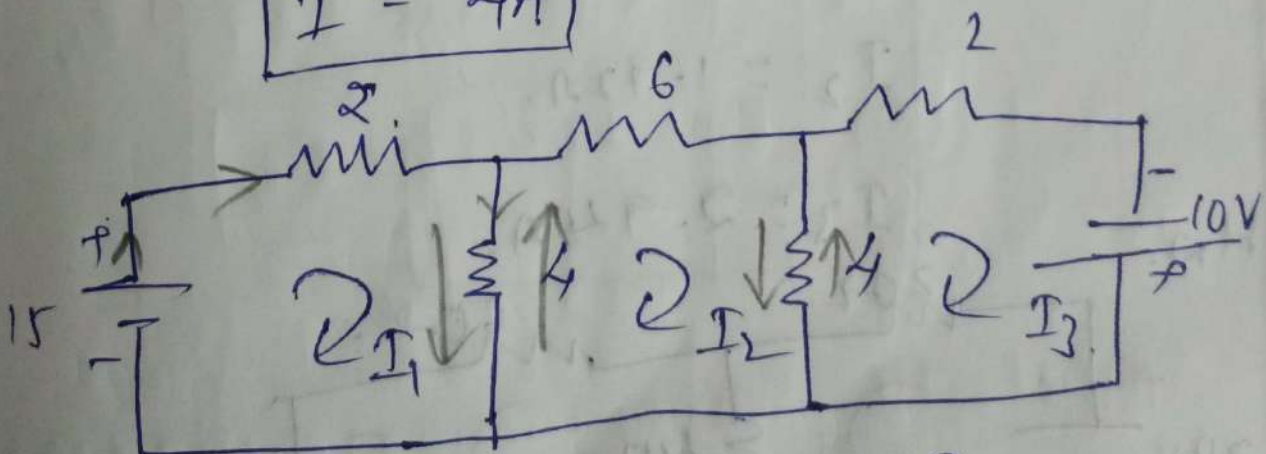

$$-15 + 2I_1 + 4(I_1 - I_2) = 0$$

$$6I_1 - 4I_2 = 15$$

loop 2:

$$6I_2 + 4(I_2) + 4(I_2 - I_1) = 0.$$

$$6I_2 + 8I_2 - 4I_1 = 0$$

$$14I_2 - 4I_1 = 0.$$

$$14I_2 - 4I_1 + 4I_3 = 0. \quad \text{--- (6)}$$

loop 3:

$$2I_3 - 20 + 4(I_3 - I_2) = 0.$$

$$2I_3 - 10 + 4I_3 - 4I_2 = 0.$$

$$6I_3 - 4I_2 = 10.$$


$$3I_3 - 2I_2 = 5. \quad \text{--- (7)}$$

$$I_1 = 3.78A.$$



$$I_2 = 1.92A.$$

$$I_3 = 2.94A.$$

H.W.

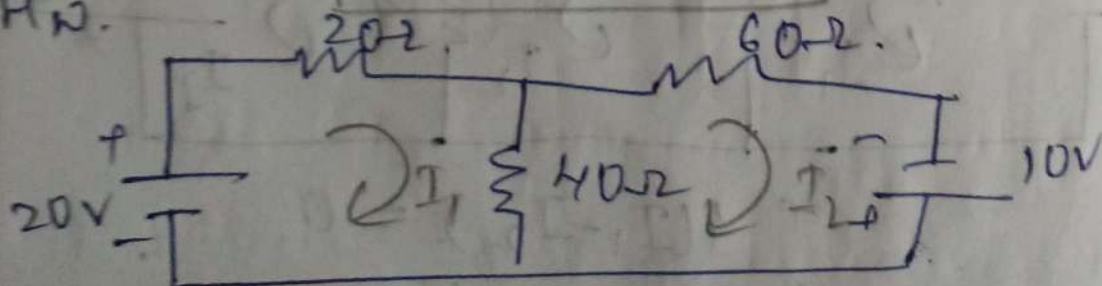

→ Resistors - Series Connection:

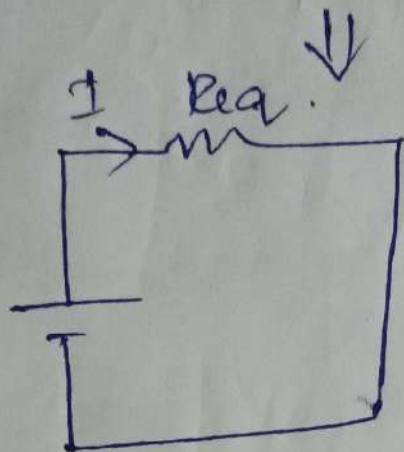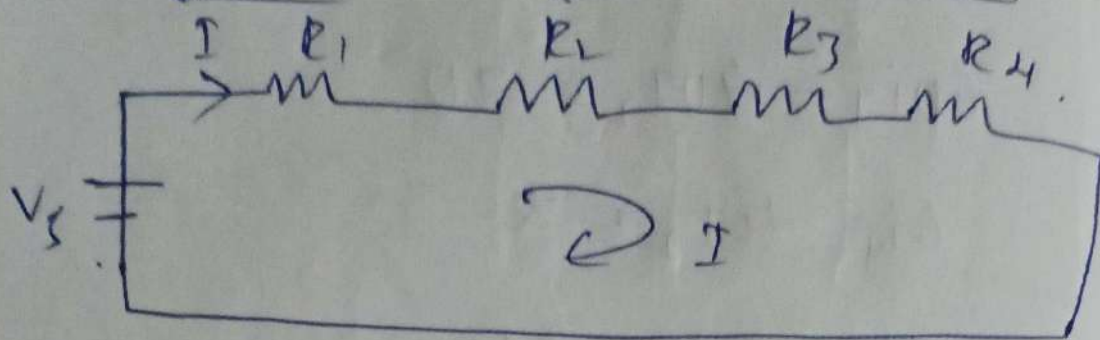

Equivalent circuit.

$$-V_s + V_1 + V_2 + V_3 + V_4 = 0.$$

$$V_1 + V_2 + V_3 + V_4 = V_s.$$

$$I R_{eq} = I R_1 + I R_2 + I R_3 + I R_4.$$


$$\boxed{R_{eq} = R_1 + R_2 + R_3 + R_4.}$$

In series connection R_{eq} is equal to summation of all resistors.

Consider a series, resistive circuit in which two resistors R_1 and R_2

are connected in series across one voltage source in these series circuits current is constant voltage drop across each resistor is given by IR .

Voltage division principle:

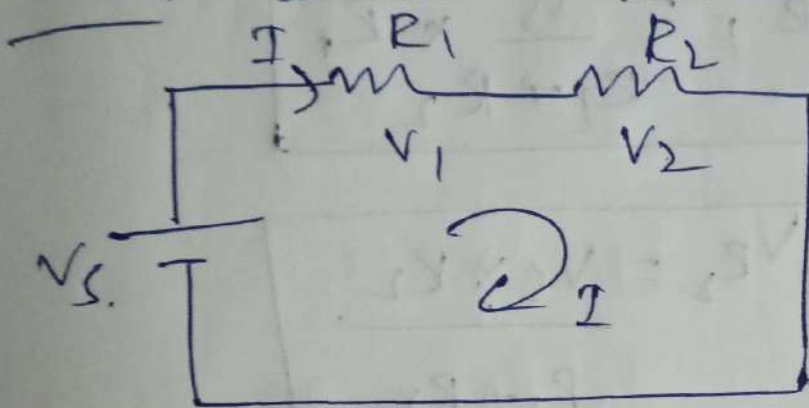

consider a series resistive circuit in which R_1 & R_2 are connected in series across a single voltage source. Here, since the circuit is series current is constant

$$-V_s + V_1 + V_2 = 0$$

$$V_s = V_1 + V_2$$

$$V_s = IR_1 + IR_2$$

$$V_S = I(R_1 + R_2)$$



$$I = \frac{V_S}{R_1 + R_2}$$

$$V_1 = IR_1$$

$$V_{R_1} = \frac{V_S \times R_1}{R_1 + R_2}$$

$$V_{R_2} = \frac{V_S \times R_2}{R_1 + R_2}$$

Resistor- Parallel combination:

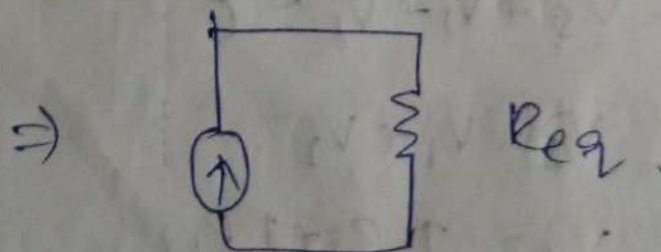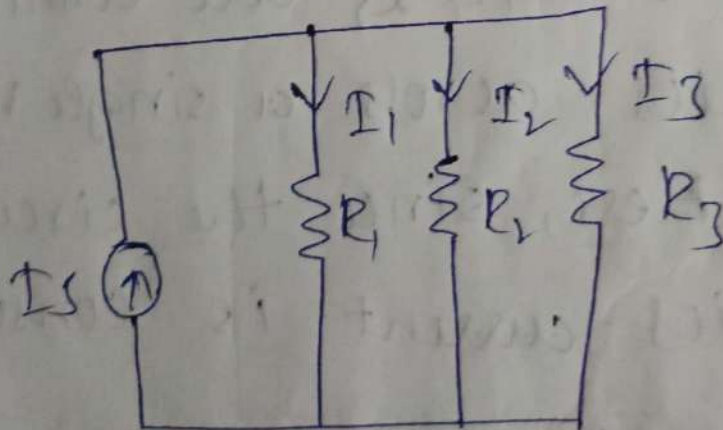

$$I_{CL} = I_1 + I_2 + I_3$$

$$\frac{V}{R_{eq}} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$I_s = \frac{V}{R_{eq}}$$


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

If n resistors are connected in parallel.

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

Current division principle:

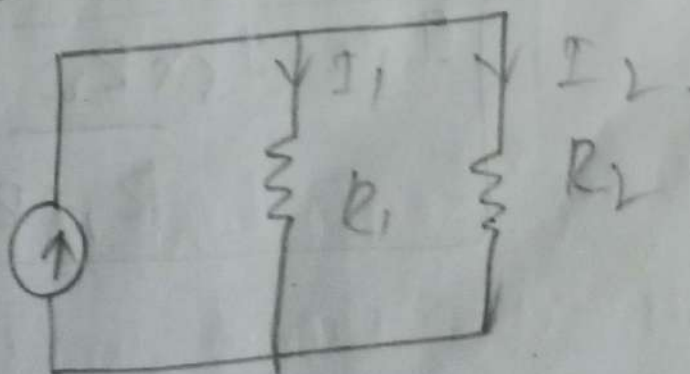current across single element in the circuit



KCL

$$I_S = I_1 + I_2$$

$$V_S = V_1 = V_2$$

$$V_1 = V_2$$

$$I_1 R_1 = I_2 R_2$$

$$I_1 = \frac{I_2 R_2}{R_1}$$

$$I_S = I_1 + I_2$$

$$= \frac{I_2 R_2}{R_1} + I_2$$


$$I_S = I_2 \left(\frac{R_2 + R_1}{R_1} \right)$$

$$I_2 = I_S \frac{R_1}{R_1 + R_2}$$

$$I_1 = I_S \frac{R_2}{R_1 + R_2}$$

Problem!

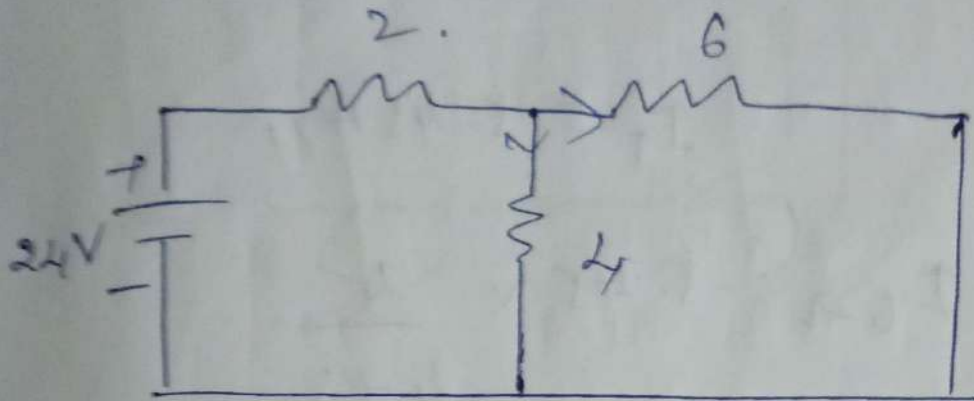1) Determine power dissipated by 6 ohms resistor & using required technique.



$$P = VI$$

$$P_{6\Omega} = I_6^2 R$$

$$I_6 = I_T \times \frac{4}{4+6}$$

$$I_T = \frac{V}{R_{eq}}$$

$$R_T \text{ (or) } R_{eq} = \frac{6 \times 4}{6+4} + 2$$

$$= \frac{24}{10} + 2$$

$$R_{eq} = 4.4 \Omega$$

$$I_T = \frac{V}{R_{eq}}$$

$$= \frac{24}{4.4}$$

$$I_T = 5.45 A //$$

$$I_{6\Omega} = 5.45 \times \frac{4}{4+6}$$

$$= \frac{5.45 \times 4}{10}$$

$$I_{6\Omega} = 2.18 A //$$


$$P_{6\Omega} = I_6^2 R_6$$

$$= (2.18)^2 \times 6$$

$$P_{6\Omega} = 28.512 W //$$

8) Determine R_{eq} b/w A & B terminals. as shown in the below

circuit. came in final exams

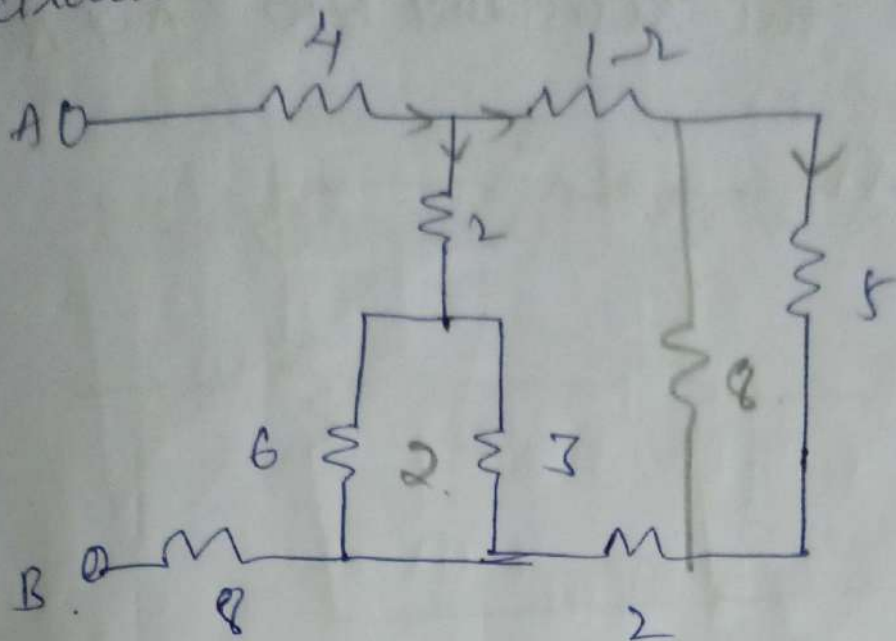


$$1 + 5 + 2$$

$$= 8$$

$$\frac{8 \times 8}{8+8}$$

$$4 +$$

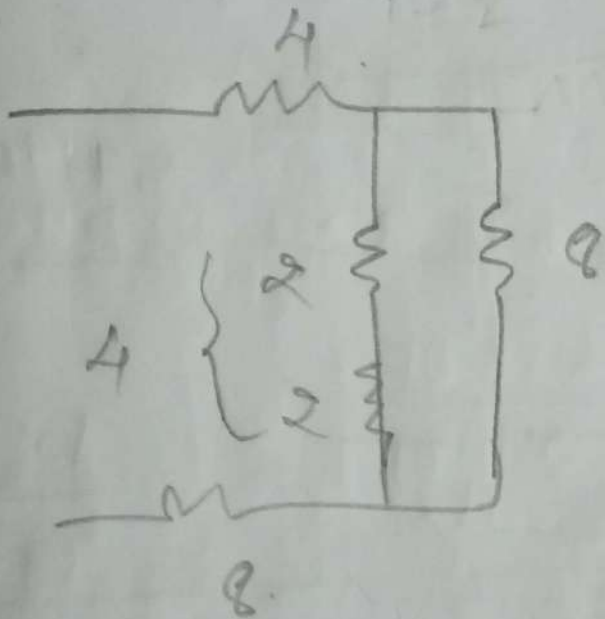


$$\frac{32}{4+8}$$

$$\frac{32}{12} = 8$$

$$12$$


$$3$$

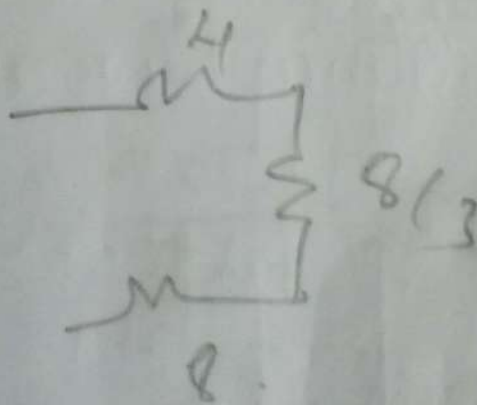

$$4 + 8/3 + 8$$

$$R_{AB} = 14.67$$


8) Evaluate the resistance b/w A & B

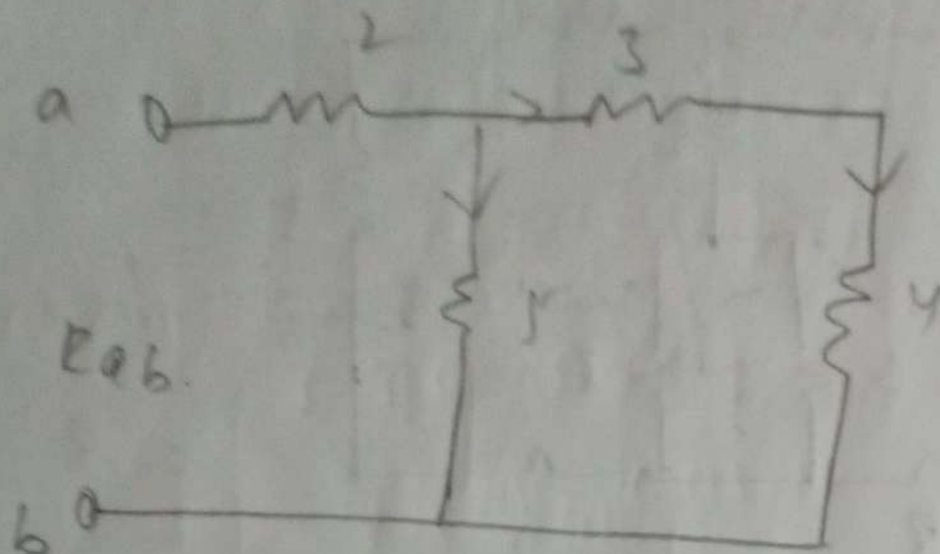


R_{ab}

3, 4 series

$$3+4=7$$

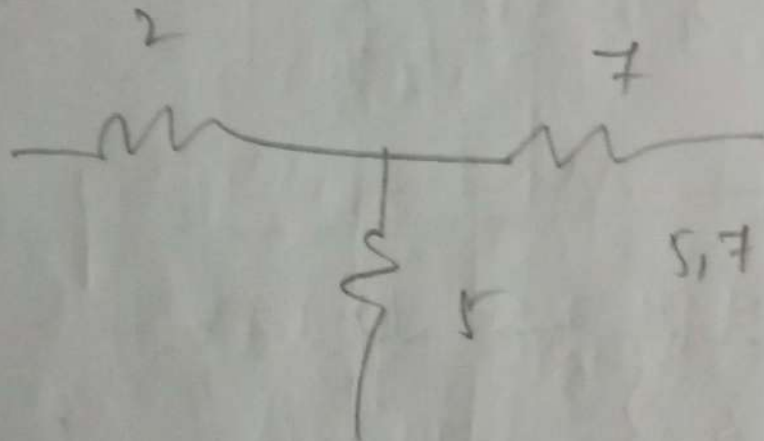

5, 7 ||

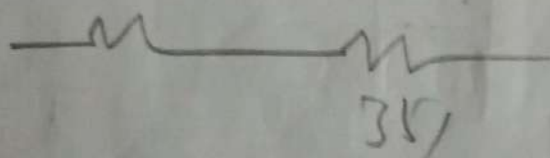

$$\frac{5 \times 7}{5+7}$$

$$5+7$$

$$\frac{35}{12}$$

$$12$$

$$2 + \frac{35}{12}$$



$$\frac{24+35}{12}$$

$$\frac{59}{12}$$

$$R_{ab} = 4.91$$


Always sort our nodes from left

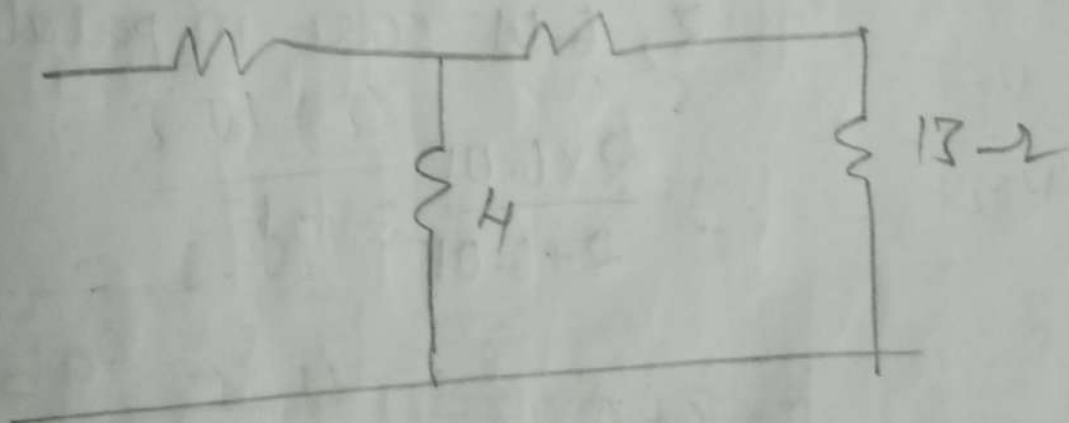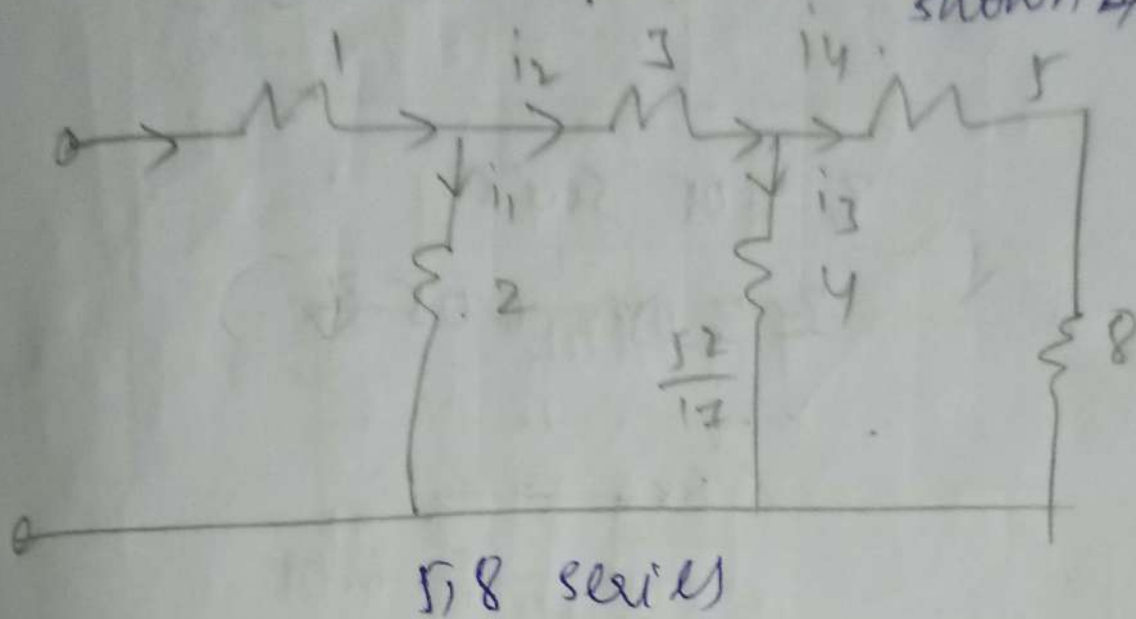8) calculate the resistance b/w
A B terminals of the circuit below
shown b/w.




4, 13 ||.
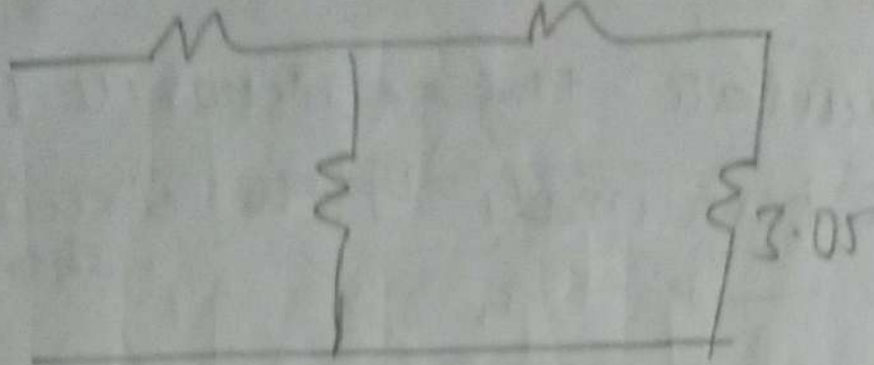
$$\frac{4 \times 13}{4 + 13} = 3.05 \Omega$$



3, 3.05 series.

$$3 + 3.05 = 6.05 \Omega$$

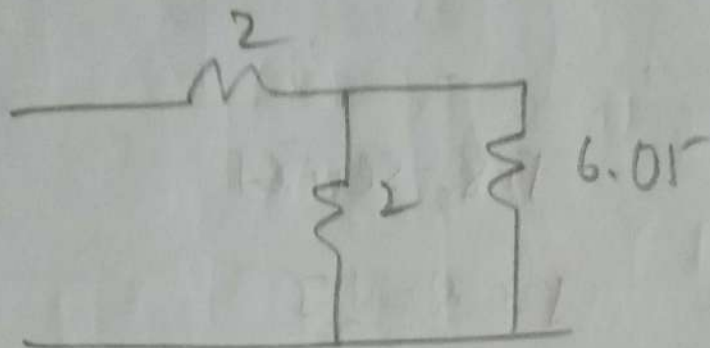


2, 6.05 are in parallel



$$\frac{2 \times 6.05}{2 + 6.05} = 1.5$$

$$1 + 1.5 = \boxed{2.5 = R_{ab}}$$

6 marks.

Q) Evaluate resistance b/w ab terminals

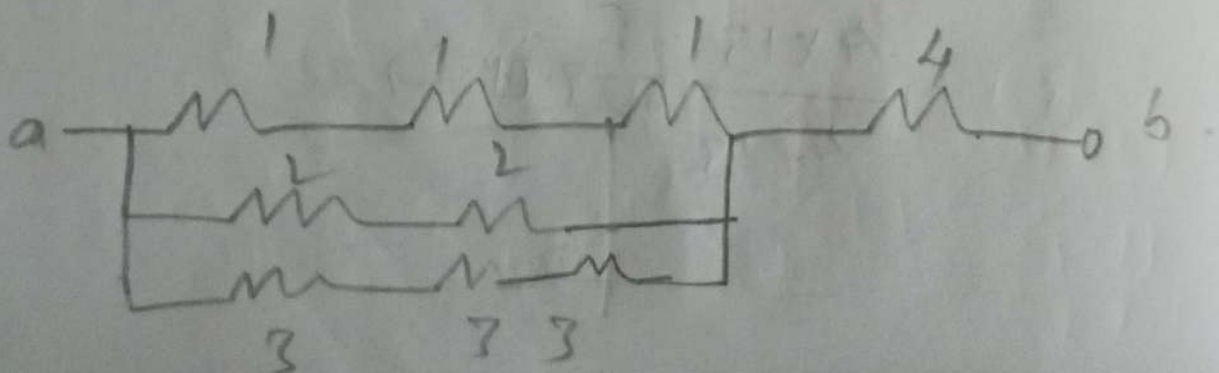

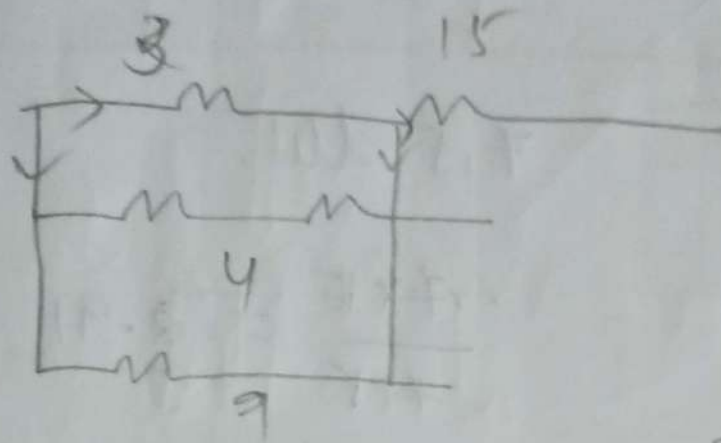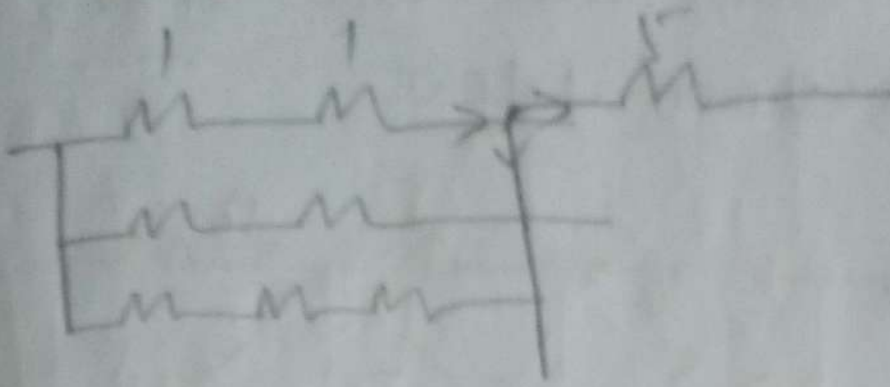

$$\frac{\frac{12}{7} \times 9}{\frac{12}{7} + 9} + 15 = \frac{\frac{3 \times 4}{7}}{\frac{12}{7} + 9} + 15$$


$$\frac{1.7 \times 9}{1.7 + 9} + 15$$

$$\frac{15.3}{10.7} + 15$$

$$1.42 + 4$$


$$R_{ab} = 5.42 \Omega$$

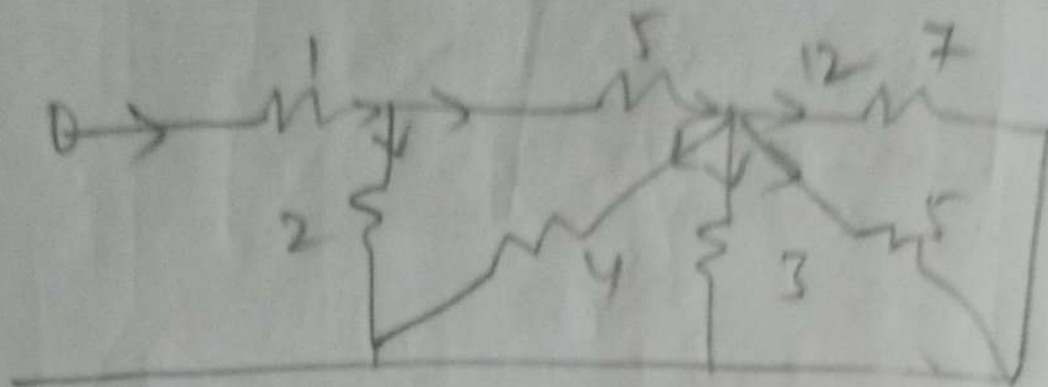Calculate the total resistance of the circuit shown below:




7,5 Ω .






$$\frac{7 \times 5}{7+5} = 2.91$$

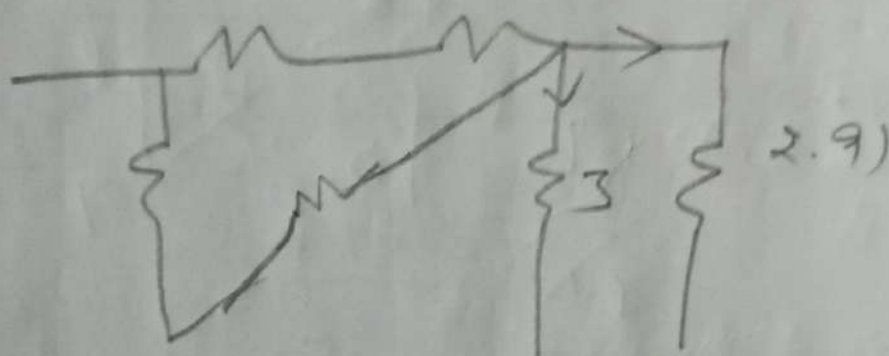


$$\frac{3 \times 2.91}{3+2.91} = 1.5$$

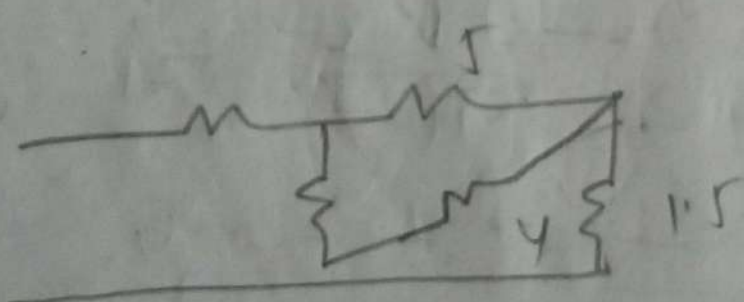


$$\frac{4 \times 1.5}{4+1.5} = 1.12$$

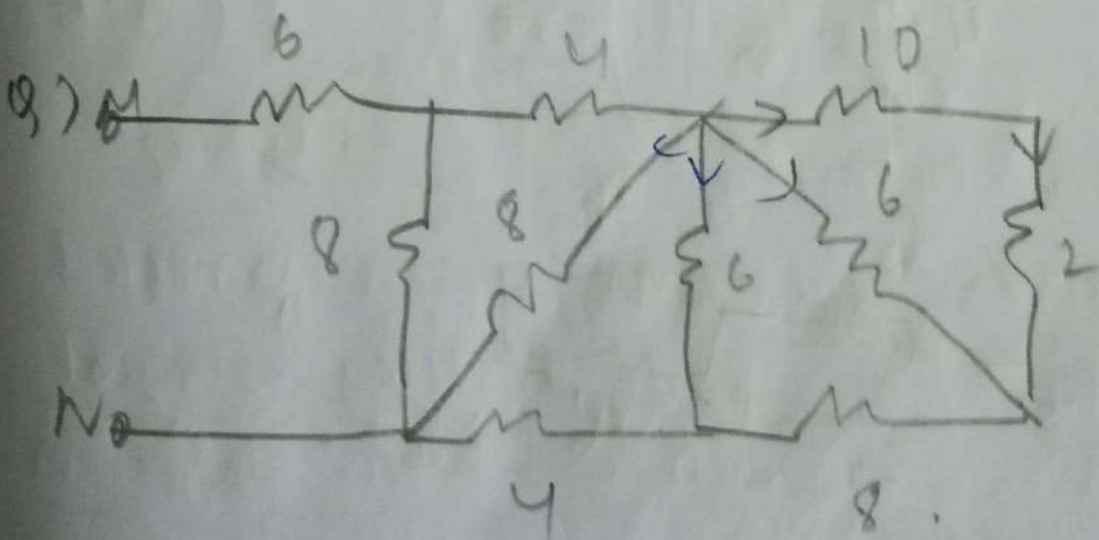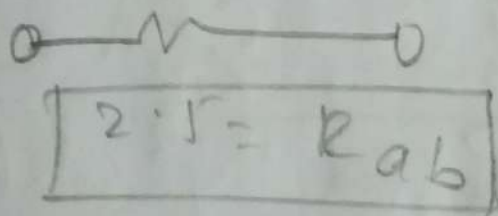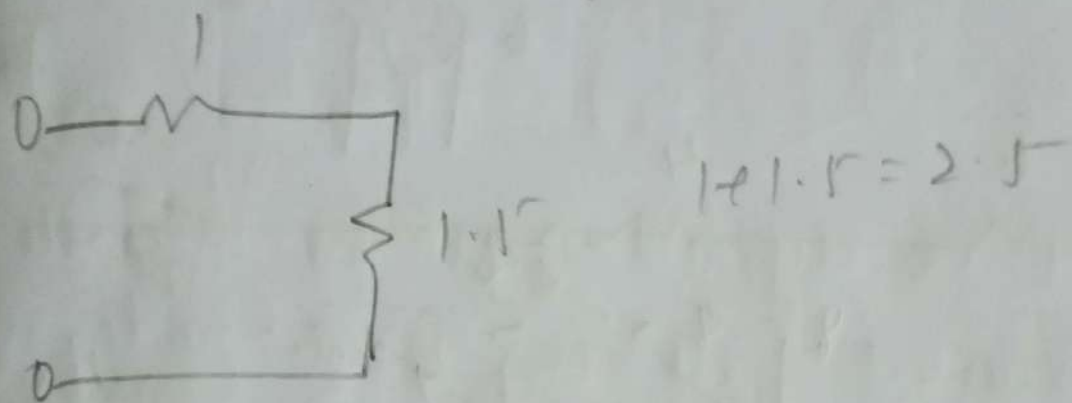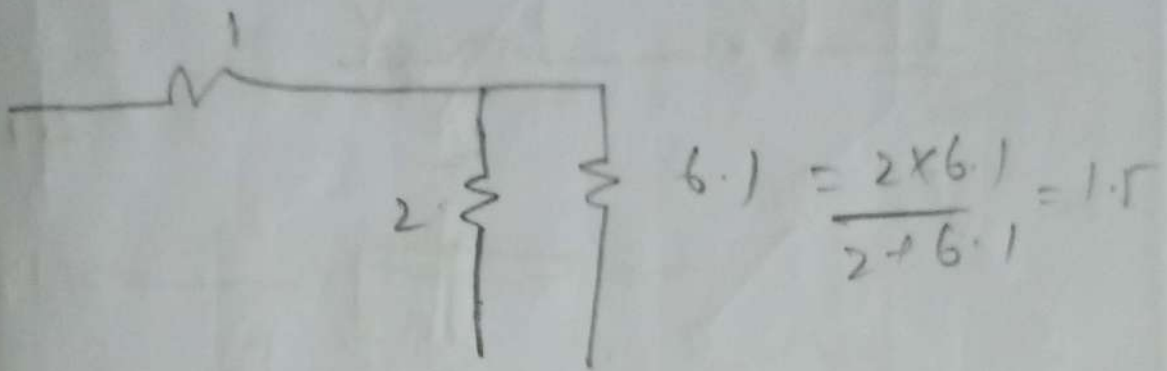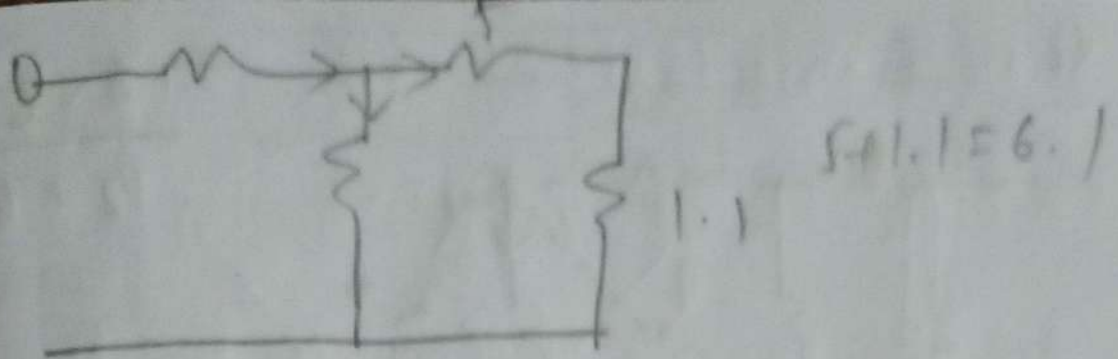

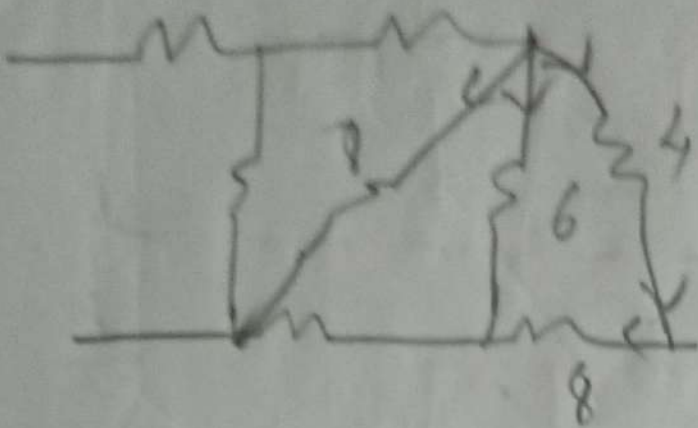


$$\frac{12 \times 6}{12 + 6}$$

$$4 + 8$$

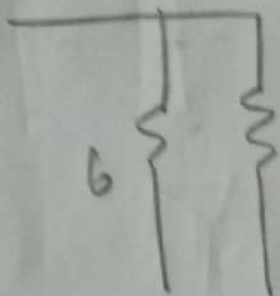

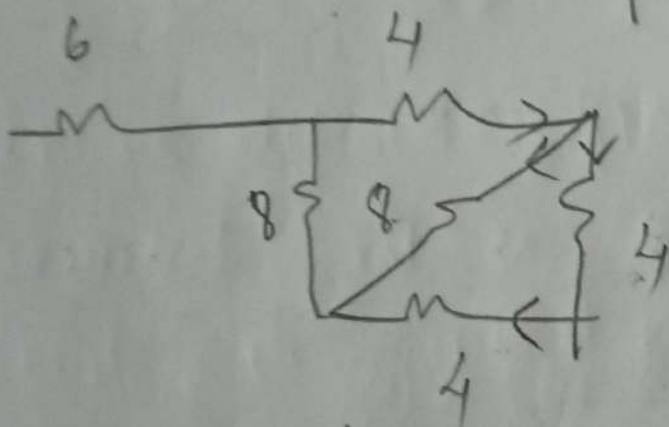
$$\frac{12 \times 4}{12 + 4} = \frac{12 \times 4}{16} = 3$$




$$\frac{8 \times 8}{8 + 8} = 4$$

$$\frac{4 \times 8}{4 + 8}$$

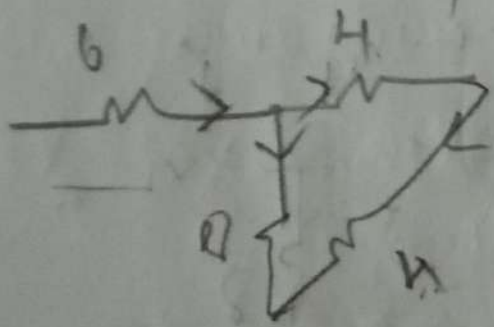

$$\frac{32}{12}$$

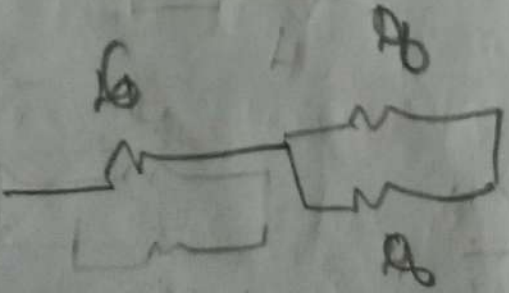


$$\frac{1}{4}$$

$$4$$

$$6 \times 4 = 10$$

Star Connection:

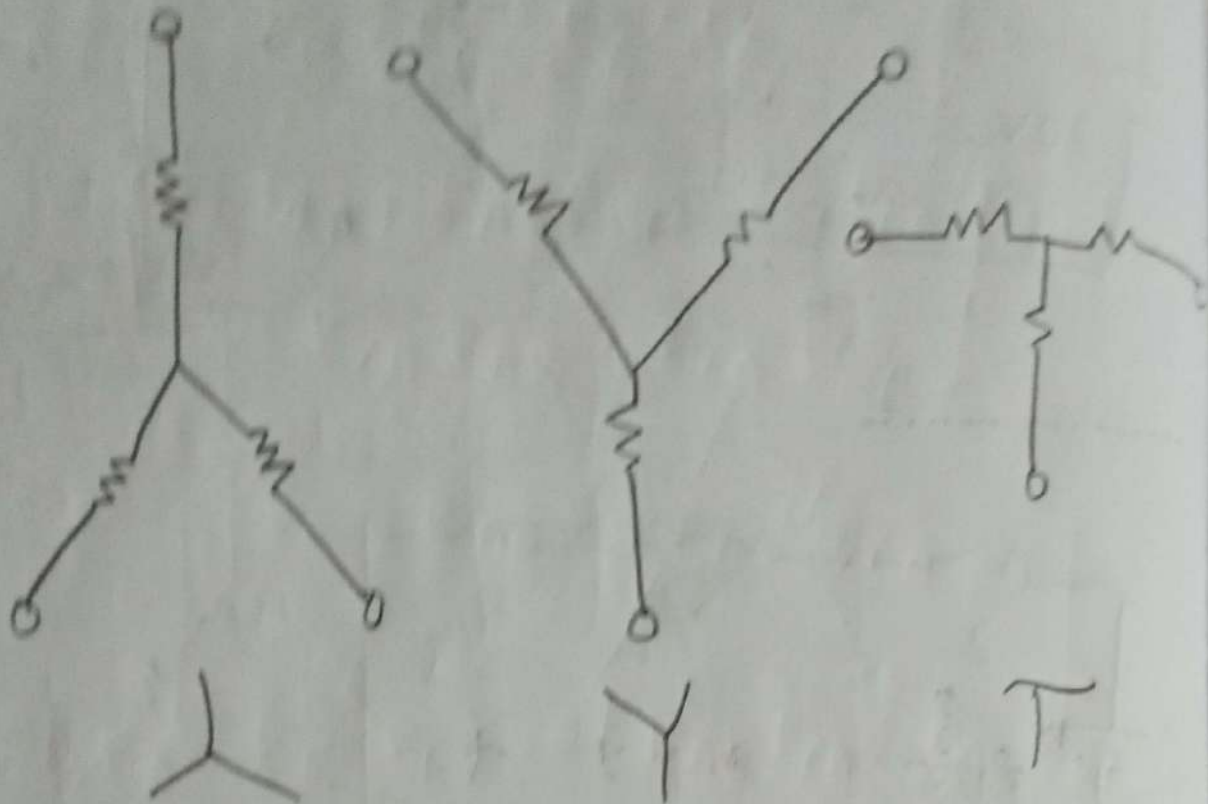



It is defined as the three elements connected at a single node, node point or neutral point known as star connection.

It is represented by \star (star)
(Y-network) Y (T-shape)
 $T \rightarrow$

Delta Connection:


Whenever 3 elements are connected together it forms a delta network either it will be Δ shape or π shape.

Delta Connection: 3 elements are taken

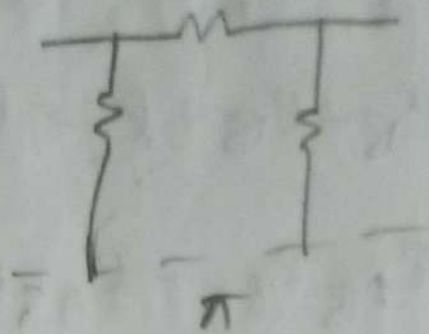
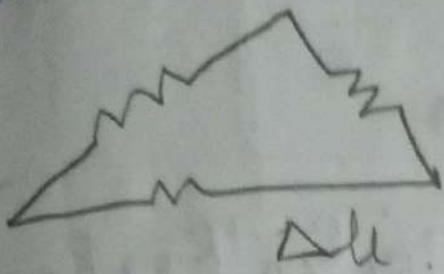


and connected together as a closed loop.

Delta to star Connection:

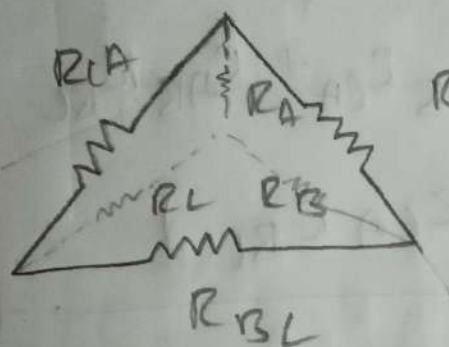

$R_A B \Rightarrow$

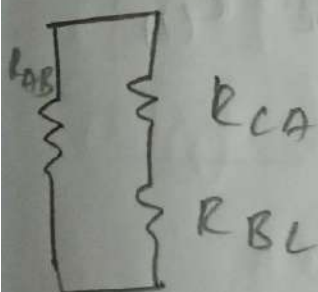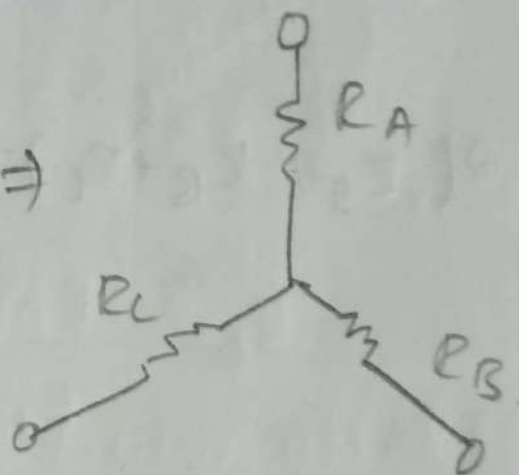

$$R_{AB} + R_B = \frac{R_{AB} \parallel (R_{CA} + R_{BC})}{R_{AB} + R_{BC} + R_{CA}} \quad \text{--- (1)}$$

$$R_B + R_C = \frac{R_{BC} \parallel (R_{CA} + R_{AB})}{R_{AB} + R_{BC} + R_{CA}} \quad \text{--- (2)}$$

$$R_C + R_A = \frac{R_{CA} \parallel (R_{AB} + R_{BC})}{R_{AB} + R_{BC} + R_{CA}} \quad \text{--- (3)}$$

Adding ① + ② + ③

$$R_A + R_B + R_C + R_C + R_C + R_A$$

$$= R_{AB} R_{CA} + R_{AB} R_{BC} + R_{BC} R_{CA} + R_{CA} R_{AB} + R_{CA} R_{BC}$$

$$R_{AB} + R_{BC} + R_{CA}$$

$$2(R_A + R_B + R_C) = 2(R_{AB} R_{CA} + R_{AB} R_{BC} + R_{CA} R_{BC})$$

$$R_{AB} + R_{BC} + R_{CA} \quad \text{--- ④}$$

$$\text{④} - \text{①}$$

$$R_A + R_B + R_C - R_A - R_B$$

$$= R_{AB} R_{CA} + R_{AB} R_{BC} + R_{CA} R_{BC}$$

$$R_{AB} + R_{BC} + R_{CA}$$

$$- \frac{R_{AB} R_{CA} + R_{AB} R_{BC}}{R_{AB} + R_{BC} + R_{CA}}$$

$$R_{AB} + R_{BC} + R_{CA}$$

$$R_C = \frac{R_{CA} R_{BL}}{R_{AB} + R_{BL} + R_{CA}}$$

$$(4) - (2)$$

$$R_A + \cancel{R_B} + \cancel{R_C} - \cancel{R_B} - \cancel{R_C}$$

$$= R_{AB} R_{CA} + \cancel{R_{AB} R_{BL}} + \cancel{R_{CA} R_{BL}}$$

$$- \cancel{R_{BL} R_{CA}} - \cancel{R_{BL} R_{AB}}$$

$$R_{AB} + R_{BL} + R_{CA}$$

$$R_A = \frac{R_{AB} R_{CA}}{R_{AB} + R_{BL} + R_{CA}}$$

$$(4) - (1)$$

$$\cancel{R_A} + R_B + \cancel{R_C} - \cancel{R_A} - \cancel{R_C}$$


$$= \cancel{R_{AB} R_{CA}} + R_{AB} R_{BL} + \cancel{R_{CA} R_{BL}}$$

$$- \cancel{R_{AB} R_{CA}} + \cancel{R_{CA} R_{BL}}$$

$$R_{AB} + R_{BL} + R_{CA}$$

$$R_R = \frac{R_{AB} R_{BC}}{R_{AB} + R_{BC} + R_{CA}}$$

Star to Δ transformation:

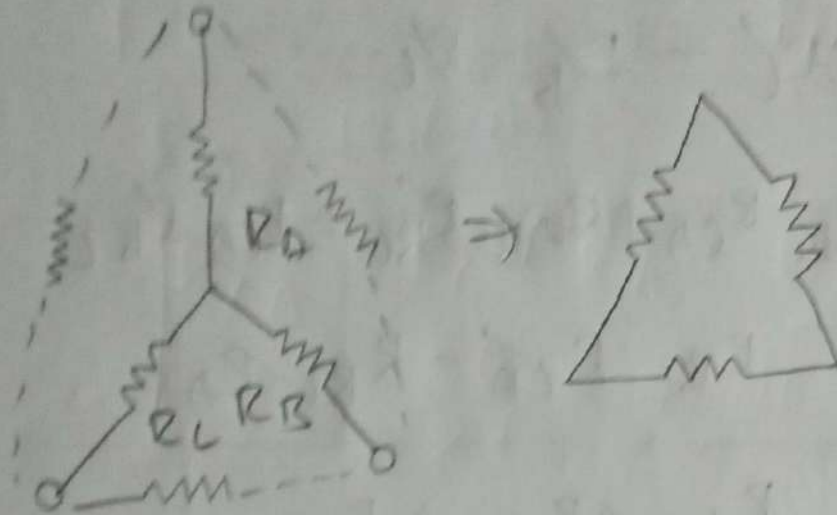

$$R_A = \frac{R_{AB} R_{CA}}{R_{AB} + R_{BC} + R_{CA}} \quad \text{--- (1)}$$

$$R_B = \frac{R_{BC} R_{AB}}{R_{AB} + R_{BC} + R_{CA}} \quad \text{--- (2)}$$

$$R_C = \frac{R_{CA} R_{BC}}{R_{AB} + R_{BC} + R_{CA}} \quad \text{--- (3)}$$

$$\textcircled{1} \textcircled{2} + \textcircled{2} \textcircled{3} + \textcircled{3} \textcircled{1}$$

$$R_A R_B + R_B R_C + R_C R_A$$

$$= \frac{R_A R_C \cdot R_B R_A B}{(R_A B + R_B C + R_C A)^2} + \frac{R_B C R_A B R_C A R_B C}{(R_A B + R_B C + R_C A)^2}$$

$$+ \frac{R_C A R_B C R_A B R_C A}{(R_A B + R_B C + R_C A)^2}$$

$$= \frac{R_A^2 R_B R_C + R_B^2 R_A R_C + R_C^2 R_A R_B}{(R_A B + R_B C + R_C A)^2}$$

$$(R_A B + R_B C + R_C A)^2$$

$$R_A R_C + R_A R_B + R_B R_C$$

$$= R_A R_B R_C (R_A B + R_B C + R_C A)$$

$$(R_A B + R_B C + R_C A)^4$$

$$4/1$$

$$\frac{R_C R_A + R_A R_B + R_B R_C}{R_A} = \frac{R_B C R_A B R_C A}{R_A B + R_B C + R_C A}$$

$$R_C + R_B + \frac{R_B R_C}{R_A} = R_{BC}$$

$$R_{AB} = R_A + R_B + \frac{R_A R_B}{R_C}$$

$$R_{CA} = R_C + R_A + \frac{R_C R_A}{R_B}$$

Problem:

Q) Delta values are given by 2Ω , 3Ω , and 4Ω resistances find star values


$$R_{AB} = 2\Omega$$

$$R_{BC} = 3\Omega$$

$$R_{CA} = 4\Omega$$

$$R_A = \frac{(2)(4)}{2+3+4}$$

$$= \frac{8}{9} \Omega = 0.88 \Omega$$

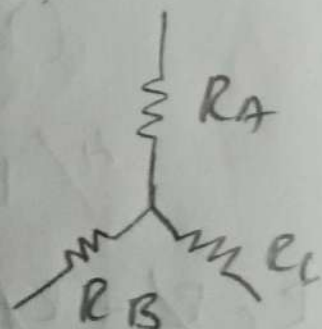

$$R_B = \frac{(2)(3)}{2+3+4}$$

$$= \frac{6}{9}$$

$$= 0.66 \Omega$$

$$R_C = \frac{(4)(3)}{2+3+4}$$

$$= \frac{12}{9}$$

$$= 1.33 \Omega$$

9) Star values are given by 4Ω , 5Ω , 6Ω find delta values.

$$R_A = 4\Omega, R_B = 5\Omega, R_C = 6\Omega$$

$$R_{AB} = 4 + 5 + \frac{20}{6}$$

$$= 9 + 3.3$$

$$= 12.33 \Omega$$

$$R_{CA} = (4) + 6$$

$$+ \frac{24}{5}$$


$$= 10 + 4.8$$

$$= 14.8 \Omega$$

$$R_{BC} = 5 + 6 + \frac{30}{4}$$

$$= 18.5 \Omega$$

Q)

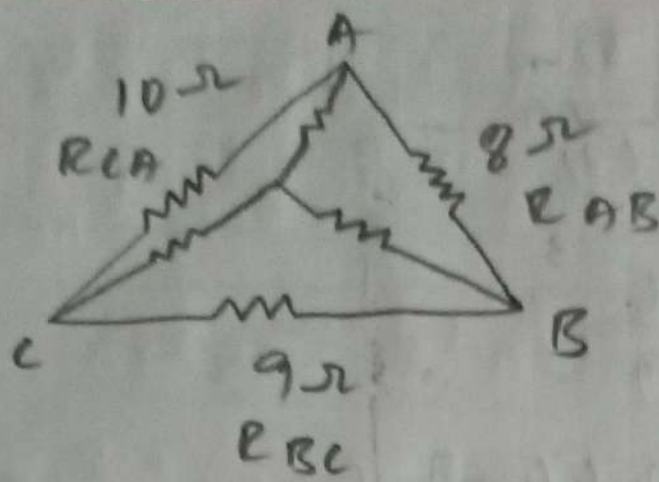

Star from
delta.

$$R_A = \frac{(8)(10)}{8+9+10}$$

$$= \frac{80}{27} = 2.96 \Omega$$

$$R_B = \frac{(8)(9)}{10+9+8}$$

$$= \frac{72}{27}$$



$$= 2.66 \Omega$$

$$R_C = \frac{(10)(9)}{27}$$

$$= \frac{90}{27}$$

$$= 3.33 \Omega$$

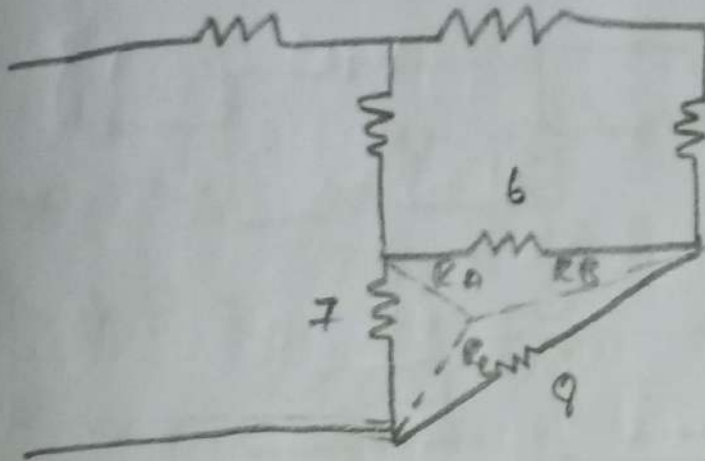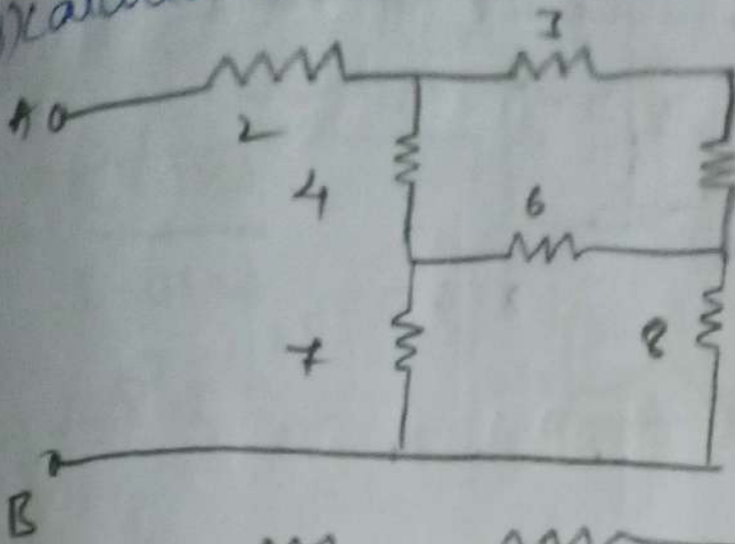Calculate the resistance b/w A & B terminals by using star delta transformation



$$R_A = \frac{7 \times 6}{7 + 6 + 8} = 2 \Omega$$

$$R_B = \frac{6 \times 8}{7 + 6 + 8} = 2.3 \Omega$$

$$R_C = \frac{7 \times 8}{6 + 7 + 8} = 2.6 \Omega$$

$$\frac{1}{10} + \frac{1}{6}$$


$$\frac{10}{10} + \frac{1}{6}$$



$$0.0977$$

$$0.166$$


$$= \frac{1}{0.263}$$

$$3 + 5 + 2.3 = 10.3$$

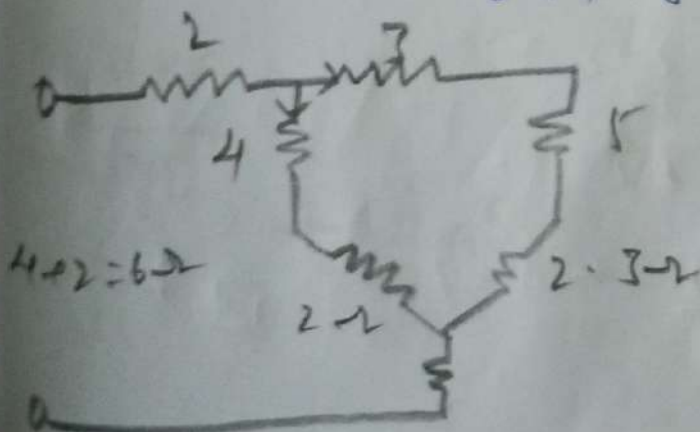

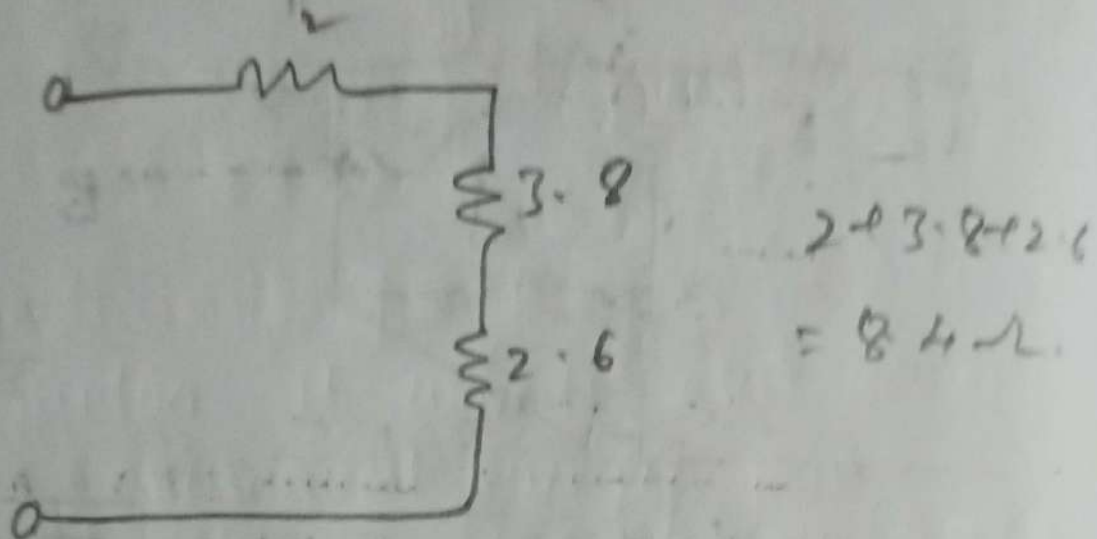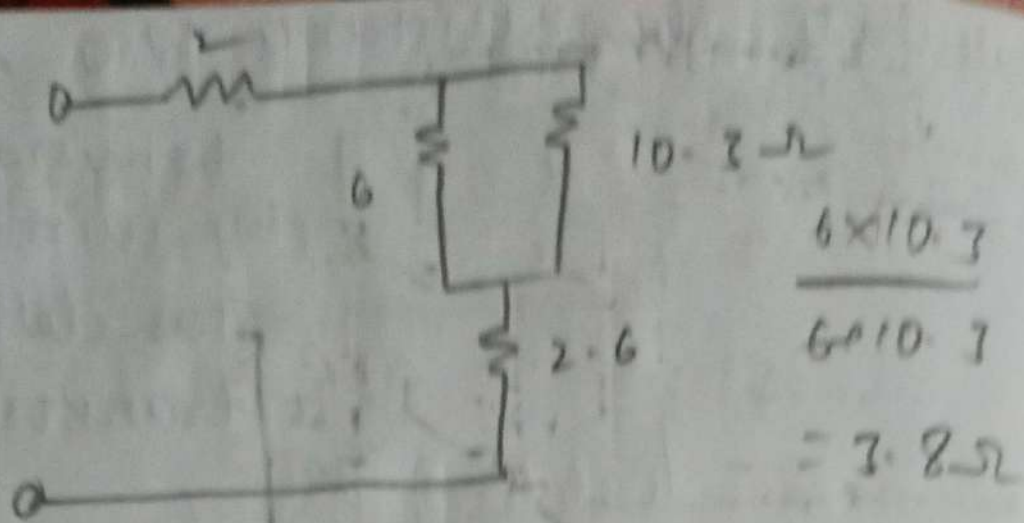


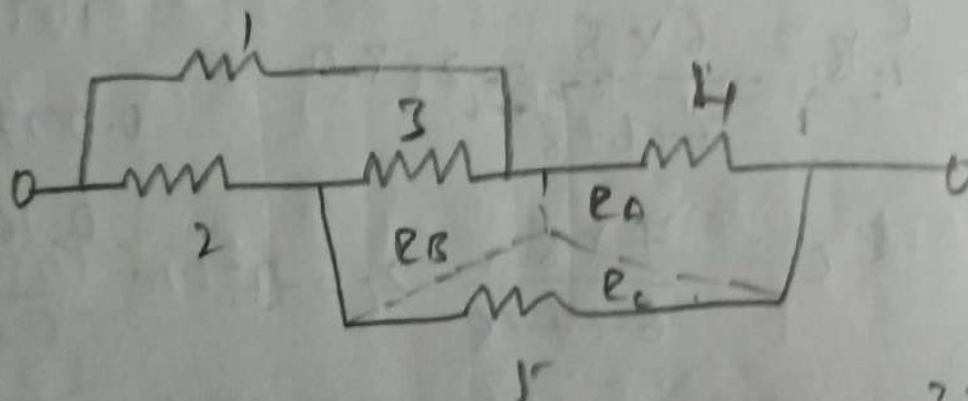
Q) calculate resistance b/w AB terminals.




$$\frac{3 \times 5}{12} = \frac{15}{12} = 1.25$$

$$R_A = 1 \Omega$$
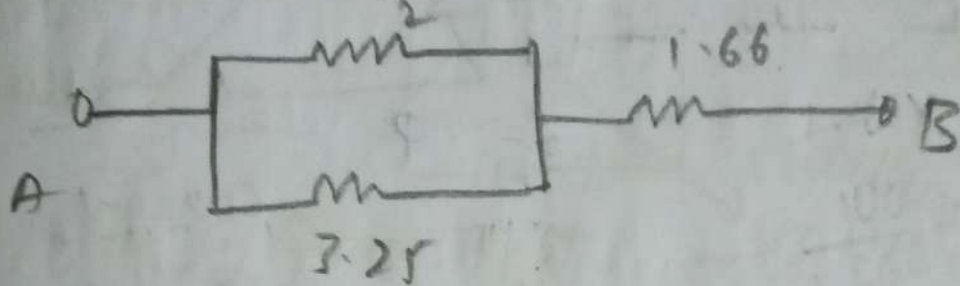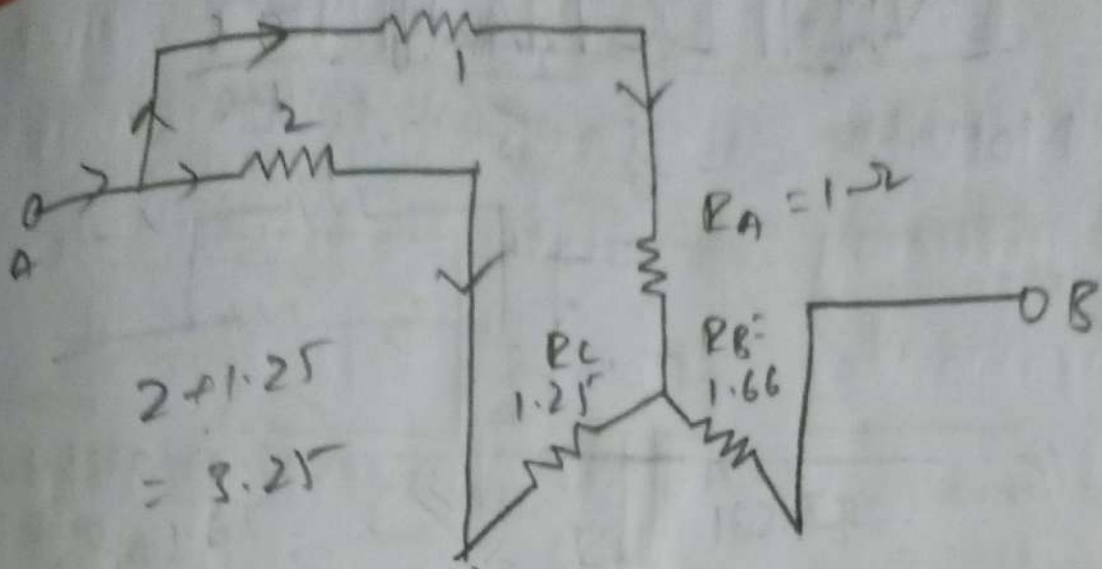
$$\frac{3 \times 4}{3 + 4} = \frac{12}{7}$$


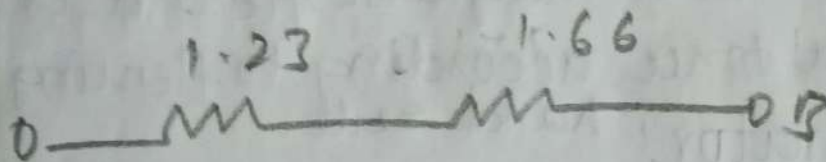
$$\frac{2 \times 3.25}{5.25} = \frac{6.5}{5.25} = 1.23 \Omega$$



$$R_{eq} = 2.89 \Omega$$

DC Machine

UNIT-II DC MACHINES

DC Motor:

Main field flux

Motor converts electrical energy to mechanical energy

commutator

DC motor it converts electrical energy into mechanical energy

Principle: when a current carrying conductor is placed in a magnetic field it experiences mechanical force according to Fleming's left hand rule


DC Generator:

(made up of cast steel laminations)
commutator
changes AC to DC


Brushes are made up of carbon material & collect current


$R \rightarrow$ variable resistance
 $V \leftarrow \rightarrow$

Nature of supply is DC itself

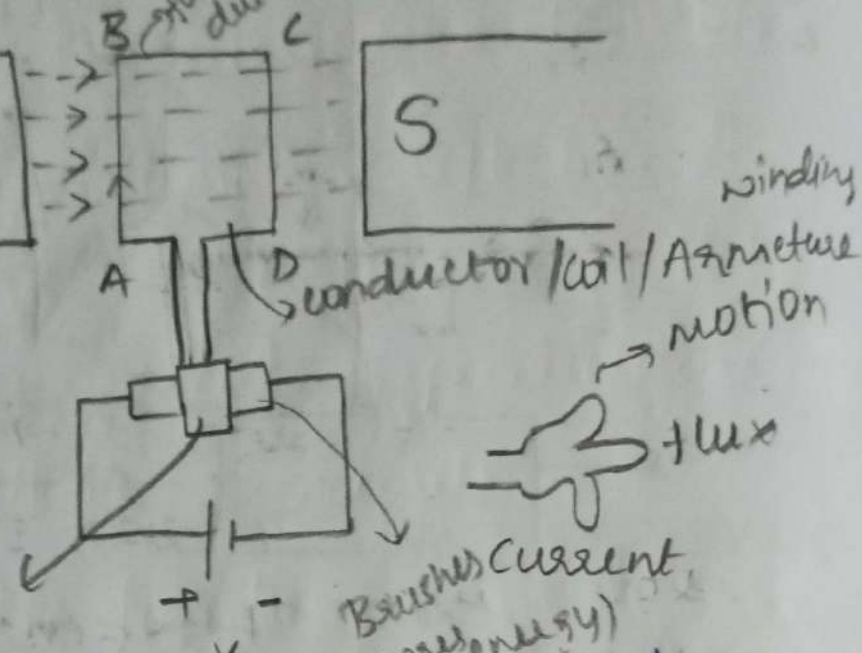

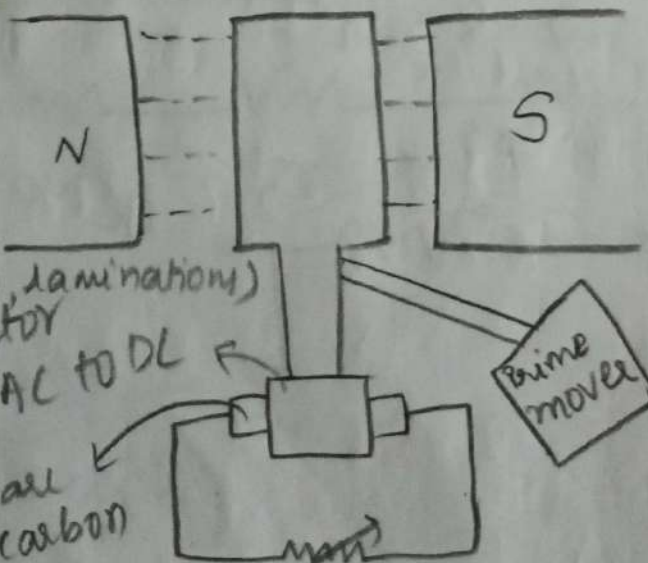(forefinger) flux
(thumb) motion
emf (middle)



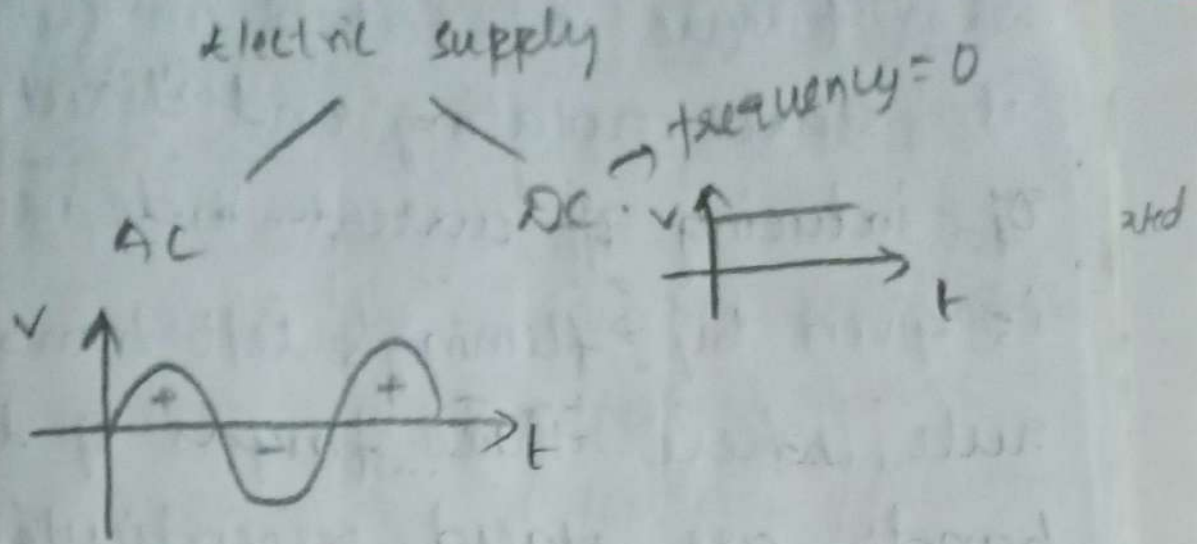

1 ϕ , 3 ϕ supplies will be there
 ↓ ↓ Indian standard
 240V, 415V frequency 50Hz
 50Hz 50Hz
 Vs standard
 frequency 60Hz

DC motor:

There are two fluxes produced in DC motor

- 1) Main field flux due to field winding
- 2) flux which is produced due to current flow in the conductor.

Due to interaction b/w these two fluxes there is a twisting or turning force produced which is nothing but torque.

When torque is exerted on the coil it starts rotating and direction of inducing of current in dc motor is given by Fleming's left hand rule where three fingers of left hand are placed perpendicular (90°) to each other & namely

thumb, forefinger, middle finger

Where

thumb - Represents motion of the conductor

forefinger - Indicates the direction of flux lines

middle finger - Represents direction of inducing of current in it

DC Generator:

Working principle of DC generator:

It is a rotating electrical machine

which works under the principle of electromagnetic induction here it is a two pole DC generator with a armature coil of ABCD sides placed in magnetic field which is rotating with external prime mover known as rotating conductor or coil. Whenever a rotating conductor cuts magnetic field there is a relative speed b/w flux and conductor according to Faraday's laws of electromagnetic induction, an emf gets induced in ABCD coil.

According to Fleming's right hand rule :

Fore finger - Indicates flux direction

Middle finger - Direction of induced emf

Thumb - Indicates motion of conductor.

Construction of DC generator

field winding

Repaired with
cast steel, cast iron

It is outermost
layer.
Gives mechanical
support to machine

Yoke

Protects flux
from escaping

Armature core

Pole

Armature winding

commutator brushes

Base


Pole & Armature
winding provide
required flux

Purpose of Pole is to hold the
field winding.

coil / conductor \Rightarrow Armature
winding

Armature core \Rightarrow to hold

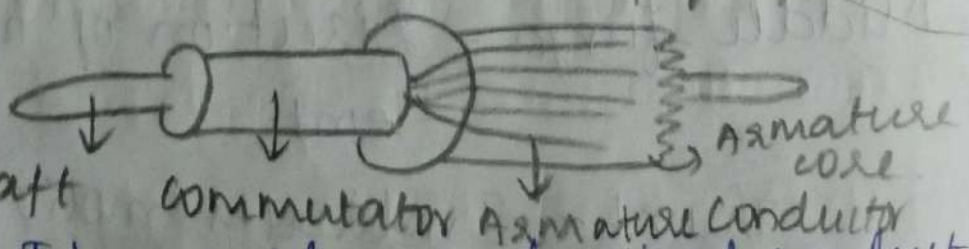Armature winding \Rightarrow made up of copper
Armature winding



Yoke: It provides mechanical support
to the entire machine made up

or cast iron or cast steel

Field Winding & Pole:

Pole is made up of high permeable material which holds field winding and also provides magnetic flux in the machine.

Field winding is made up of copper material which supports to develop magnetic flux.

Armature Core:

Armature core is a cylindrical drum shaped structure punched into slots on peripherals to hold armature winding made up of silicon laminated steel.

Commutator:


It is a mechanical rectifier used to convert pure AC to DC voltage. It is made up of ^{Hard drawn} copper.


Brushes: It is soft material.

They are made up of carbon and used to collect current from rotating

commutator.

Armature winding: Made up of copper.

① lap (It will be overlapped) 

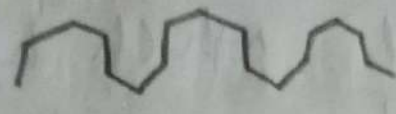② wave ($\uparrow V \downarrow I$) 

At high current and low voltage

At high voltage & low current

Armature Winding:

It is a distributed winding as per the requirement it is classified into two types ① lap winding

② wave winding.

It is a main winding of the machine which supports to produce EMF and torque.

★ ★ EMF eqⁿ of a DC generator:

According to Faraday law of EMF induction

$$E = N \frac{d\phi}{dt}$$

$$N = 1$$

N = no of turns

E = Induced EMF conductor per conductor

change in $\phi = d\phi = \phi \times P$

ϕ = flux

P = Poles (no of poles)

$$dt = \frac{60}{N}$$

change in time.

$$E = \frac{d\phi}{dt} = \frac{\phi \times P}{\frac{60}{N}}$$

$$E = \frac{N\phi P}{60} \times \left(\frac{1}{A} \times Z \right)$$

A = no of lld paths.

Z = no of conductors

ϕ = flux

N = speed.

P = poles.

$$E_g = \frac{\phi Z N P}{60 A}$$

$$E_g = \frac{\phi Z N P}{60 A}$$

E_g = EMF induced for 'Z' no of conductors.

A = no of parallel paths.

P = Poles.

Z = no of conductors.

N = Speed.

ϕ = flux.

Lap $A = P$ $\uparrow I \downarrow V$

$$\text{lap } E_g = \frac{\phi Z N P}{60 A} = \frac{\phi Z N}{60}$$

$$\text{lap } E_g = \frac{\phi Z N}{60}$$

wave $A = 2$ $\uparrow V \downarrow I$

$$\text{wave } E_g = \frac{\phi Z N P}{60 \times 2} = \frac{\phi Z N P}{120}$$

$$\text{wave } E_g = \frac{\phi Z N P}{120}$$

A four pole generator having wave wound armature winding has 51 slots each slot consisting of 20 conductors determine the generated EMF in the machine when driven at 1500 RPM if flux per pole is 7 milliwbebers.

flux units = milliwbebers
= mwb.

$P = 4$

$$\phi = 7 \text{ mwb} = 7 \times 10^{-3} = 0.007$$

$$P = 4$$

$$Z = 51 \times 20$$

$$A = 2$$

$$N = 1500$$

$$E_g = \frac{\phi Z N P}{60 A} = \frac{10^{-3} \times 7 \times 51 \times 20 \times 1500 \times 4}{60 \times 2}$$

$$= \frac{7 \times 51 \times 18 \times 4}{60}$$

$$E = 357 \text{ V}$$

Q) A 4 pole DC generator has a lap wound armature with 792 conductors if flux per pole is 0.0121 weber determine the speed at which it should run to generate 240V

$$E_g = \frac{\phi Z N P}{60 A}$$

$$P = 4$$

$$P = A$$

$$\phi = 0.0121$$

$$N = ?$$

$$240 = 0.0121 \times 792$$

$$E = V = 240$$

$$\times N \times$$

$$60$$

$$N = \frac{240 \times 60}{121 \times 792 \times 10^{-4}}$$

$$= \frac{24 \times 6 \times 10^6}{121 \times 792}$$

$$= \frac{144 \times 10^6}{95832} = 1502.6$$

$$95832 = 1502.6$$

1500 \rightarrow Rated RPM. if load is there there would be around 1400.

Q) A 6 pole DC generator have wave wound armature with 574 conductors and armature is rotating with a 1492 RPM determine flux per pole at which it should run to generate

220V

$A = 22$

$P = 6$
 $Z = 574$

$N = 1492$

$\phi = ?$

$E = 220V$

$$220 = \frac{6 \times 574 \times 1492 \times \phi}{60 \times 2}$$


$$\phi = \frac{220 \times 60 \times 2}{6 \times 574 \times 1492}$$

$$= \frac{26400}{5138448}$$


$$= 5.137 \times 10^{-3}$$

$$= 5.137 \text{ mweber}$$

Types of DC Generator

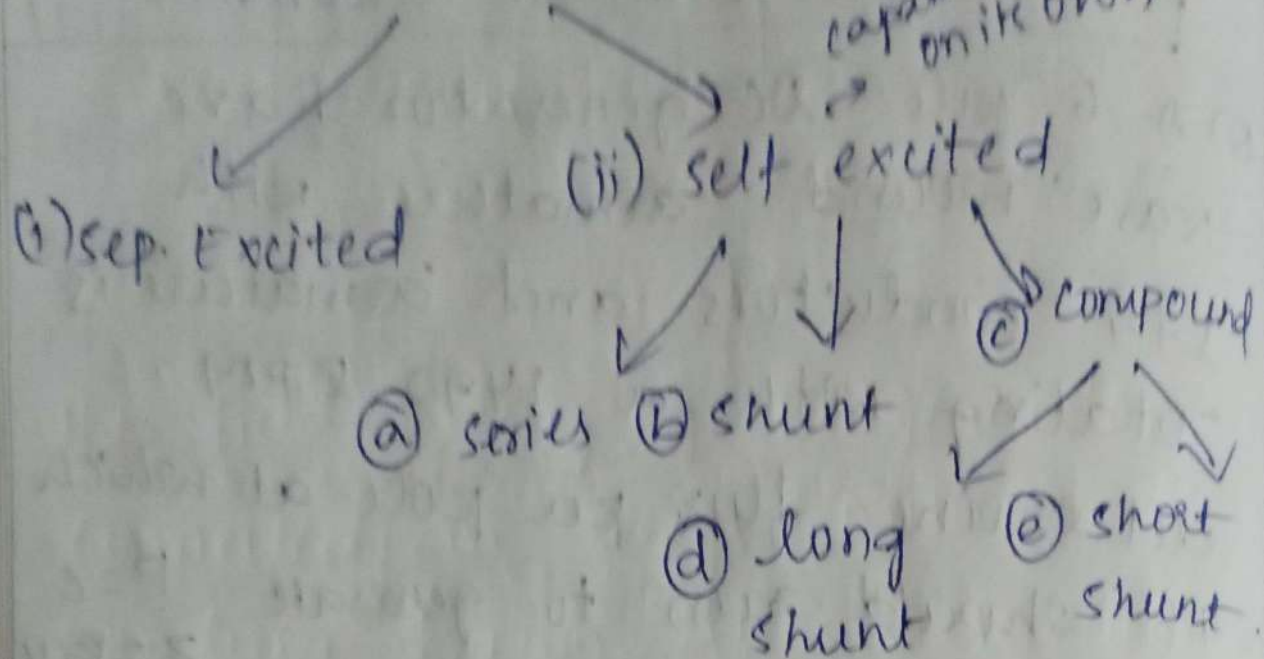

(1) Separately generated DC generators:

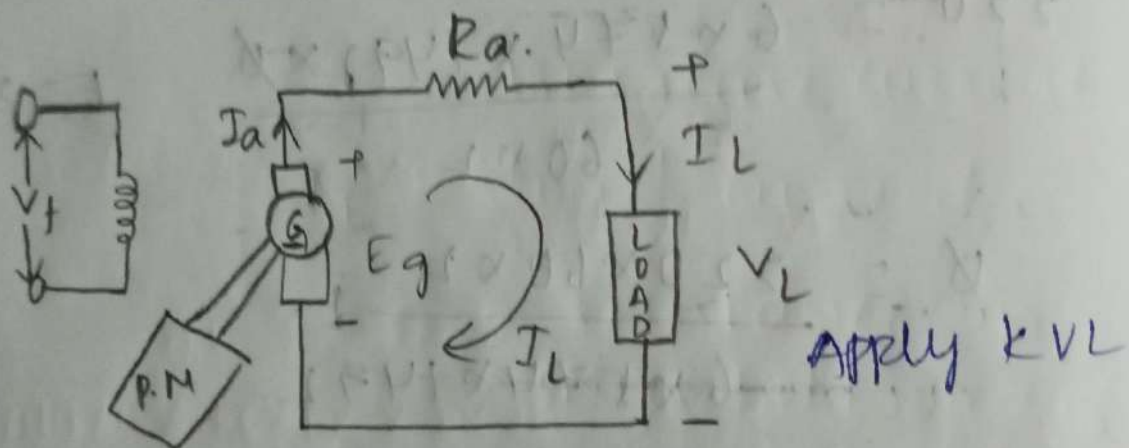

$$-E_g + I_a R_a + V_L + B.C.D = 0.$$

B.C.D = Brush contact drop.

In problem

If mentioned about BCD take that BCD value if not take

$B.C.D = 2V$ in problems.

$$E_g = I_a R_a + V_L + BCD$$

armature generated power.

$$P_g = E_g I_a$$

Power generated by load.


Power consumed.

$$P_L = I_L V_L$$

$$I_a = I_L$$

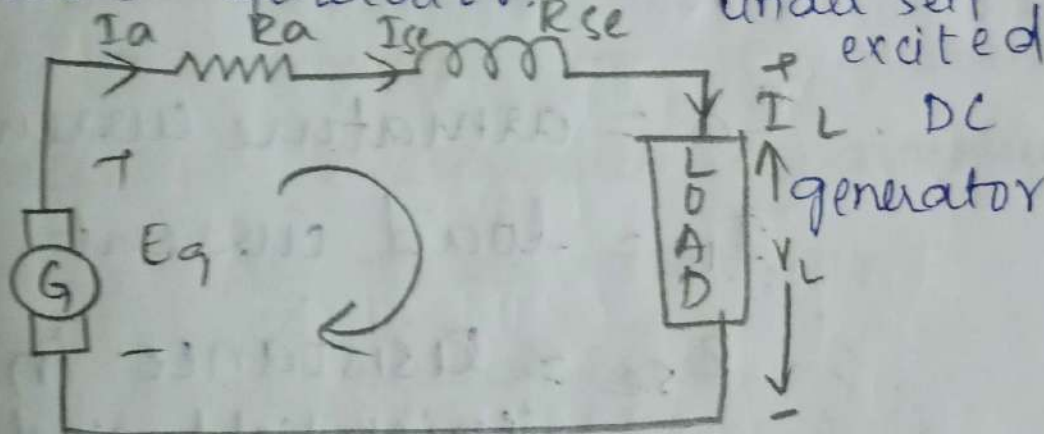(ii) Self Excited:

⊗ Series Generator: The field winding under self excited by



Apply KVL

$$-E_g + I_a R_a + I_{se} R_{se} + V_L + BCD = 0$$

$$E_g = I_a R_a + I_{se} R_{se} + V_L + BCD$$

$$P_g = E_g I_a$$

Power generated in armature.

$$P_L = V_L I_L$$

Power consumed by load.

The field winding of DC generator connected in series with armature winding known as series generator.

I_{se} = current in series field winding

I_a = armature current.

I_L = load current.

R_{se} = Resistance in series field winding.


R_a = armature resistance.

E_g = Generated voltage.

V_L = load voltage.

B_{CD} = Brush contact drop.

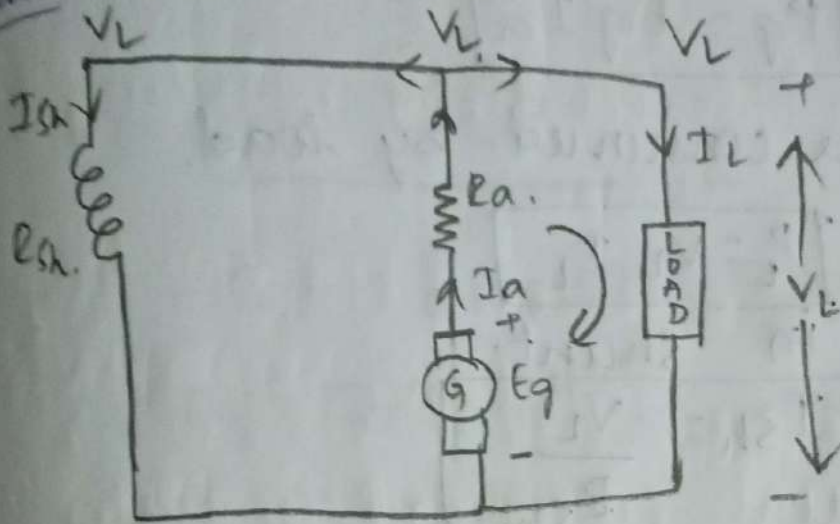separately Generated!
 need to separately provide
 electrical energy to the stator
 get working flux on armature
shunt Generator:



The field winding of the generator
 connected in parallel to armature
 known as shunt generator.

I_L = load current.

I_a = armature current.

E_g = generated EMF.

Applying
 ΣV_L
 $-E_g + I_a R_a$
 $+ V_L + I_{sh} R_{sh} = 0$

R_a = armature resistance.

R_{sh} = shunt field resistance.

V_L = load voltage or
 terminal voltage

I_{sh} = shunt current.

$E_g = I_a R_a + V_L + I_{sh} R_{sh}$

Armature current

$$I_a = I_L + I_{sh}$$

Power generated by armature

$$P_g = E_g I_a$$

Power consumed by load

$$P_L = V_L I_L$$

current in shunt

$$I_{sh} = \frac{V_L}{R_{sh}}$$

crane, weight lifting \rightarrow compound generator

train \rightarrow series generator \rightarrow to produce more torque


mills \rightarrow shunt generator \rightarrow for constant speed

we use field winding in these series & shunt for flux.

③ compound:

\rightarrow combination:

① long shunt compound generator:

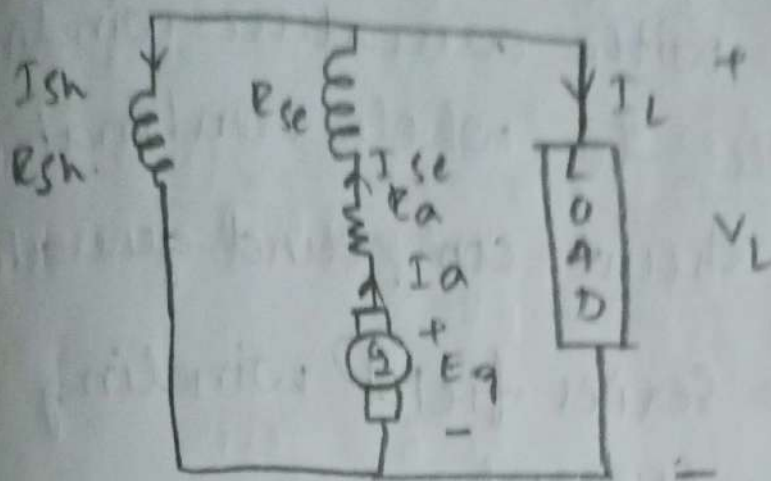

$$-E_g + I_a R_a + I_{se} R_{se} + V_L + R_{CD} = 0$$

$$E_g = I_a R_a + I_{se} R_{se} + V_L + R_{CD}$$

current through armature and shunt are same

$$I_a = I_{se}$$

current is getting divided in I_{sh} & I_L

$$I_a = I_{se} = I_{sh} + I_L$$

Emf

$$E_g = I_a R_a + I_{se} R_{se} + V_L + R_{CD}$$

$$E_g = I_a (R_a + R_{se}) + V_L + R_{CD}$$

Power generated by armature

$$P_g = V E_g I_a = E_g I_{se}$$

$$P_L = V_L I_L$$


long shunt! The field winding in series with armature winding and parallel to whole combination is long shunt compound generator.

I_{se} = series field winding current.

R_{se} = series field winding resistance.

Short shunt compound generator!


Application for short shunt

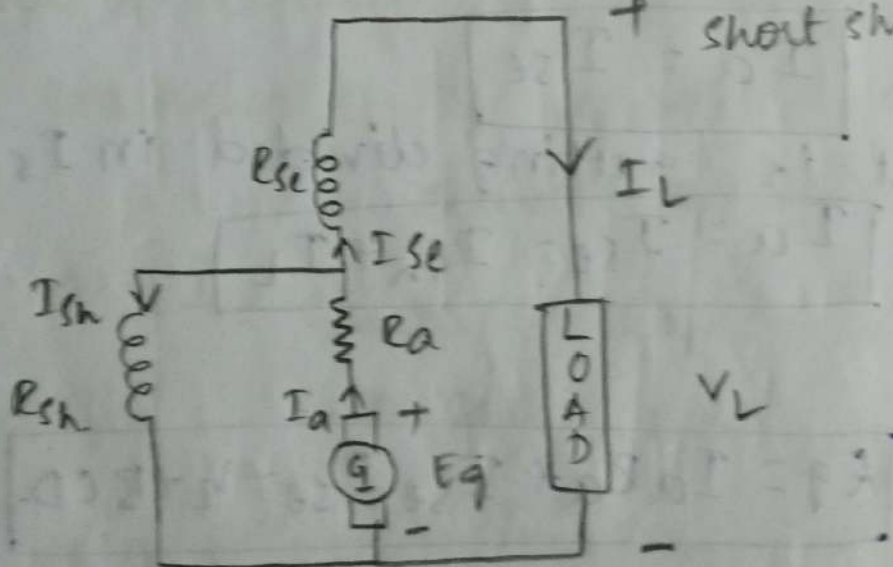

$$-E_g + I_a R_a + I_{se} R_{se} + V_L + R_{CD} = 0$$

$$I_{sh} R_{sh} = I_{se} R_{se} + V_L$$
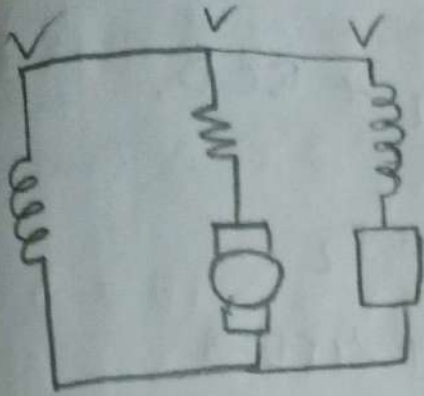
$$I_{sh} = \frac{I_{se} R_{se} + V_L}{R_{sh}}$$



$$I_a = I_{sh} + I_L$$

$$I_{se} = I_L$$

$$P_g = E_g I_g$$

$$P = V_L I_L$$

Q) A shunt generator delivers 450 A at 230 V the resistance of shunt field and armature resistance are 50Ω and 0.03Ω respectively calculate the generated emf.

~~$$I_L \quad I_{sh} = 450 \text{ A.}$$~~

~~$$I = 450 \text{ A}$$~~

~~$$V_{sh} = 230 \text{ V}$$~~

~~$$R_a = 50 \Omega$$~~

~~$$R_{sh} = 50 \Omega$$~~

~~$$R_a = 0.03 \Omega$$~~

~~$$V_{sh}$$~~

$$I_L = 450 \text{ A, } V_L = 230 \text{ V}$$

$$R_{sh} = 50 \Omega \quad R_a = 0.03 \Omega$$

$$E_g = I_a R_a + V_L + BCD.$$

$$I_a = I_{sh} + I_L$$


$$= \frac{230}{50} + 450 \text{ A}$$

$$= 4.6 + 450.$$

$$= 454.6.$$

$$E_g = (454.6)(0.03) + 230 + 2$$

$$= 245.638 \text{ V} //$$

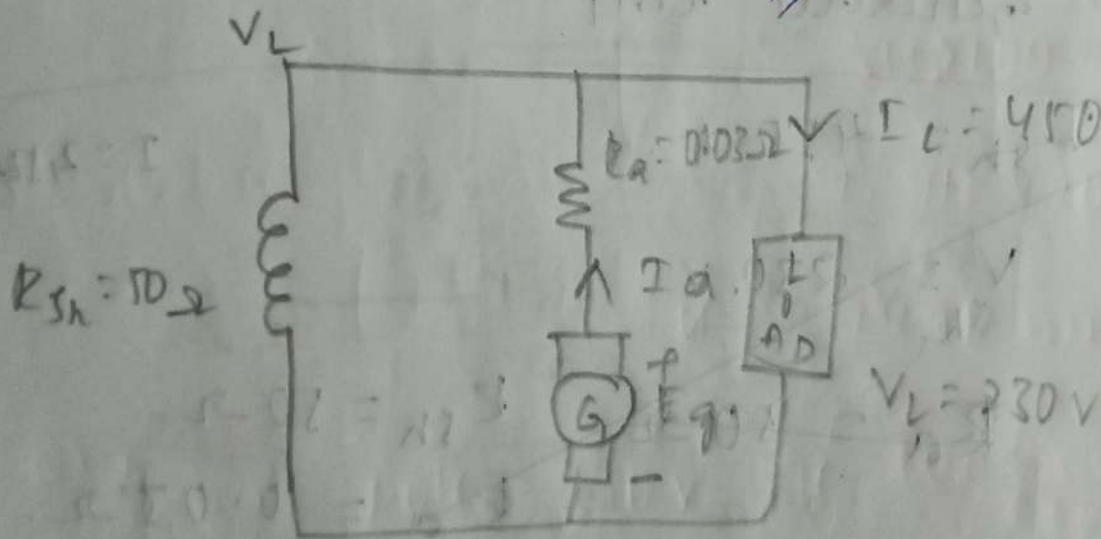

Q) A 8V 8 pole DC generator with 778 wave connected armature running at 500 RPM supplies a load of 12.5Ω resistance. $P=8$, $N=500$, $A=2$

$R_L = 12.5$ Terminal Voltage is 250V
calculate

- 1) Armature current
- 2) Generated EMF
- 3) Flux per pole

Assume armature resistance is
 0.24Ω and shunt field resistance
is 250Ω .

Armature current.

$$I_a = I_{sh} + I_L$$

$$I_a = \frac{V_L}{R_a}$$

$$= \frac{250}{0.24} + \frac{250}{12.5}$$

$$= 1041$$

$$I = 213$$

$$I_L = \frac{V_L}{R_L} = \frac{250}{12.5} = 20A$$

$$I_{sh} = \frac{V}{R_{sh}} = \frac{250}{250} = 1A$$

$$R_{sh} = 250 \Omega$$

$$V_L R_{sh} = 250$$

$$R_a = 0.24 \Omega$$

$$Z = 778$$

$$\frac{V_L}{R_{sh}}$$

$$R_{sh}$$

$$I_a = 21 \text{ A}$$

$$E_g = I_a R_a + V_L + BCD$$

$$= (21)(0.24) + 250 + 2$$

$$E_g = 257.04 \text{ V}$$

$$\phi = \frac{E = \phi Z N P}{60 A}$$

$$257.04 = \frac{\phi \times 7.78 \times 8 \times 500}{120}$$

$$\phi = \frac{30844.8}{3112000}$$

$$= 9.911 \times 10^{-3}$$

$$\phi = 9.91 \text{ mwb.}$$

Q) A 4 pole 250 V DC long shunt compound generator supplies a load of 10 kW at the rated voltage. The armature, series ~~field~~ field and shunt field

resistances are 0.1, 0.15, 250 Ω respectively the armature is lap connected

$$P = 4$$

$$N = ?$$

$$P_2 = 10 \text{ kW}$$

$$\phi = 50 \text{ mwb}$$

$$A = P$$

$$Z = 50 \times 6$$

with 10 slots each slot containing 6 conductors if the flux per pole is 50 mwb. calculate N .

$$R_a = 0.1 \Omega$$

$$V_L = 250 \text{ V}$$

$$R_{se} = 0.15 \Omega$$

$$R_{sh} = 250 \Omega$$

$$E = \frac{\phi Z N P}{60 A}$$

$$E = I_a R_a + I_{se} R_{se} + V_L + RCD$$

$$I_a = \frac{250}{0.1} = 2500 \text{ A}$$

$$I_{se} = \frac{V_L}{R_{se}} = \frac{250}{0.15} = 1666.66$$

$$R_g = \frac{V_{ZNA}}{60A}$$

$$E_g = I_a R_a + I_{se} R_{se} + V_L + RCD$$

$$I_a = I_{se}$$

$$= I_a (R_a + R_{se}) + V_L + RCD$$

$$\text{3 } P_L = 10kW = V_L I_L$$

$$I_L = \frac{P_L}{V_L} = \frac{10 \times 10^3}{250} = 40A$$

$$I_{sn} = \frac{V}{R_{sn}} = \frac{250}{250} = 1A$$

$$I_a = I_{se} = I_{sh} + I_L$$

$$I_a = 1 + 410 = 411 \text{ A}$$

$$E_g = 411(0.1 + 0.15) \times 250 + 2$$


$$= 262.25 \text{ V}$$

$$262 = \frac{50 \times 10^{-3} \times 300 \times N \times \cancel{\pi}}{60 \times \cancel{\pi}}$$

$$N = 10498 \text{ rpm} //$$

Torque eqⁿ of a DC motor:

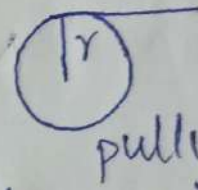Torque is defined as twisting / turning force or of movement



or force and it is given by product of force and radius.

Let us consider a pulley of radius r acted upon circumference by a force newton's which causes it to rotate at ' N ' rpm

$$T = F \times r \quad (\because P = \frac{W}{t})$$

$$W = F \times D$$

where $D =$ Distance travelled in 1 revolution.

Work done to complete 1 revolution

$$W = F \times D$$

$$= F \times 2\pi r$$

time taken complete 1 revolution

$$N - \text{rpm.}$$

$$N \text{ rev} - 60 \text{ sec.}$$

$$\text{rev} - ? \Rightarrow \frac{60}{N}$$

$$t = \frac{60}{N}$$

$$P = \frac{W}{t} = \frac{F \times D}{\frac{60}{N}}$$

$$P = \frac{F \times 2\pi r}{60/N}$$

$$= \frac{F \times Y \times 2\pi N}{60}$$

$$\boxed{P = T \times \omega}$$

$$\omega = \frac{2\pi N}{60} \Rightarrow \text{Angular velocity.}$$

$$P = E_b \times I_a$$

$$E_b I_a = T \times \omega$$

$$E_b = \frac{T \times \omega}{I_a}$$

$$\frac{\cancel{\phi} \times \cancel{2\pi} P}{\cancel{60} A} = \frac{T_a \times \cancel{2\pi} \cancel{N}}{\cancel{60} I_a}$$

$$\boxed{T_a = \frac{\phi \times P \times I_a}{2\pi \times A}}$$

N-m.

units of torque are 'N-m'.

where ϕ = flux

z = speed

P = pole

I_a = armature current

A = No of 11el paths.

Q) calculate the value of Torque established by the armature of a 4 pole motor having 774 conductors. 2 paths in 11el 24 mwb flux per pole when I_a is 50 A.

$$P = 4 \quad z = 774$$

$$A = 2 \quad \phi = 24 \text{ mwb}$$

$$I_a = 50 \text{ A.}$$

$$T_a = \frac{4 \times 24 \times 774 \times 50 \times 10^{-3}}{2 \times 3.14 \times 2.}$$

$$= \frac{4 \times 9288 \times 10^{-1}}{12.56} = 295.718 \text{ N.m.}$$

8) Determine the value of T in N-m developed by armature of 6 pole wave wound motor having 492 conductors and has an armature current of 40 A find out E_g ?

$$P = 6$$

$$A = 2$$

$$Z = 492$$

$$\phi = 30 \times 10^{-3} \quad I_a = 40$$

$$E_g = \frac{\phi \times 30 \times 10^{-3} \times 40 \times 492}{\frac{60 \times 2}{10}}$$

$$= \frac{3542.4}{60 \times 2}$$

$$= \frac{15 \times 492 \times 10^{-2}}{20}$$

$$= 15 \times 492 \times 10^{-2}$$

$$= 282.0392$$

Q) A 250V dc motor runs at 1500 rpm and takes I_a of 10 A. back emf of dc motor is 240V. Obtain Torque developed in motor.

$$V_L = 250$$

$$N = 1500 \text{ rpm}$$

$$I_a = 10 \text{ A}$$

$$E_b = 240 \text{ V}$$

$$E_g = \frac{\phi Z N P}{60 A}$$

$$E_b = \frac{T \times W}{I_a}$$

$$W = \frac{2\pi N}{60}$$

$$\frac{9420}{60}$$

$$W = 157$$

$$240 = \frac{157 \times T}{10}$$

$$\frac{12000}{157} = T$$

$$T = 76.433 \text{ N-m}$$

Q) A 250 V 4 pole wave wound dc series generator delivers a current of 180 A. take $R_a = 0.75 \Omega$ and $R_{se} = 0.15 \Omega$ calculate EMF generated & $P = 4$ $A = 2$ I_a of generator.

$$I_a = 180 \quad R_a = 0.75 \Omega$$

$$R_{se} = 0.15 \Omega$$

$$E_g = 250 \text{ V}$$

$$V_L = 250 \text{ V}$$

$$I_a = I_{se} = I_L \quad I_a = \frac{E_g}{R_a}$$

$$E_g = I_a R_a + I_{se} R_{se} + V_L + B.C.D. = \frac{250}{0.75}$$


$$= (180)(0.75) +$$

$$(180)(0.15) + 250 + 2$$


$$= 135 + 27 + 252$$

$$= 414 \text{ V}$$

Types of DC Motors:

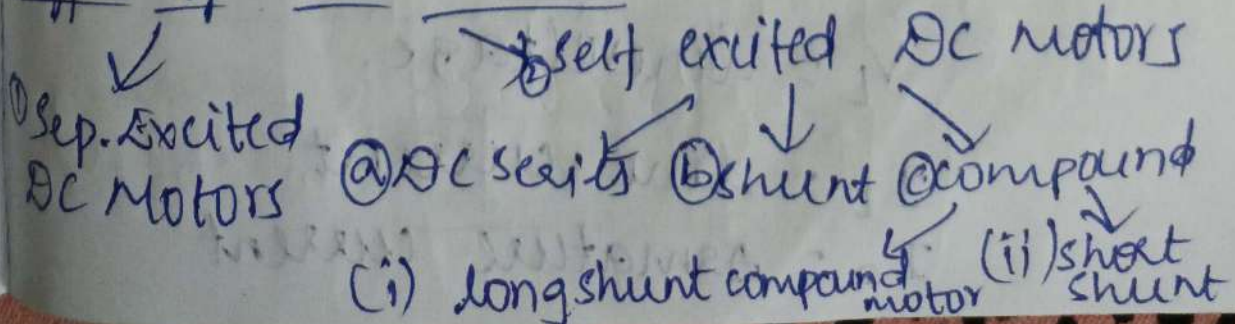

① Separately excited DC motor:

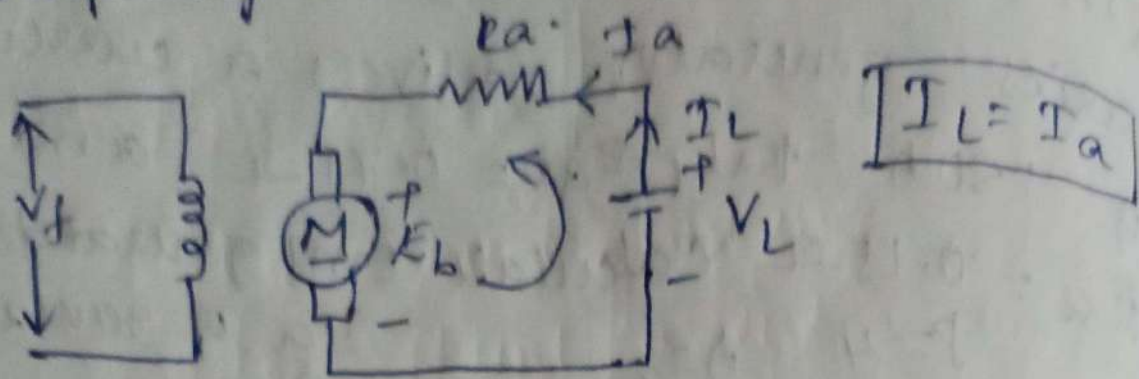

Applying KVL

$$-V + I_a R_a + E_b = 0.$$

$$E_b = V - I_a R_a \quad \text{BCD}$$

Power generated across source.

$$P_s = V_L I_L$$

Mechanical

Power generated by motor/armature

$$P_m = E_b I_a$$

→ whenever excitation to the field winding is provided by some external source is called separately excited DC motor.

V_L = line voltage.

I_L = line current

I_a = armature current

R_a = armature resistance

V_f = field excitation.


P_s = source power.

E_b = back emf.

P_m = Mechanical power generated by armature.

2) self-Excited DC motors:

a) DC series motor:

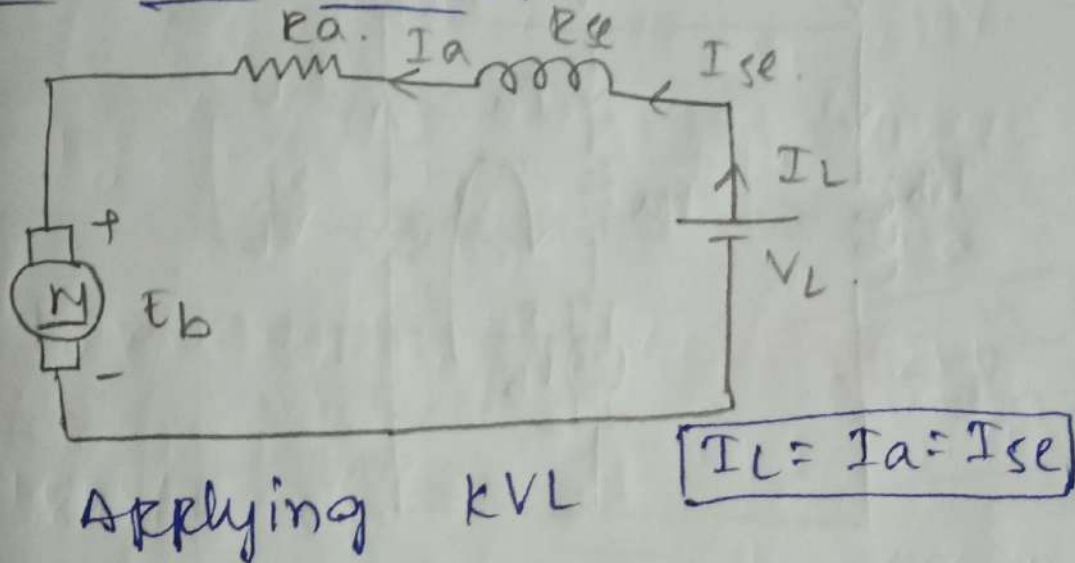

$$-V_L + I_{se} R_{se} + I_a R_a + E_b = 0$$

$$V_L = I_{se} R_{se} + I_a R_a + E_b + BCD$$

$$-V_L + I_a (R_a + R_{se}) + E_b = 0$$

$$E_b = V - I_a (R_a + R_{se}) + BCD$$

source power

$$P_s = V_L I_L$$


Mechanical power generated

$$P_m = E_b I_a$$

R_{se} = shunt resistance

I_{se} = shunt current

b) DC shunt motor

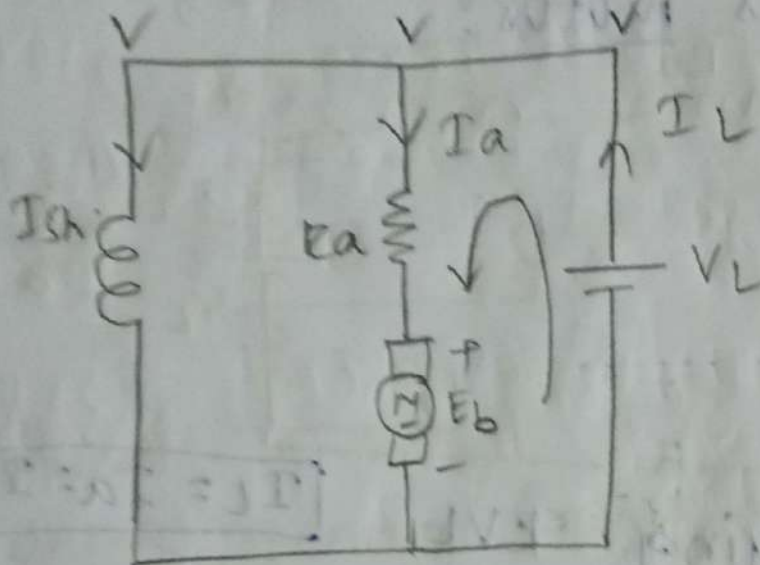

Applying KVL

$$-V + I_a R_a + E_b = 0$$

$$E_b = V - I_a R_a$$

$$I_{sh} = \frac{V}{R_{sh}}$$

$$I_L = I_a + I_{sh}$$

$$P_s = V_L I_L$$

$$P_m = E_b I_a$$

DC series motor:


Whenever the field winding is connected in series with armature is called DC series motor.

DC shunt motor:

Whenever the field winding is connected in parallel with armature is called DC shunt motor.

② Compound motors:

long shunt compound motor:

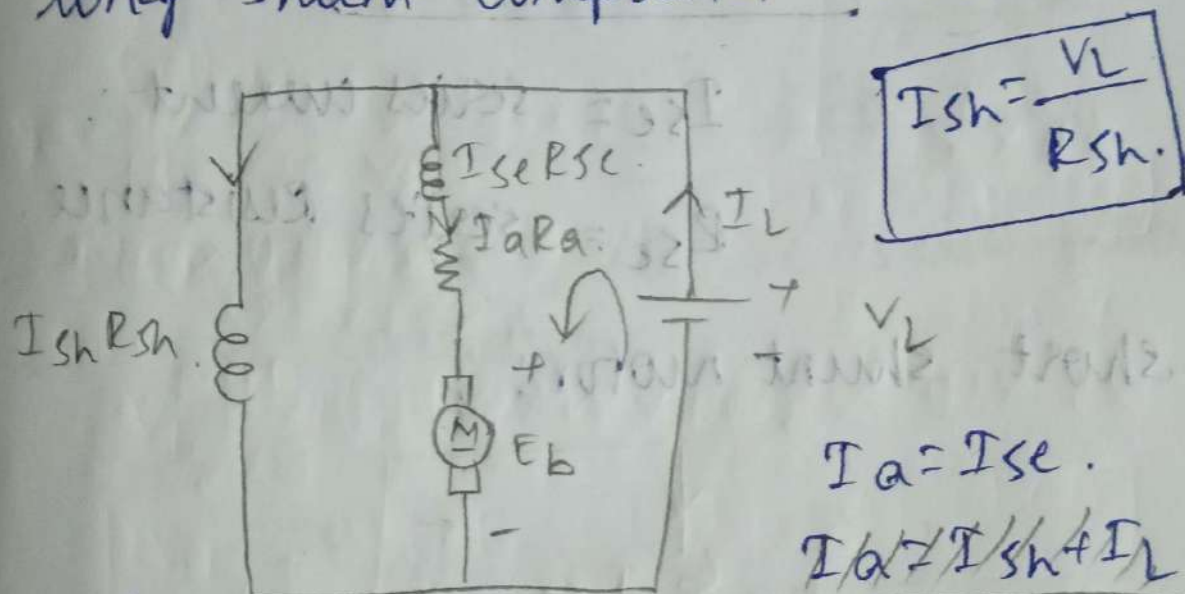

$$I_{sh} = \frac{V_L}{R_{sh}}$$

$$I_a = I_{se}$$

$$I_L = I_{sh} + I_a$$

$$I_L = I_{se} + I_{sh}$$

Applying KVL

$$-V_L + I_{se} R_{se} + I_a R_a + E_b = 0$$

$$V_L = I_{se} R_{se} + I_a R_a + E_b$$

$$E_b = V_L - I_{se} R_{se} - I_a R_a$$

$$E_b = V_L - I_a (R_{se} + R_a) - BCD$$

Power in motor

$$P_m = E_b I_L$$

Power across source

$$P_s = V_L I_L$$

$$I_{sh} = \frac{V}{R_{sh}}$$


$$I_L = I_{se} + I_{sh}$$

$$\frac{V}{R_{se}} = I_{se}$$

I_{se} = series current.

R_{se} = series resistance.

short shunt motor:

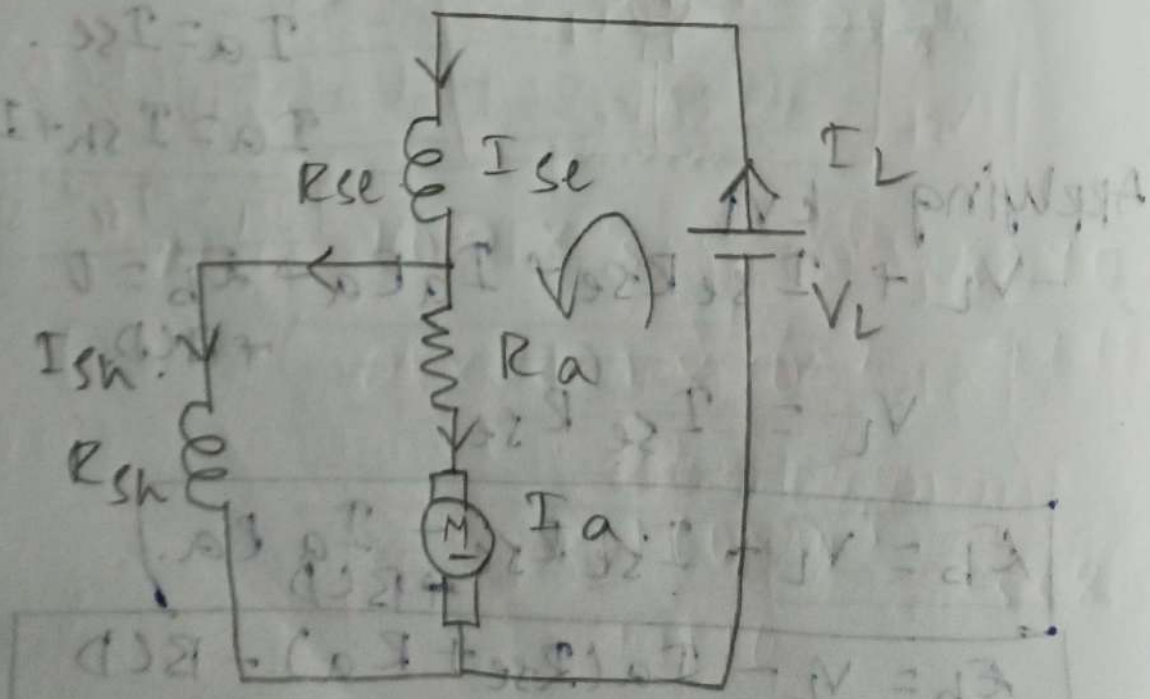

$$-V_L + I_{se} R_{se} + I_a R_a + BCD = 0.$$

$$+ E_b$$

$$E_b = V_L - I_{se} R_{se} - I_a R_a - E_b - BCD.$$

$$I_L = I_{se}$$

$$I_L = I_{se} = I_{sh} + I_a$$

$$V_L I_L + I_{se} R_{se} = I_{sh} R_{sh}.$$

$$I_{sh} = \frac{I_{se} R_{se} + V_L}{R_{sh}}.$$

Q) A ^{sc}_x 6 pole shunt motor has wave connected armature with 87 slots, each slot containing 6 conductors. The $\phi = 30 \text{ mwb}$. The armature has resistance $= 0.10 \Omega$. Calculate N , when motor is connected to 250V supply & taking $I_a = 80 \text{ A}$.

$$P = 6, A = 2$$

taking $I_a = 80 \text{ A}$

$$Z = 87 \times 6$$

$$\phi = 30 \text{ mwb} = 30 \times 10^{-3}$$

$$R_a = 0.10 \Omega$$

$$V_L = 250 \text{ V}$$

$$I_a = 80 \text{ A}$$

$$\frac{I}{S_n} = \frac{V}{R_{S_n}}$$

$$E_b = V - I_a R_a + BLD$$

$$= 250 - 80 \times 0.10 + 2$$

$$= 250 - 8 + 2$$

$$= 250 - 10 = 240.$$

$$I_L = I_a + I_{sh}$$

$$P_s = V_L I_L$$

$$P_m =$$

$$E_b = \frac{\phi Z N P}{60 A}$$

$$240 = \frac{30 \times 10^{-3} \times 87 \times 6 \times N \times 6}{60 \times 2}$$

$$\frac{240 \times 120}{3 \times 87 \times 6 \times 6 \times 10^{-2}} = N$$

$$\frac{24 \times 12}{3 \times 36 \times 87} = \frac{288}{9396} = N = 0.03065$$

$$= 306.5$$

Q) A 4 pole DC shunt motor has $\phi = 0.04 \text{ Wb}$ & Armature is lap wound with 720 conductors

$$P = 4, \phi = 0.04 \text{ Wb}, A = P$$

$$Z = 720$$

shunt field resistance is 240Ω &
 $R_a = 0.2 \Omega$ & BCD is $2V$ per
 $R_{sh} = 240 \Omega$

brush. Determine drop the N of
machine running as motor at

$60 A$.

$$BCD = 2 \times 1$$

$$P = 4.$$

$$= 2V.$$

$$I_L = 60A.$$

$$E_b = V - I_a R_a - BCD \quad V_L = 240V.$$

$$E_b = 240 - (I_a)(0.2) - 2.$$

$$I_L = I_a + I_{sh} \quad I_{sh} = \frac{V}{R_{sh}}$$

$$60 = I_a + I_{sh}.$$

$$= \frac{240}{240}.$$

$$60 = I_a + 1.$$

$$= 1$$

$$I_a = 59.$$

$$E_b = 240 - (59)(0.2) - 2.$$

$$E_b = 226.2$$


$$\frac{226.2 \text{ W}}{0.04 \times 720 \times} = E_b \quad \frac{0.2 \text{ V}}{60 \text{ A}}$$

$$\frac{226.2 \times 60}{0.04 \times 720 \times} = N$$

$$\frac{13572}{28.8} = N$$

$$N = 471.25 \text{ rpm.}$$

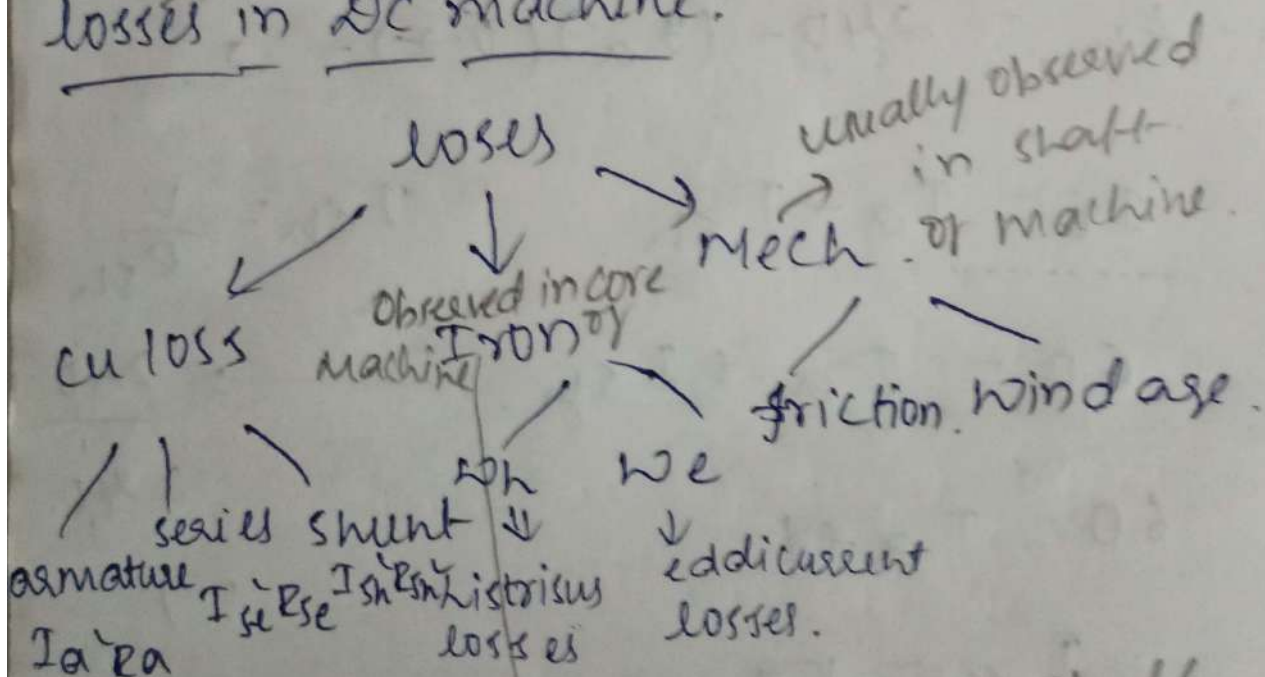Power lost in the form of heat.
losses in DC machine!




for mechanical energy we use shaft.

depends on materials used
 $B_m \Rightarrow$ max. flux density $\eta_h \Rightarrow$ hysteresis coefficient

To reduce we use laminated core

t = thickness of each lamination

(i) cu losses:

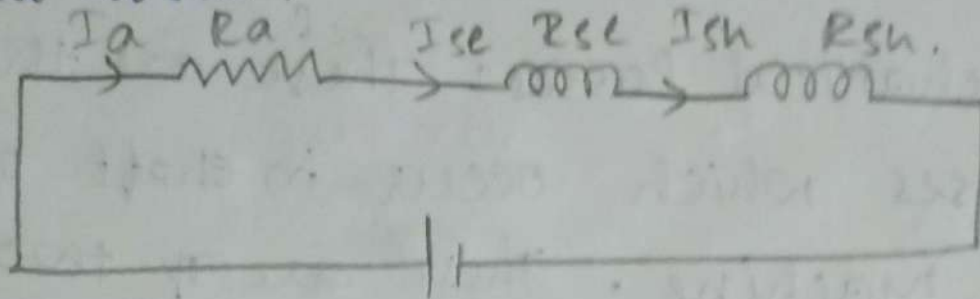

$$\text{cu losses} = I_a^2 R_a + I_{se}^2 R_{se} + I_{sh}^2 R_{sh}$$

load will be connected to shaft.

It will be coupled directly.

(ii) iron losses: η_e = eddy current coefficient.

$$\text{hysteresis}(W_h) = \eta_h B_m^{1.6} f v$$

$$\text{eddy losses}(W_e) = \eta_e B_{\max}^2 f^2 t^2 + L$$

η_h = hysteresis coefficient.

$B_m^{1.6}$ = maximum flux density.

f = frequency.

v = volume of core.

t = thickness of lamination

losses
↳ to minimise the eddy current

η_e = eddy current co-efficients.

B_{max} = Maximum flux density.

f = frequency.

t = thickness.

Mechanical losses: These are the losses which occur in shaft of DC machine. These are of two types.

1) friction loss.

2) windage loss.

Copper losses: Power wasted in the form of I^2R and these type of losses occur in dc winding of the machine are called copper losses. These are of three types.

Efficiency (η)

1) armature

2) series

3) shunt.

Efficiency (η): The ratio of output power and input power is known as

efficiency. It is denoted by η

$$\eta = \frac{\text{output power}}{\text{input power.}}$$

$$\eta = \frac{P_o}{P_i}$$
$$= \frac{P_o}{P_o + \text{losses}}$$

$$\therefore \eta = \frac{P_o}{P_o + \text{losses}} \times 100.$$

Q) A 230V shunt motor delivers 30 HP at the shaft at 1120 RPM if the motor has efficiency of 87% at this load determine

i) Total input power

ii) line current. (I_L)

$$V_L = 230V.$$

$$N = 1120 \text{ RPM.}$$

$$\eta = 87\%.$$

$$P_{out} = 30 \text{ HP.}$$
$$= 30 \times 746$$

$$\eta = \frac{P_o}{P_i} \times 100$$

$$87 = \frac{30 \times 746}{P_i} \times 100$$

$$P_i = \frac{30 \times 746}{87} \times 100$$

$$P_i = 25724.137$$

$$= 25724$$

$$I_L = \frac{V_L}{P_i}$$

$$= \frac{230}{25724}$$

$$P_i = I_L V_L$$

$$I_L = \frac{P_i}{V_L}$$

$$= \frac{25724}{230} = 111.843A$$

Q) A shunt generator delivers 195 A at a terminal voltage of 250 V. The armature & sh. R are 0.02Ω , 50Ω respectively. The iron & friction losses = 950 W. Find 1) E.M.F generated.

2) Cu losses.

3) Output of generator.

4) η .

$$I_L = 195 \text{ A}$$

$$V_L = 250 \text{ V}$$

$$R_a = 0.02 \Omega$$

$$R_{sh} = 50 \Omega$$

$$\eta_m = 1.6 \text{ B.m.f.v}$$

$$W_{cu} = ?$$

$$E_{mf} =$$

$$I_a = 195 + 5$$

$$= 200$$

friction so take it as mechanical 1095.

$$W_i \& W_f$$

$$W_m = 950 \text{ W}$$

$$I_a = I_L + I_{sh}$$

$$I_{sh} = \frac{V_L}{R_{sh}}$$

$$= \frac{250}{50}$$

$$= 5$$

$$P_{emf} = I_a R_a + V_L + BCD.$$

$$= (200)(0.02) + 250 + 2.$$

$$= 4 + 252$$

$$= 256.$$

$$P_{cu} = I_a R_a + I_{sh} R_{sh}.$$

$$= (200)(200)(0.02) + (5)(5)(50)$$

$$= (200)(4) + (25)(50)$$

$$= 800 + 1250$$

$$= 2050 \text{ W.}$$

$$\eta = \frac{P_o}{P_i}$$

$$950 + 2050.$$

$$= \frac{P_o}{P_o + \text{loss.}}$$

$$= \frac{48750}{48750 + 300}$$

$$P_o = V_L I_L$$

$$= (250)(200)$$

$$= 500$$

$$= (250)(195)$$

$$= 48750.$$

$$\times 100 = 94.2\%$$

$$18750$$

$$51750.$$

$$\eta = \frac{P_o}{P_o + \text{losses}}$$

$$\begin{aligned} \text{losses} &= W_{cu} + W_i + W_m \\ &= 950 + 2050 \\ &= 3000 \end{aligned}$$

~~W_i~~

8) A long shunt compound generator, gives 240V at full load output. of 100 A amp resistance of ~~100 Ω~~ . The resistance of various windings of the machine are $R_a = 0.1 \Omega$, $R_{se} = 0.02 \Omega$, $R_{sh} = 100 \Omega$. The iron loss on full load is 1000W. Windage & friction losses 500W. Calculate full load efficiency of the machine.

$$\begin{array}{l|l} V_L = 240V & R_a = 0.1 \Omega \\ I_L = 100 A & R_{se} = 0.02 \Omega \\ W_i = 1000W & R_{sh} = 100 \Omega \end{array}$$

$$\eta = \frac{P_o}{P_i + \text{losses}}$$

$$I_a = I_{se} = I_{sh} + I_L$$

$$E_g = I_a R_a + I_{se} R_{se} + V_L + E_L R_{cd}$$

$$P_o = V_L \times I_L$$

$$P_o = (100)(240)$$

$$= 24000$$

$$I_a = I_{sh} + I_L$$

$$= 2.4 + 100$$

$$= 102.4$$

$$I_{sh} = \frac{V}{R_{sh}}$$

$$= \frac{240}{100}$$

$$= 2.4$$

$$E_g = 102.4(0.1 + 0.02) + 240$$

$$= (102.4)(0.12) + 242$$

$$= 12.288 + 242$$

$$= 254.288$$

$$P_{cu} = (I_a^2 R_a) + I_{sc}^2 R_{se} + I_{sn}^2 R_{sn}$$

$$= (102.4)(102.4)(0.1) + (102.4) \text{ kA}^2$$

$$(102.4)(0.02) +$$

$$(2.4)(2.4)(100)$$

$$= 1048.57 + 213 + 576$$

$$= 1837.57$$

$$\text{losses} = 1837.57 + 1000 + 500$$

$$= 3337.57$$

$$\eta = \frac{24000}{240000 + 3337.57} \times 100$$

$$= \frac{24000}{27337} \times 100$$

$$= 87.79$$

$$= 87.8$$

UNIT-III


AC MACHINES

Construction of Transformers:-


static machine.

Magnetically coupled

Electrically isolated

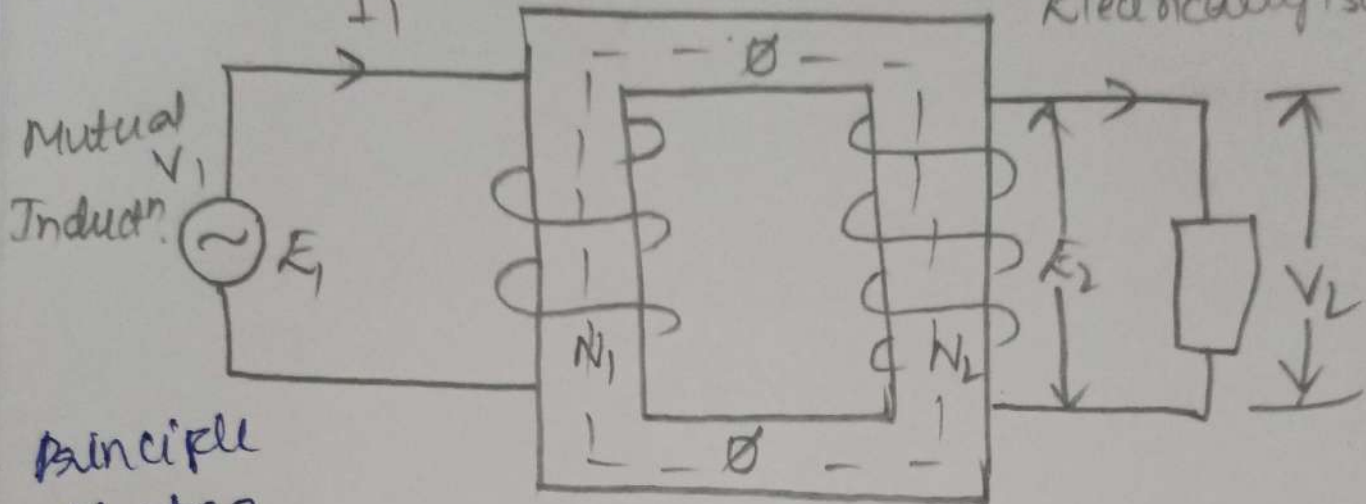

Principle Electro

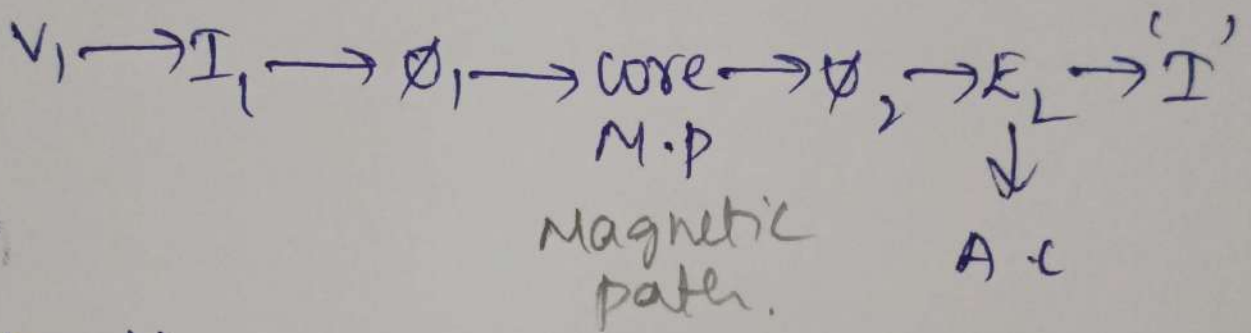

classification:

construction

windings

phase

1. Core

1. step Up

1. 1 ϕ

2. Shell

2. step down

2. 3 ϕ

3. Berry

Principle: Faraday's laws of electromagnetic induction,
mutual induction b/w 2 coils:

Working principle of transformer:

The basic principle behind working of transformer is mutual induction b/w two windings linked by common magnetic flux. Basically

a transformer consists of two inductive coils


primary & secondary these are electrically separated but magnetically coupled when

primary winding is connected to source of alternating voltage (AC), Alternating magnetic flux is produced around the winding.

The core provides magnetic path for the flux to get link with the secondary winding. Most of the flux gets linked with secondary is called useful flux or main flux. & the flux which doesnot link with secondary winding is called leakage flux. The flux which is produced is alternating in nature.

Emf gets induced in the secondary winding according to faraday's laws of electro magnetic inductⁿ. This emf is called mutually induced Emf & this frequency is same as supply emf. If the secondary winding is closed then mutually induced current flows through it & hence electrical energy is transferred from 1 circuit (primary) to another circuit (secondary)

Emf eqⁿ of a transformer:

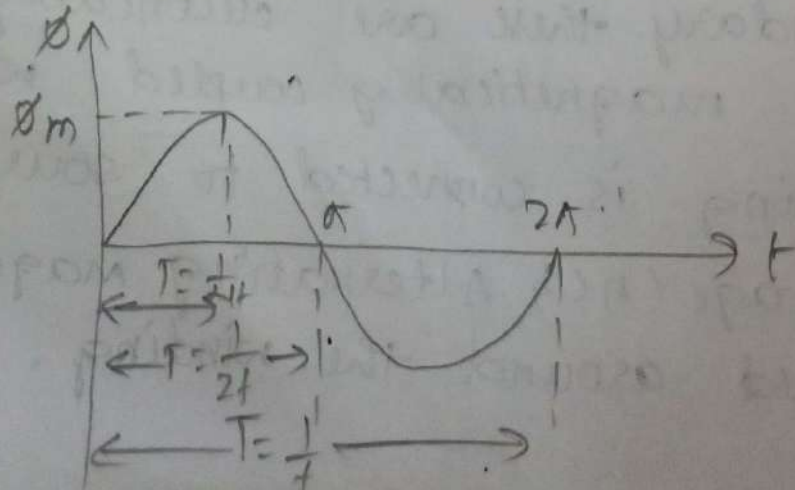

According to faraday's laws of electromagnetic induction:

$$\boxed{E = N \frac{d\phi}{dt}}$$

$N = \text{no of turns}$

$$N = 1$$

$$E = \frac{d\phi}{dt}$$

change in flux

$$d\phi = \phi_m - 0$$

$$dt = \frac{1}{4f}$$

$$E = \frac{\phi_m}{\frac{1}{4f}}$$

$$E = 4f\phi_m$$

$$\text{form factor} = \frac{\text{Rms value}}{\text{avg value}}$$

$$\text{form factor} = 1.11 (\sin)$$

$$E = 4f\phi_m \times 1.1$$

$$= 4.4f\phi_m$$

E_{mf} induced in primary winding

$$\boxed{E_1 = 4.44f\phi_m N_1}$$

E_{mf} induced in secondary winding

$$\boxed{E_2 = 4.44f\phi_m N_2}$$

turns ratio

$$k = \frac{N_2}{N_1} = \frac{E_2}{E_1} = \frac{V_2}{V_1} = \frac{I_1}{I_2}$$

- 8) A 40 kVA single phase ideal transformer has 400 turns on primary & 100 turns on secondary the primary is connected to 2000V, 50 Hz (i) supply determine secondary voltage on \downarrow open circuit.
- (ii) current flowing through 2 windings on full load.
- (iii) max value of ϕ .

$$P = 40 \text{ kVA}:$$

$$N_1 = 400.$$

$$N_2 = 100.$$

$$E_1 = 2000 \text{ V}.$$

$$f = 50 \text{ Hz}.$$

$$\frac{V_2}{40 \times 2000} = 4,$$

$$V_2 = 8000.$$

$$\frac{V_2}{2000} = \frac{1}{4}$$

$$V_2 = 500 \text{ V}.$$

$$V_2 = ?$$

$$I_1 = ?, I_2 = ?$$

$$\phi = ?$$

max.

$$\frac{V_2}{V_1} = \frac{N_2}{N_1}$$

$$P = 40 \text{ kVA}$$

$$N_1 = 400$$

$$N_2 = 100$$

$$E_1 = 2000 \text{ V}, f = 50 \text{ Hz}$$

$$E_2 = V_2 = ? \quad I_1 = ? \quad I_2 = ? \quad \phi_m = ?$$

$$\frac{E_2}{E_1} = \frac{N_2}{N_1}$$

$$P_1 = V_1 \times I_1$$

$$40 \times 10^3 = (2000) I_1$$

$$I_1 = \frac{40 \times 10^3}{2000}$$

$$I_1 = 20 \text{ A}$$

$$40 \times 10^3 = (500) I_2$$

$$I_2 = \frac{40 \times 10^3}{500}$$

$$I_2 = 80 \text{ A}$$

$$E_1 = 4.44 f \phi_m N_1$$

$$2000 = 4.44 \phi_m (400) (50)$$

$$\phi_m = 0.022$$

8) the number of load ratio required to a single phase 50 Hz transformer is $\frac{6600}{600}$ 6600/600V if the max value of ϕ in core is to be about 0.08 Wb find no of turns in each winding.
 $f = 50 \text{ Hz}$.

$$\frac{V_2}{V_1} = \frac{6600}{600}$$

$$\phi_m = 0.08$$

$$N = ?$$

$$E = 4.4 f \phi_m$$

$$= 4.4 \times 50 \times 0.08$$

$$E = 17.6$$

$$E_2 = 6600$$

$$E_1 = 4.4 f \phi_m N_1$$

$$E_1 = 600$$

$$\frac{600}{4.4 \times 50 \times 0.08} = N_1$$

$$6600 = 4.4 f \phi_m N_2$$

$$\frac{6600}{4.4 \times 50 \times 0.08} = N_2$$

$$\frac{600}{17.76} = 33.78$$

$$\frac{6600}{17.76} \Rightarrow 371.62$$

$$= 371.62$$

losses in transformer:

1) Cu $\left\{ \begin{array}{l} \text{primary} \rightarrow I_1^2 R_1 \\ \text{secondary} \rightarrow I_2^2 R_2 \end{array} \right.$

2) Iron loss $\left\{ \begin{array}{l} \text{hysteresis} \rightarrow w_h = \eta_h B_m^{1.6} f_v \\ \text{Eddy current losses} \rightarrow w_e = \eta_e B_m^2 f^2 \end{array} \right.$

$f_v \Rightarrow$ volume of core

$t \Rightarrow$ thickness of transformer.

Efficiency (η): ratio of output power & input power

$$\eta = \frac{P_o}{P_i} \text{ is called } \eta.$$

$$P_o = P$$

$$P_i = P_o + \text{losses}$$

$$\text{losses} = w_{cu} + w_{\text{iron losses (P)}}$$

$$\% = \frac{P_o}{P_o + \text{losses}} \times 100$$

Q) A single phase transformer is connected to a 230V, 50Hz supply the net cross sectional area of the core is 60 cm^2 the no of turns

efficiency in primary is 100% in secondary is 100% determine transformation ratio.

2) Max value of flux density in the core

3) Emf induced in secondary winding.

$$f = 50 \text{ Hz}$$

$$V_1 \Rightarrow E_1 = 230 \text{ V} \quad \Phi_m = B_m A$$

$$A = 60 \text{ cm}^2 \quad B_m = ?$$

$$N_1 = 500$$

$$N_2 = 100$$

$$\frac{N_2}{N_1} = \frac{100}{500} = 0.2$$

~~$$\Phi_m = B_m A$$~~

$$k = \frac{E_2}{E_1}$$

$$E_2 = ?$$

$$5) 230 \left(\frac{46}{3} \right)$$

$$\frac{E_2}{E_1} = \frac{N_2}{N_1}$$

$$E_2 = \frac{100}{500} \times 230 \times \frac{46}{3}$$

$$\frac{23}{1332.5}$$

$$\Phi_m = B_m A$$

$$E_1 = 4.44 f \Phi_m N_1$$

$$E_1 = 4.44 f B_m A N_1$$

$$B_m = \frac{230}{4.44 \times 50 \times 60 \times 10^{-4} \times 500}$$

$$B_m = 0.345 \text{ wb/m}^2 \text{ (or) Tesla.}$$

$$E_2 = 4.44 f \Phi_m N_2 = 459.5 \text{ V.}$$

$$\Phi_m = B_m A = 2.07 \text{ mwb}$$

Q) A 500 kVA transformer is desired to have a 4.13 mwb maximum core flux in a transformer at 110V & 50 Hz determine the required no of turns in primary $N_1 = ?$

$$P = 500 \times 10^3$$

$$\Phi_m = 4.13 \times 10^{-3}$$

$$V_1 = E_1 = 110 \text{ V} \quad f = 50 \text{ Hz.}$$

$$E_2 = 4.44 f \Phi_m N_2$$

$$110 = 4.44 \times 4.13 \times 10^{-3} \times 50 \times N_2$$

$$110 = 916.86 \times 10^{-3}$$

$$110 = 0.916 N_1$$

$$N_1 = 120.08$$

$$\frac{6400}{10.5}$$

$$320 \times 1362.5$$

Q) A 400 KVA transformer has a primary winding resistance of 0.5Ω & a secondary winding resistance of 0.001Ω & the iron loss is 2.5 kW & primary & secondary voltages are 5 kV & 320 V respectively if the power factor of the load is 0.85 determine the efficiency of transformer on full load & half full load.

$$E_1 = 5 \times 10^3 \text{ V} \quad P = 400 \text{ KVA}$$

$$E_2 = 320 \text{ V}$$

$$r_1 = 0.5 \Omega$$

$$r_2 = 0.001 \Omega$$

$$\cos \phi = 0.85$$

$$\eta_{FL} = ?$$

$$\eta_{H.FL} = ?$$

$$\boxed{\text{Power factor} = \cos \phi}$$

$$W_p = 2.5 \text{ kW} = 2.5 \times 10^3$$

$$\eta = \frac{P_o}{P_o + \text{losses}}$$

$$P_o = \text{rating} \times \text{power factor}$$

$$P_o = 400 \times 10^3 \times 0.85$$

$$= 340 \text{ kW}$$

$$\text{losses} = W_{cu} + W_i$$

$$W_{cu} = I_1^2 R_1 + I_2^2 R_2$$

$$P = V_2 I_2$$

$$I_2 = \frac{400 \times 10^3}{320}$$

$$P = V_1 I_1$$

$$= 1250 \text{ A}$$

$$400 \times 10^3 = 80 \times 10^3 \times I_1$$

$$I_1 = 80 \text{ A}$$

$$W_{cu} = (80)^2 \times 0.5 \times (1250)^2 \times 0.001$$

$$= 4762.5 \text{ W}$$

$$\eta_{HFL} = \frac{\frac{1}{2} P_0}{\frac{1}{2} P_0 + \left(\frac{1}{2}\right)^2 w_{cu} + w_i}$$

$$\eta_{FL} = \frac{340 \times 10^3}{340 \times 10^3 + 4762.5 + 2.5 \times 10^3}$$

$$= \frac{340000}{340000 + 4762.5 + 2500} \times 100$$

$$= \frac{340000}{347262.5} \times 100$$

$$= 97.9$$

$$\eta_{HFL} = \frac{\frac{1}{2} P_0}{\frac{1}{2} P_0 + \frac{1}{4} w_{cu} + w_i}$$

$$\frac{12.5 \times 10^3}{12.5 \times 10^3 + 450} = \frac{125 \times 100}{12500 + 450} = 96.52$$

8) In a 25 kVA, 2000/200V power transformer, the Iron loss & full load copper loss are 350 & 400W respectively calculate the η at unity power factor at full load & HFL

$$P = 25 \text{ kVA}$$

$$\cos \phi = 1$$

$$\eta_{FL} = ?$$

$$\frac{V_2}{V_1} = \frac{2000}{200}$$

$$W_i = 350$$

$$W_{cu} = 400 \quad \eta_{HFL} = ?$$

$P_0 = \text{rating} \times \text{power factor}$

$$P_0 = 25 \times 10^3$$

$$\text{losses} = 350 + 400 = 750$$

$$\eta_{HFL} = \frac{P_0}{P_0 + \text{losses}} \times 100$$

$$\eta_{HFL} = \frac{25 \times 10^3}{25 \times 10^3 + 750} \times 100$$

$$\frac{25 \times 10^3 + \frac{1}{4}(750)}{25 \times 10^3 + 750} = \frac{25 \times 10^3}{25 \times 10^3 + 750} \times 100$$

$$= 12.5 \times 10^3$$

$$12.5 \times 10^3 + 187.5$$

$$= \frac{125 \times 10^4}{125000 + 187.5}$$

$$= \frac{25 \times 10^3}{25750}$$

$$\times = 97.087$$

Q) calculate the current drawn by the primary of transformer which steps down 200 to 20V to operate a device of resistance 20Ω assume η of transformer to be 80%.

$$V_1 = 200V$$

$$I_1 = ?$$

$$V_2 = 20V$$

$$R_2 = 20\Omega$$

$$\eta = 80\%$$

$$I_2$$

$$80\% = \frac{V_2 \times I_2}{V_1 \times I_1} \times 100$$

$$\frac{V_2}{R_2} = I_2$$

$$80 = \frac{200 \times I_2}{20 \times I_1} \times 100$$

$$I_2 = \frac{200}{20}$$

$$0.8 = \frac{2000}{20 I_1}$$

$$I_2 = 10$$

$$20 I_1 = \frac{20000}{8}$$


$$I_1 = \frac{20000}{8 \times 20}$$

$$= \frac{1000}{8}$$



$$I_1 = 125$$

Induction Motors:

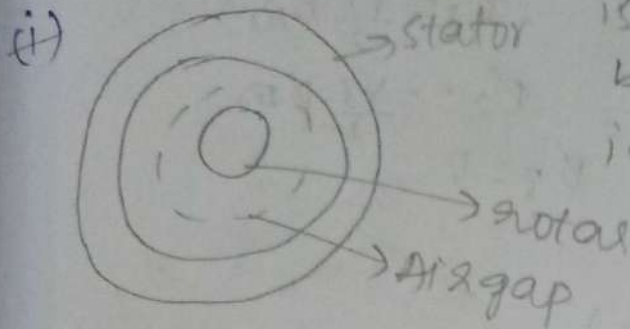It consists of two parts stator, rotor & has air gap in b/w them & due to current in R, Y, B a magnetic flux is generated & due to the interaction b/w these fluxes a rotating field is produced in the air gap



(i) Rotating Magnetic field:

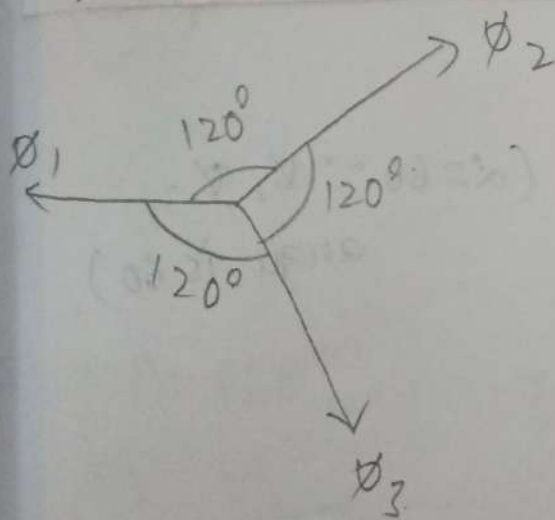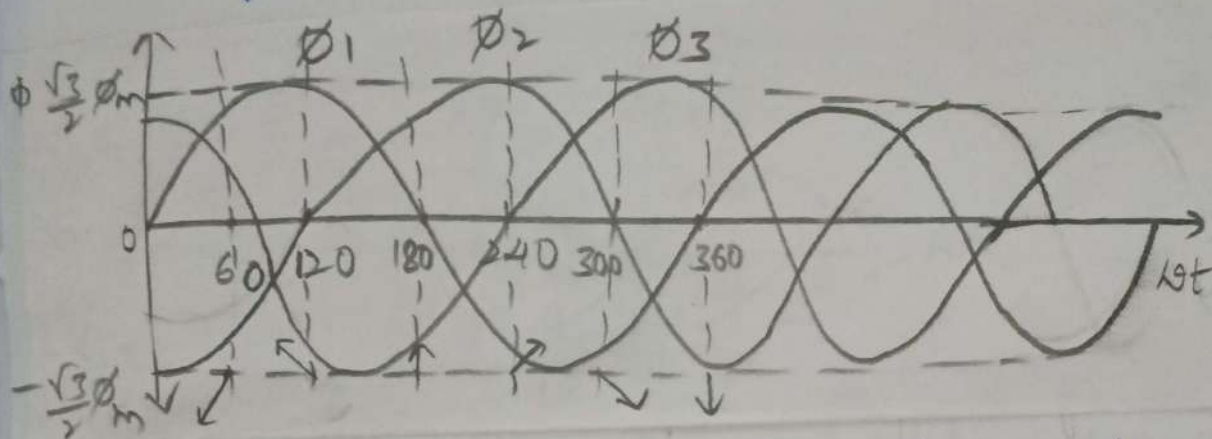

$$\phi_1 = \phi_m \sin \omega t$$

$$\phi_2 = \phi_m \sin(\omega t - 120^\circ)$$

$$\phi_3 = \phi_m \sin(\omega t - 240^\circ)$$

a) at position 1; $\omega t = 0$

$$\phi_1 = \phi_m \sin(0) = 0$$

$$\phi_2 = \phi_m \sin(0 - 120^\circ)$$

$$= -\phi_m \sin 120^\circ$$

$$= -\phi_m \sin(90 + 30)$$

$$= -\phi_m \cos 30^\circ$$

$$\phi_2 = -\frac{\sqrt{3}}{2} \phi_m$$

$$\phi_3 = \phi_m \sin(0 - 240)$$

$$= -\phi_m \sin(180 + 60^\circ)$$

$$= +\phi_m \sin 60^\circ$$


$$\phi_3 = \phi_m \frac{\sqrt{3}}{2}$$

at position ②

$$\phi_1 = \frac{\sqrt{3}}{2} \phi_m$$

$$\phi_2 = -\frac{\sqrt{3}}{2} \phi_m$$

$$\phi_3 = 0$$

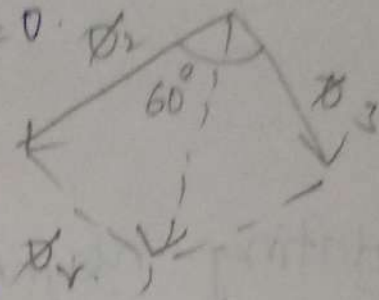

According to parallelogram law resultant phasor magnitude:

$$\text{flux } \phi_y = 2a \cos \frac{\alpha}{2}$$

$$= 2 \frac{\sqrt{3}}{2} \phi_m \cos \frac{60}{2}$$

($\alpha = 60^\circ \because \phi_2, \phi_3$
angle is 60°)

$$= 2 \frac{\sqrt{3}}{2} \phi_m \cos 30^\circ$$

$$= 2 \left(\frac{\sqrt{3}}{2} \times \frac{\sqrt{3}}{2} \right) \phi_m$$

$$= \frac{3}{2} \phi_m$$


$$\boxed{\phi_y = 1.5 \phi_m}$$

a) at position ②

$$\phi_1 = \frac{\sqrt{3}}{2} \phi_m$$

$$\phi_2 = -\frac{\sqrt{3}}{2} \phi_m$$


$$\phi_3 = 0$$

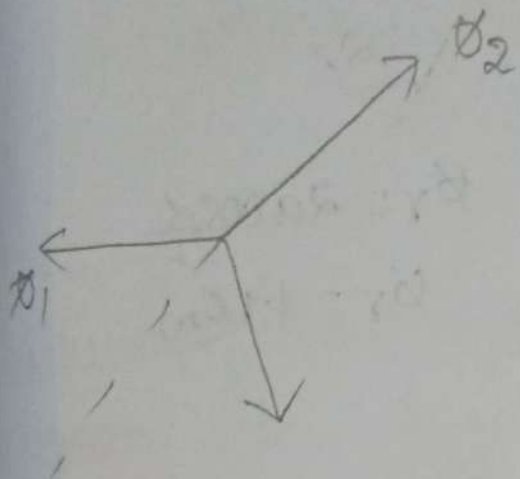

$$\phi_r = 2a \cos 30^\circ$$

$$= \left| \frac{\sqrt{3}}{2} \phi_m \right|$$

$$\boxed{\phi_r = 1.5 \phi_m}$$

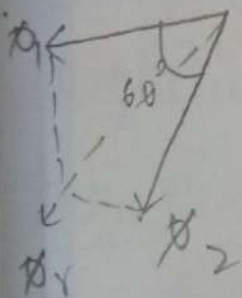


3) $\text{rot} = 120^\circ$

$$\phi_1 = \frac{\sqrt{3}}{2} \phi_m$$

$$\phi_2 = 0$$

$$\phi_3 = -\frac{\sqrt{3}}{2} \phi_m$$

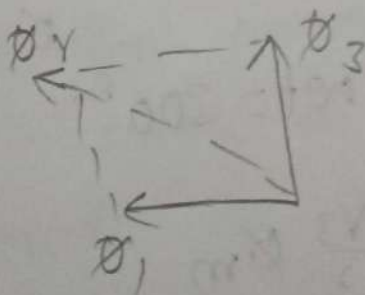

$$\phi_r = 2a \cos 30^\circ$$

$$= \left| \frac{\sqrt{3}}{2} \phi_m \right|$$


$$\boxed{\phi_r = 1.5 \phi_m}$$

at (A) position. $\omega t = 180^\circ$

$$\phi_1 = 0$$

$$\phi_2 = \frac{\sqrt{3}}{2} \phi_m$$

$$\phi_3 = -\frac{\sqrt{3}}{2} \phi_m$$

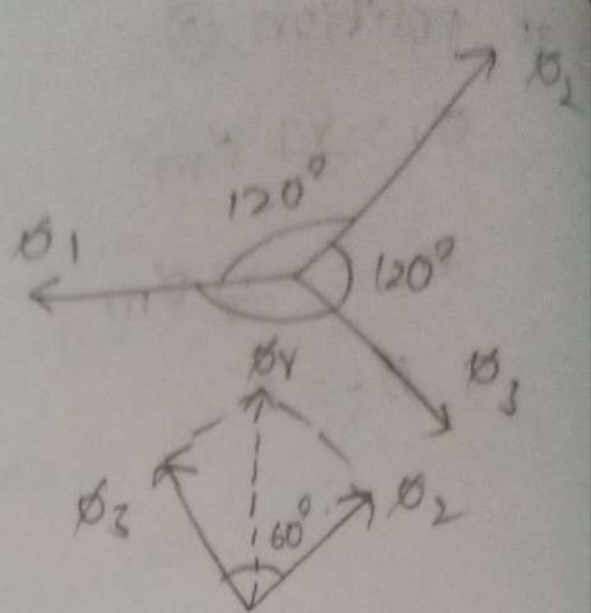

$$\phi_Y = 2a \cos \frac{\alpha}{2}$$


$$\phi_Y = 1.5 \phi_m$$

at position (B) $\omega t = 240^\circ$

$$\phi_1 = -\frac{\sqrt{3}}{2} \phi_m$$

$$\phi_2 = \frac{\sqrt{3}}{2} \phi_m$$

$$\phi_3 = 0$$

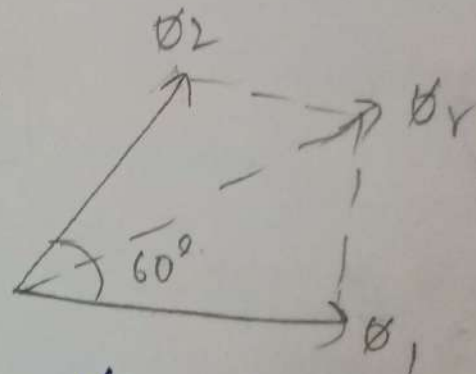

$$\phi_Y = 2a \cos \frac{\alpha}{2}$$


$$\phi_Y = 1.5 \phi_m$$

at position (C) $\omega t = 300^\circ$

$$\phi_1 = -\frac{\sqrt{3}}{2} \phi_m$$

$$\phi_2 = 0$$

$$\phi_3 = \frac{\sqrt{3}}{2} \phi_m$$

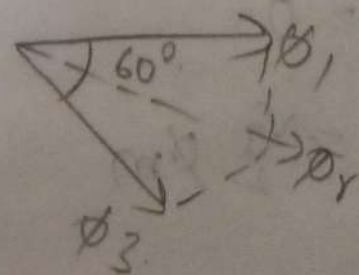


at position $\theta = 360^\circ$

$$\phi_1 = 0$$

$$\phi_2 = -\frac{\sqrt{3}}{2} \phi_m$$

$$\phi_3 = \frac{\sqrt{3}}{2} \phi_m$$

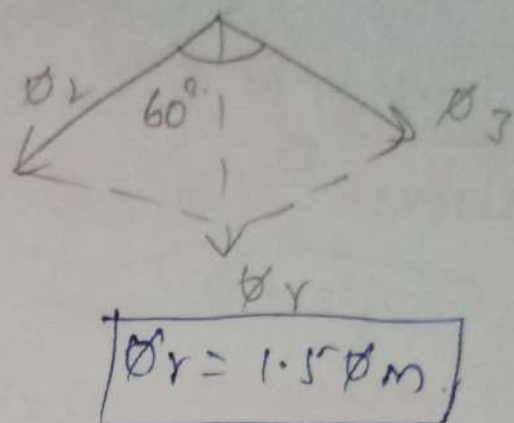

Whenever three phase (3 ϕ) input AC voltage given to the induction motor three phase currents starts flowing which produce magnetic flux &

Definition of rotating magnetic field (RMF):

The magnetic field due to three phase flux interaction the magnetic rotates in the air gap with a fixed speed & constant magnitude is known as rotating magnetic field!

winding which acts as current carrying conductor now. Whenever a current carrying conductor placed in the magnetic field it will experience a mechanical force. This twisting or turning movement of force is called Torque. Because of this torque the rotor starts in the direction of EMF. Rotor always tries to catch the synchronous speed but it can never catch the N_s (^{synchronous} speed) and will always run less than synchronous speed.

3 ϕ Induction motor:

Principle: B1H

Induction motor works on the principle of electromagnetic induction when three phase supply is given to stator winding. RMF is produced and the induction motor will rotate with synchronous speed (N_s). The induction motor is also called as rotating transformer.

$$N_s = \frac{120f}{P}$$

f = frequency


P = Poles.

Units of N_s is r.p.m

Construction of Induction motor:

- 1) Stator
- 2) Rotor {
 - squirrel cage rotor
 - or slip ring motor.

stator:

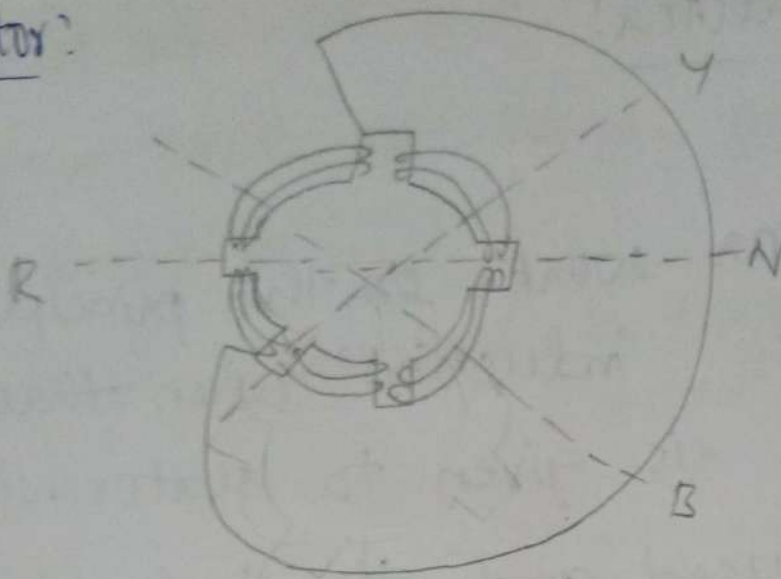

Silicon
laminated
Steel.


or delta

stator has laminated type of construction and made up of stampings and thickness of each stamping is 0.4 to 0.5mm. And these stampings are slotted to carry stator winding. Stator core carries a 3 phase winding connected either in star or delta. So, this winding is excited by 3 ϕ supply produces rotating magnetic field.

2) Rotor!

low torque appli

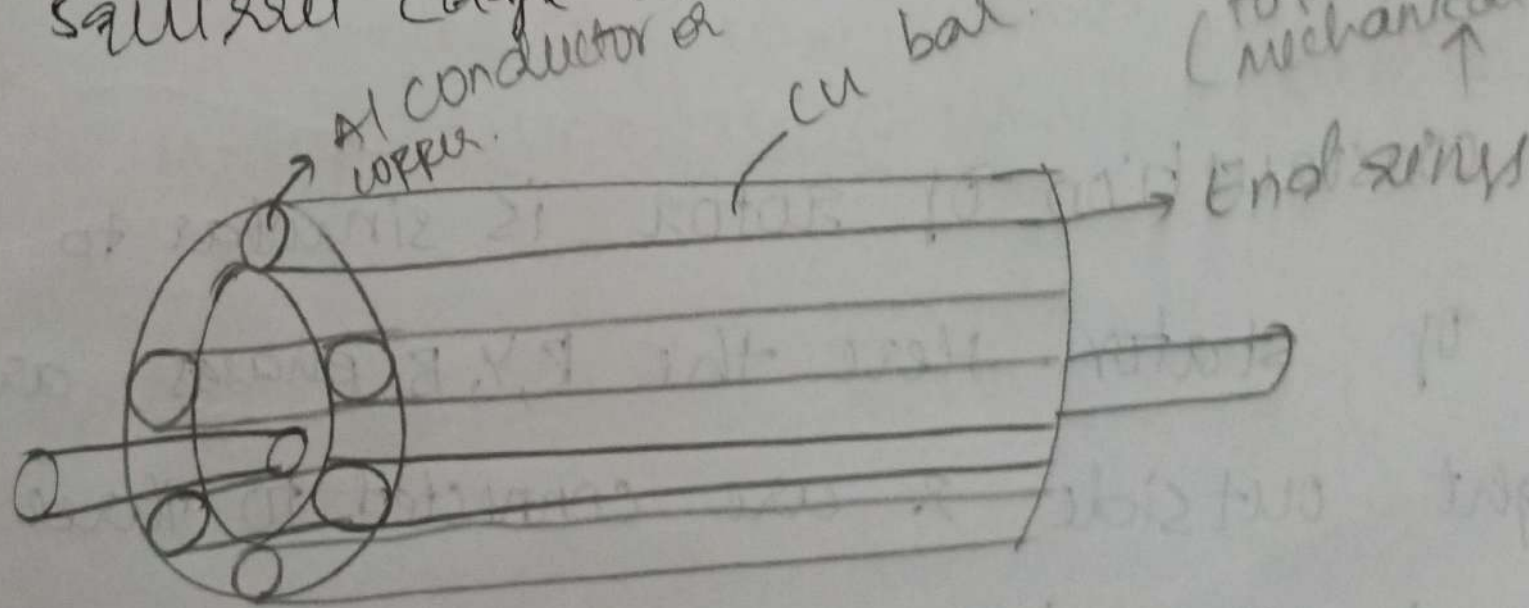(i) squirrel cage rotor: low cost due to no use of resistance.
(to provide good mechanical strength)




increasing low starting torque! we use it

The rotor consisting of copper and aluminium bar conductor these are the rotor conductors
the copper bars are permanently

shorted at each end with the help of end rings. These end rings provide good mechanical strength.

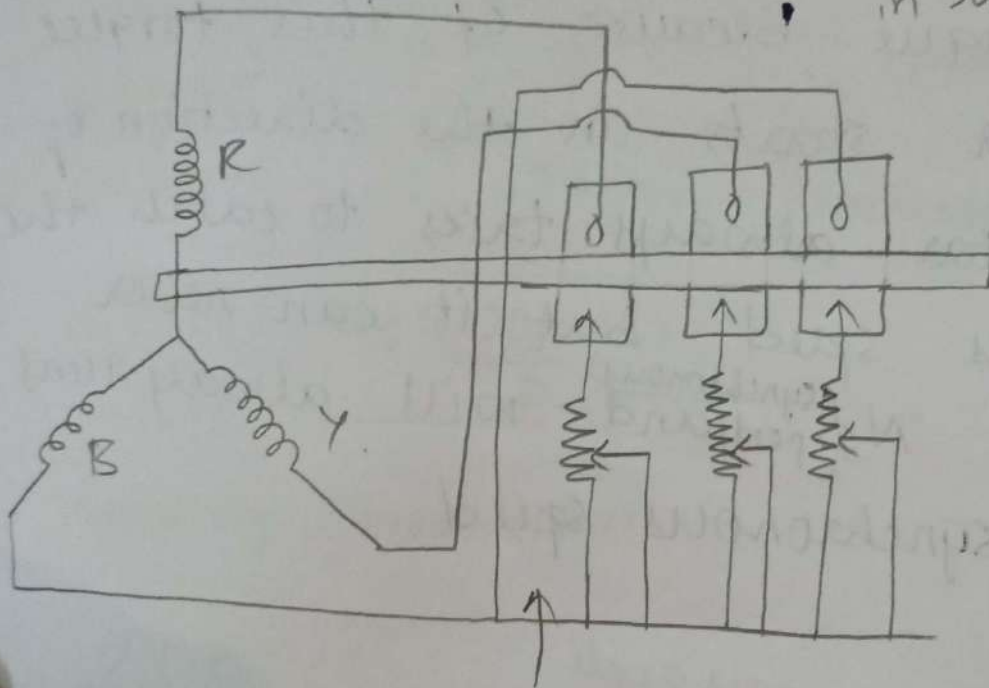~~2) (ii)~~ (ii) slip Ring rotor: To limit the starting current & are also used in lifts.



$$T \propto \frac{R_2}{X_2}$$

External resistance box


in case of High torque applications

High $\cos \phi$ due to the use of resistances & brushes.

The construction of rotor is similar to that of stator. Here the R, Y, B phases are brought outside & are connected to three slip rings with the help of brushes & then external resistances will be added in each phase to improve the starting Torque.

shorted at each end with the help of end rings. These end rings provide good mechanical strength.

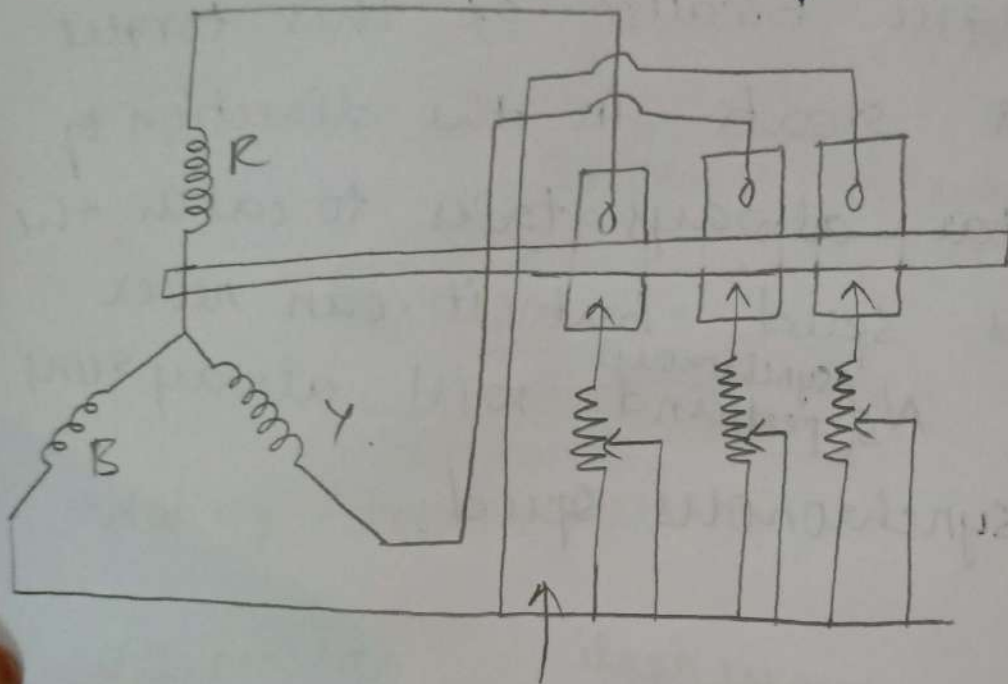(ii) slip Ring rotor: To limit the starting current & are also used in lifts.



External resistance box

in case of High torque applications High cost due to the use of resistances & brushes. The construction of rotor is similar to that of stator. Here the R, Y, B phases are brought outside & are connected to three slip rings with the help of brushes & then external resistances will be added in each phase to improve the starting Torque.

Under running condition the brushes will be removed & now 3 slip rings form closed path that is joined together to form a simple bar. Now, it will act similar to that of squirrel cage rotor (motor) to limit losses.

Slip (s):

$$s = \frac{N_s - N_r}{N_s}$$

N_s = synchronous speed.

N_r = rotor speed / (motor) actual speed.

$$N_s = \frac{120f}{P}$$

$$sN_s = N_s - N_r$$

$$N_r = N_s - sN_s$$

$$N_r = N_s(1-s)$$

$$\% s = \frac{N_s - N_r}{N_s} \times 100$$

It is defined as the ratio of difference b/w synchronous speed & motor speed to the synchronous speed.

And it is denoted by s .

Rotor frequency (f_r):

$$\text{Slip speed} = N_s - N_r$$

dividing with N_s on both sides.

$$\frac{\text{slip speed}}{N_s} = \frac{N_s - N_r}{N_s}$$

$$\frac{120f_r}{P} = s$$

$$\frac{120f}{P}$$

$$\boxed{f_r = sf}$$

f_r = rotor frequency.


f = supplied frequency.

s = slip.

Rotor EMF (E_{2r}):
 EMF induced $\propto N_s$ (synchronous speed)
 in rotor.

E_{2r} = rotor emf at running condⁿ.
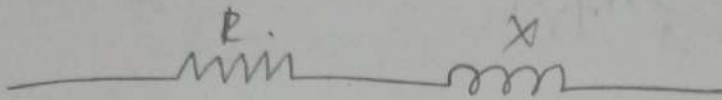
$$I = \frac{V}{R} \Rightarrow \text{for DC circuits}$$



$$I = \frac{V}{Z} \Rightarrow \text{for AC}$$

$Z \Rightarrow$ Impedance.

$$= \frac{V}{R + jX}$$

$$= \frac{V}{\sqrt{R^2 + X^2}} \quad \sqrt{R^2 + X^2} \Rightarrow \text{magnitude}$$

$$E_{2r} \propto N_s$$

$$E_{2r} \propto N_s - N_r$$

$$\frac{E_{2r}}{E_2} \propto \frac{N_s - N_r}{N_s}$$

$$\frac{E_{2r}}{E_2} = s$$

$$\boxed{E_{2r} = sE_2}$$

→ Rotor resistance (R_2):

$$\boxed{R_{2r} = R_2}$$

→ Rotor reactance X_2 :

$$X_2 = \omega L \quad [\because \omega = 2\pi f]$$
$$= 2\pi f_r L$$

$$X_{2r} = 2\pi(f_s s) L \quad f_r = s f_s$$
$$= (2\pi f_s) \cdot s \cdot L$$

$$\boxed{X_{2r} = s \cdot X_2}$$

→ Rotor Impedance Z_2

$$Z_2 = \sqrt{R_2^2 + X_2^2}$$

$$Z_{2r} = \sqrt{R_{2r}^2 + (X_{2r})^2} \quad [\because R_{2r} = R_2]$$

$$\boxed{Z_{2r} = \sqrt{R_2^2 + (sX_2)^2}}$$

Z_{2r} = Impedance of rotor at running condition

R_2 = Resistance of rotor.

X_2 = rotor reactance

s = slip

Rotor current (I_{2r}):

$$I_2 = \frac{E_2}{Z_2}$$

$$= \frac{E_2}{\sqrt{R_2^2 + X_2^2}}$$

E_{2r} = Emf induced in rotor under running condition.

$$I_{2r} = \frac{E_{2r}}{Z_{2r}} = \frac{sE_2}{\sqrt{R_2^2 + (sX_2)^2}}$$


Rotor power factor:

$$\cos \phi_2 = \frac{R_2}{Z_2}$$

$$= \frac{R_2}{\sqrt{R_2^2 + X_2^2}}$$

$$\cos \phi_{2r} = \frac{R_{2r}}{Z_{2r}}$$

Impedance triangle.

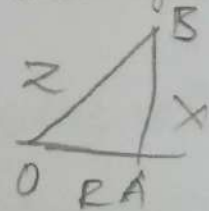

$$OB^2 = OA^2 + AB^2$$

$$OB = \sqrt{OA^2 + AB^2}$$

$$\cos \phi_{2r} = \frac{R_2}{\sqrt{R_2^2 + (sX_2)^2}}$$

$$Z = \sqrt{R^2 + X^2}$$

$$\cos \phi = \frac{\text{adj}}{\text{Hypotenuse}}$$

$$= \frac{R}{\sqrt{R^2 + X^2}}$$

★★ Torque Equation of 3phase I.M:

$$T \propto \phi I$$

$$T \propto \phi_2 I_{2r} \cos \phi_{2r}$$

I_{2r} = rotor current at running condition.

$$T \propto E_2 \cdot \frac{E_{2Y}}{Z_{2Y}} \cdot \frac{B_{2Y}}{Z_{2Y}}$$

$$T \propto E_2 \cdot \frac{SE_2}{\sqrt{R_2^2 + (SX_2)^2}} \cdot \frac{R_2}{\sqrt{R_2^2 + (SX_2)^2}}$$

$$T \propto \frac{SE_2^2 R_2}{R_2^2 + (SX_2)^2}$$

$$T = \frac{k \cdot SE_2^2 R_2}{R_2^2 + (SX_2)^2}$$

$$k = \frac{3}{2\pi N_s}$$

$$T = \frac{3SE_2^2 R_2}{2\pi N_s (R_2^2 + (SX_2)^2)}$$

$$T = \frac{3}{2\pi N_s} \frac{SE_2^2 R_2}{R_2^2 + (SX_2)^2}$$

N_s = synchronous speed

E_2 = Emf induced in rotor

R_2 = rotor resistance.

X_2 = rotor reactance

s = slip

T = Torque

I_2 = current induced in rotor

$I_2 \rightarrow$ stand still.

$\cos\phi_2$ = Power factor of rotor.

X_{2r} = rotor reactance at running condition.

$\cos\phi_{2r}$ = Power factor of rotor at running condition.

Q) A 10 pole, 50 Hz, 3 ϕ I.M runs at 485 rpm. What will be the rotor frequency of rotor current.

$$\begin{array}{r} 600 \\ - 485 \\ \hline 115 \end{array}$$

$$P = 10 \quad f = 50 \text{ Hz} \quad N_r = 485$$

$$f_r = sf$$

$$s = \frac{600 - 485}{600} = \frac{115}{600} = 0.191$$

$$N_s = \frac{120f}{P} = \frac{120(50)}{10} = 600 \text{ rpm}$$

$N_s = 600 \text{ rpm}$

$$s = 0.191$$

$$f_r = s \cdot f$$
$$= 0.191 \times 50$$

$$f_r = 9.55 \text{ Hz}$$

Q) A 3 ϕ induction motor is wound for 4 poles & is supplied from 50Hz system calculate:

(i) N_s

(ii) speed of motor at 4% of slip.

(iii) Rotor current frequency when motor runs at 600 rpm.

$$P = 4, f = 50 \text{ Hz}$$

$$s = 0.04$$

$$N_r = N_s(1 - s)$$

(i)

$$N_s = \frac{120f}{P}$$

$$= \frac{120 \times 50}{4}$$

$$= 1500 \text{ rpm}$$

$$s = \frac{N_s - N_r}{N_s} \times 100$$

$$\begin{aligned}
 \text{(ii)} \quad N_r &= N_s(1-s) \\
 &= 1500(1-0.04) \\
 &= 1500(0.96) \\
 &= 1440 \text{ rpm}
 \end{aligned}$$

$$\begin{aligned}
 \text{(iii)} \quad f_r &= s \cdot f \\
 s &= \frac{N_s - N_r}{N_s} \\
 &= \frac{1500 - 600}{1500} \\
 &= \frac{700}{1500} = 0.6 \\
 f_r &= 0.6 \times 50 \\
 &= 30 \text{ Hz}
 \end{aligned}$$

Q) A 3Ø 6 pole 50Hz induction motor is running with a slip of 4% find

(i) N_s (ii) Motor speed (iii) slip speed
(iv) frequency of Induction motor

$$P = 6 \quad f = 50 \text{ Hz} \quad s = 0.04$$

$$\text{(i)} \quad N_s = \frac{120 \times 50}{6} = 1000 \text{ rpm}$$

$$\text{(ii)} \quad N_r = N_s(1-s) = 1000(0.96) = 960 \text{ rpm}$$

$$N_r = 960 \text{ Hz rpm}$$

$$\text{slip speed} = 1000 - 960$$

$$= 40.$$

$$f_r = s \cdot f_s$$

$$s = \frac{N_s - N_r}{N_s}$$

$$= \frac{1000 - 960}{960}$$

$$= \frac{40}{960}$$

$$= 0.041$$

$$= 0.04 \times 50$$

$$= 0.4 \times 5$$

$$= 2 \text{ Hz}$$

Q) A 6 pole 3 ϕ 50Hz induction motor is running at a full load with slip of 4% the rotor is star connected its resistance

$$p = 6 \quad f_s = 50 \text{ Hz} \quad s = 0.04 \quad \left. \begin{array}{l} \text{reactances are} \\ 0.25 \times 1.5 \Omega \end{array} \right\}$$

$$R_2 = 0.25 \quad X_2 = 1.5 \Omega \quad \text{the emf } E_2 = 100 \text{ V}$$

rotor is 100 V find $I_2 = ?$

$$I_{2Y} = \frac{S E_2}{\sqrt{R_2^2 + (S X_2)^2}}$$

$$NS = \frac{120f}{P}$$

$$= \frac{120 \times 50}{6} = 1000 \text{ Hz}$$

$$S = 0.04 \quad I_{2Y} = \frac{0.04 \times 100}{\sqrt{(0.2)^2 + (0.04 \times 1.5)^2}}$$

$$= \frac{4}{\sqrt{0.0625 + 3.6 \times 10^{-3}}}$$

$$= \frac{4}{\sqrt{0.06286}} = \frac{4}{\sqrt{0.25071}}$$

0.06

$$= 15.5 \text{ A}$$

Q) A 6 pole 3 ϕ 50 Hz induction motor is running at full load with a slip of 4%. rotor is star connected & its resistances & reactance are 0.45 Ω & 2.5 Ω

$$f = 50 \text{ Hz} \quad s = 0.04 \quad R_2 = 0.45, \quad X_2 = 2.5$$

the emf b/w slip rings is 120V. Determine rotor current & Power factor assuming the slip rings are short circuited.

$$E_2 = 120V$$

$$\cos \phi_{2r} = \frac{R_2}{\sqrt{R_2^2 + (S X_2)^2}}$$

$$= \frac{0.45}{\sqrt{(0.45)^2 + (0.04 \times 2.5)^2}}$$

$$= \frac{0.45}{\sqrt{0.2125}}$$


$$= \frac{0.45}{0.4609}$$

$$\cos \phi_{2r} = 0.976$$

$$I_{2r} = \frac{0.04 \times 120}{\sqrt{(0.45)^2 + (0.04 \times 2.5)^2}}$$

$$= \frac{4.8}{0.4609} = 10.41A$$

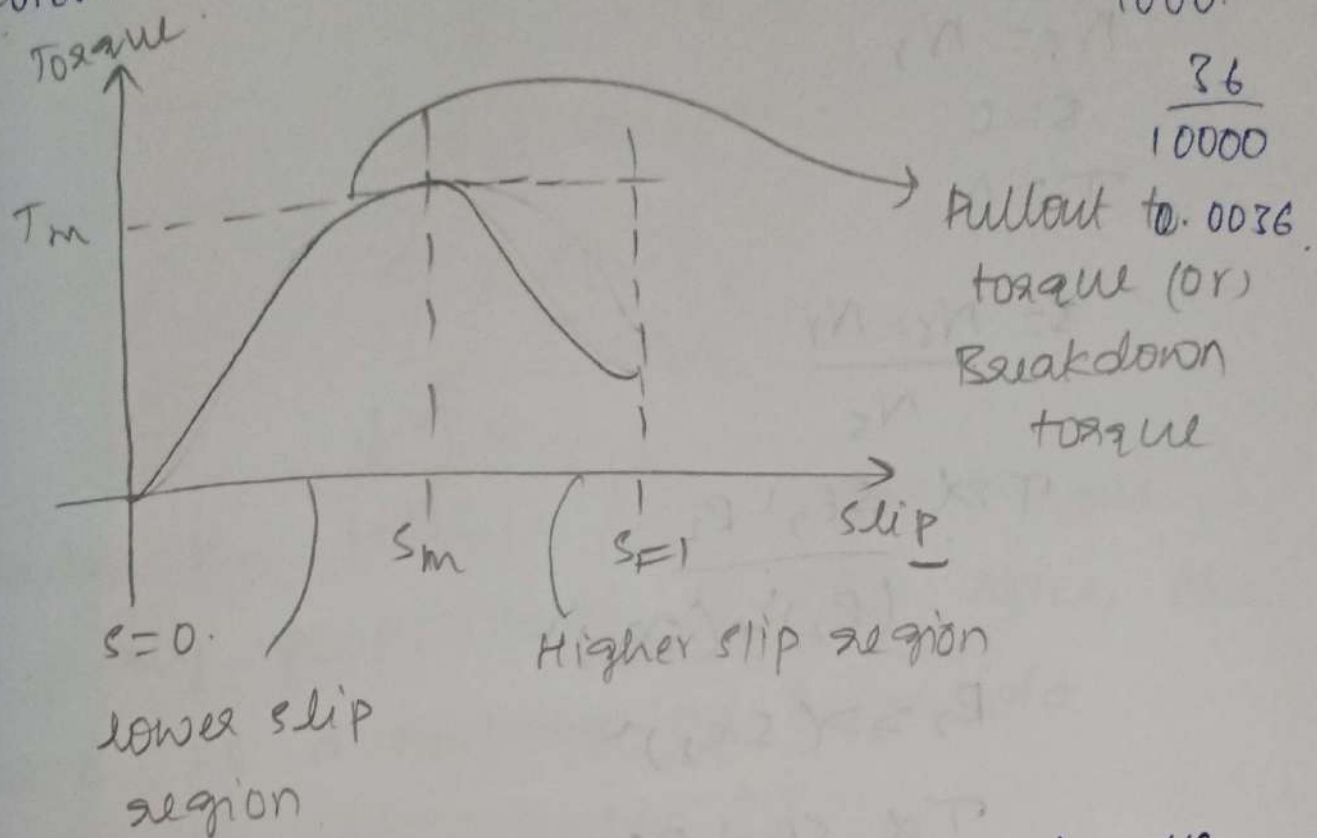417. ~~417~~ Torque-slip characteristics of 3 phase induction motor:



The performance curve drawn b/w torque against slip known as torque slip characteristics of an induction motor.

Torque expression:

$$T \propto \frac{s E_2^2 R_2}{(R_2)^2 + (s X_2)^2}$$

The relation b/w Torque and slip, the entire operating region b/w 0 & 1 is divided into two 1 is lower slip

region & higher slip region!

lower slip region!

$$N_s = N_r$$

$$s = 0$$

$$T = 0.$$

$$s = \frac{N_s - N_r}{N_s}$$

$$T \propto \frac{s E_2^2 R_2}{(R_2)^2 + (s X_2)^2}$$

$$R_2 \gg (s X_2)^2$$

$$T \propto \frac{s E_2^2 R_2}{R_2^2}$$

$$T \propto s$$

$$\text{as } T \uparrow \quad s \uparrow$$

Under the lower slip region Torque is directly proportional to slip. Hence, the curve is a straight line.

Higher slip region!

When the slip further rises beyond $s = s_m$ then the term R_2^2 is very smaller than

$$sX_2^2$$

$$T \propto \frac{SE_2^2 R_2}{R_2^2 + (sX_2)^2}$$

$$(sX_2)^2 \gg R_2^2$$

$$T \propto \frac{SE_2^2 R_2}{s^2 X_2^2}$$

$$\downarrow T \propto \frac{1}{s} \downarrow$$

Under the Higher slip region Torque is inversely proportional to slip. Hence, the curve is a rectangular hyperbola.

losses in 3 ϕ induction motor:

losses are classified into two types

- (i) constant losses
- (ii) variable losses.

(i) constant losses:

These are classified into two types

- (a) Iron losses
- (b) Mechanical losses

(a) Iron losses: The losses which occur in the core of stator & rotor. Iron losses

includes hysteresis & eddy current losses

Iron losses are also known as core losses


(i) Mechanical losses:

losses which occurs in shaft of induction motor. losses includes friction & windage losses

(ii) Variable losses: These are also called as copper losses which occur at winding of stator & rotor. Power wasted in the form of $I^2 R$ losses known as variable losses.

cu losses usually occur in windings.


star connection

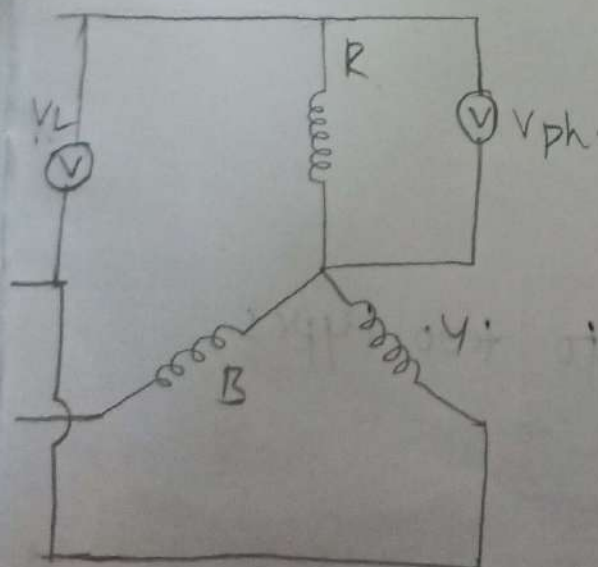

$$V_L = \sqrt{3} V_{ph}$$

$$I_L = I_{ph}$$

Delta connection

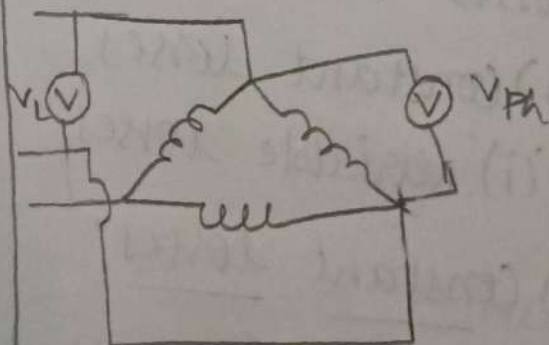


$$V_L = V_{ph}$$

$$I_L = \sqrt{3} I_{ph}$$

UNIT-IV

Diode and its characteristics


P-N Junction diode:

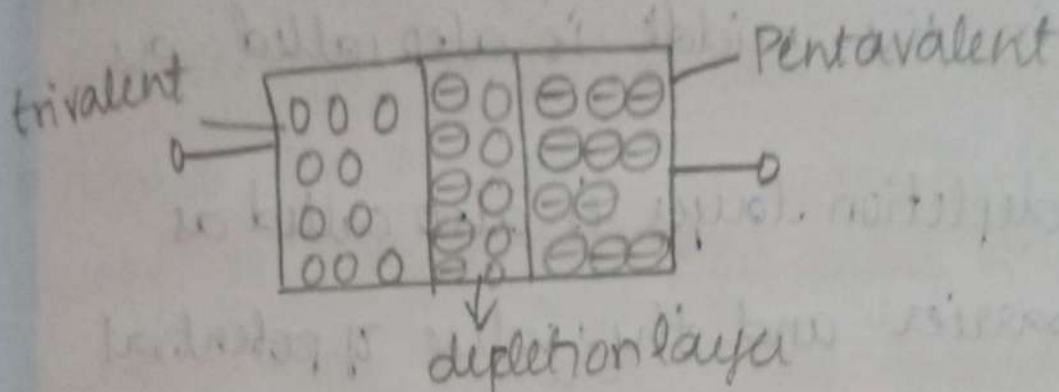

Potential barriers - Si - 0.7 V

Ge - 0.3 V

depletion layer

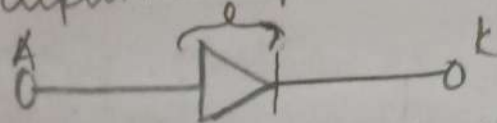

Diode symbol

→ unidirectional device

→ conduction starts from Anode to cathode in forward bias.

→ When a p-type semiconductor is sandwiched with n-type materials (trivalent impurities is added to pentavalent impurities) where p-type material consists of holes as majority carriers and electrons as minority carriers. Where as in n-type materials electrons are majority carriers & holes are minority charge carrier.

→ Whenever, it is joined together minority carriers, in p-type element moves away from the holes towards the junction & holes from n-type elements moves towards junction & thereby these holes & electrons from depletion region or layer in the middle is also called as junction.


→ Where, depletion layer is also called as potential barrier and the value of potential barrier for silicon is $0.7V$ & germanium is $0.3V$

Diode:

→ P-n junction diode is a two terminal device which allows electric current in only one direction while blocks current in opposite direction.

Working of P-N junction diode:

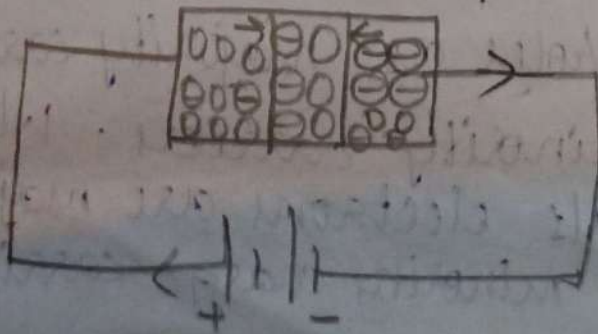1. Forward Biased mode: forward blocking mode




- Excitation is called biasing
- Insulation & resistance is reduced in forward bias
- Depletion layer becomes thin in forward bias.
- Whenever a +ve terminal is connected to p-type & -ve terminal to n-type & due to +ve charge to p-type repulsion takes b/w positive charge & holes so holes moves towards junction & combine with electrons.
- When the positive terminal of the supply or battery source is connected to p-type (Anode) and negative terminal is connected to n-type (Cathode side) of the diode is known as forward bias.
- In forward bias mode the p-side holes repulse due to charge carriers of positive terminal & in the n-side electron repulse due to charge carriers to -ve terminal.
- Due to this the width of depletion layer will be reduced at some forward voltage depletion layer will break known as

Breakdown voltage ^{current due to minority charge carriers in F.B is called leakage current}

→ In forward biased condition p-n junction diode acts as on switch due to very low resistance of depletion layer.

Reverse biased mode:

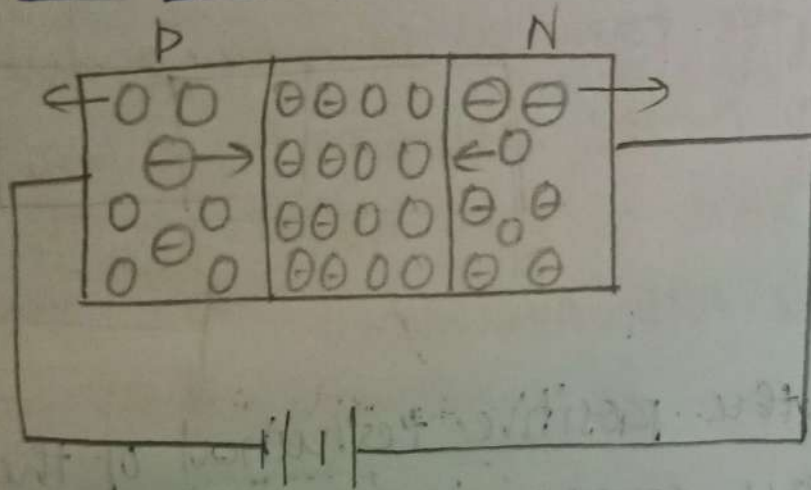


→ The supply or battery when positive terminal is connected to n-side & -ve terminal of battery connected to p-side. This mode is known as reverse biased mode.

→ In the reverse biased condition holes are attracted by the -ve terminal & vice versa.

→ Due to this the depletion layer width increases & then there is no conduction.


from p to n

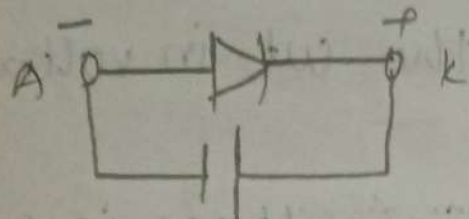→ At this instant, P-n junction diode acts as off switch due to very high resistance of depletion layer.



f. conduction state

V-I characteristics:

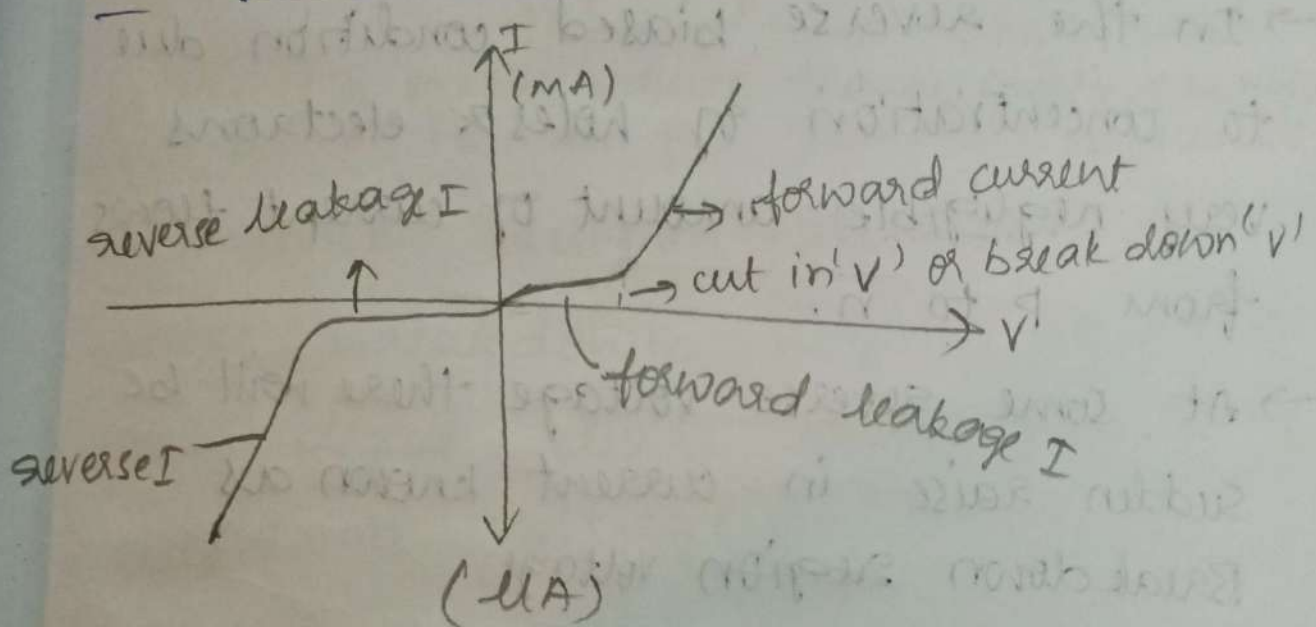

In. forward conduction state when the voltage is used the diode conducts.

Cut-in $V \rightarrow Si - 0.7V$

$Ge - 0.3V$

In the forward biased mode a small amount or negligible amount of current flows through the device in

the range of micro Amperes to milli A

→ At some ^{forward} voltage the current instant

-aneously raise known as cut-in voltage or break down voltage.

→ for Germanium the cut-in voltage is 0.3V

→ for Silicon the cut-in voltage is 0.7V

→ In the reverse biased condition due to concentration of holes & electrons very negligible amount of current flows from p to n.

→ At some reverse voltage there will be sudden raise in current known as Break down ~~region~~ voltage.


→ The sharp increase in current in reverse direction due to which some heat is produced which may damage the device

Zener diode: Properly or heavily doped compared to normal diode.



- 1) Avalanche break down mode. Properly or heavily doped.
- 2) Zener break down.

1) Avalanche break down:

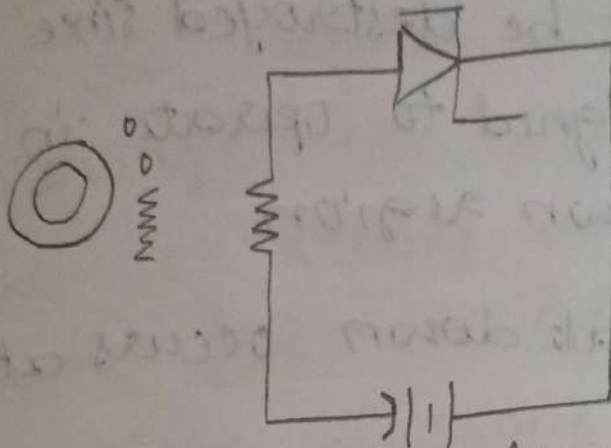

We connect resistance in series in order to provide protection

as external resistance is applied current

is reduced & heat reduces thereby safety is provided. Zener diode is a p-n junction semiconductor

- for device designed to operate in

reverse breakdown region. It is a highly doped diode which has sharp breakdown voltage.

Avalanche break down:


This break down occurs in normal & Zener diode at reverse voltage when high amount of reverse voltage is applied to p-n junction diode. free e^- s gain large amount of energy

as a result electric current in diode rises rapidly.

This sudden increase in current may permanently destroy normal diode however Zener diode may not be destroyed since it is carefully designed to operate in Avalanche break down region.

Avalanche break down occurs at greater than 6V.

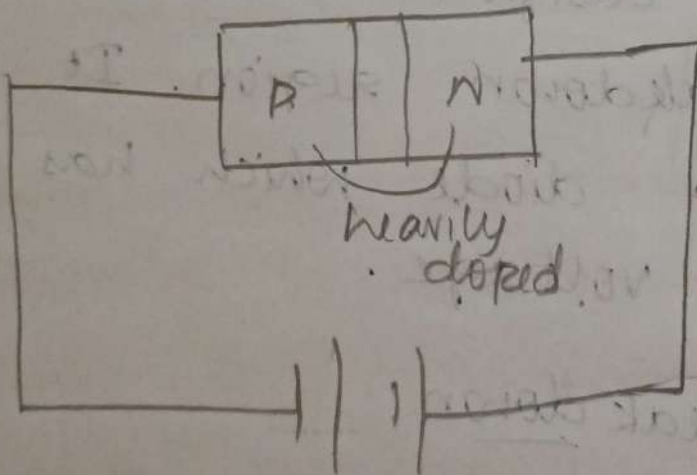2) Zener break down: Electrical intensity depends on length of depletion region




$$E = \frac{V}{d}$$

When a high amount of voltage is given, electrical field will be produced around the diode and due to the voltage the closely packed electrons with covalent

bond in depletion region can be broken easily & electrons can be pulled out & depletion layer vanishes naturally.

When reverse biased voltage applied to diode the moment it reaches close to zener voltage the electric field in depletion layer is strong enough to pull the electrons from covalent bonds of depletion layer. These electrons gain sufficient energy from electric field thereby conduction starts & zener breakdown occurs at voltage less than 6V.

I-V characteristics:

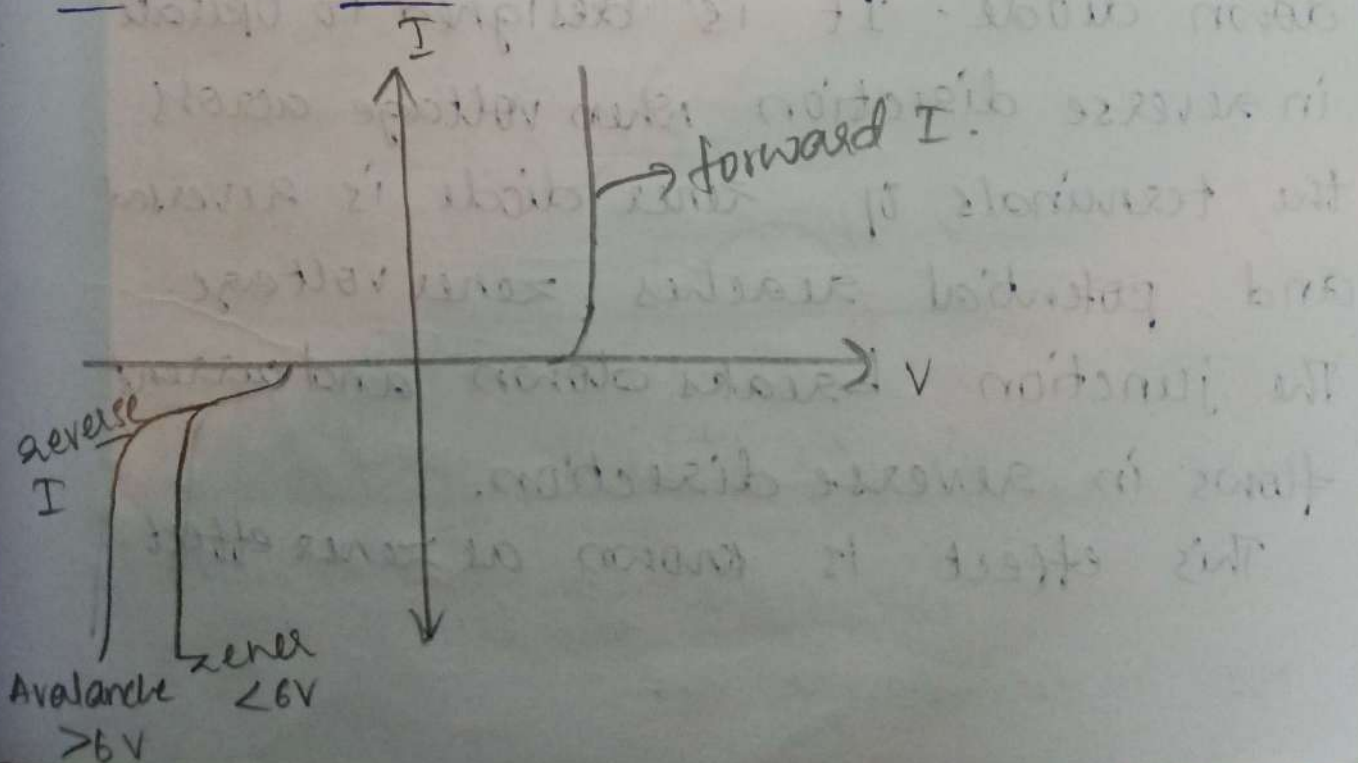

Advantages:

- 1) Power dissipation capacity is very high
- 2) High accuracy
- 3) Small in size (compact)
- 4) Low cost

Applications:



- 1) It is used in voltage stabilizers
- 2) As voltage references
- 3) Used in switching operations.
- 4) Used in various protection circuits.

Zener effect:

The zener diode also known as break down diode. It is designed to operate in reverse direction when voltage across the terminals of zener diode is reversed and potential reaches zener voltage. The junction breaks down and current flows in reverse direction.

This effect is known as zener effect.


1) Half wave rectifier!

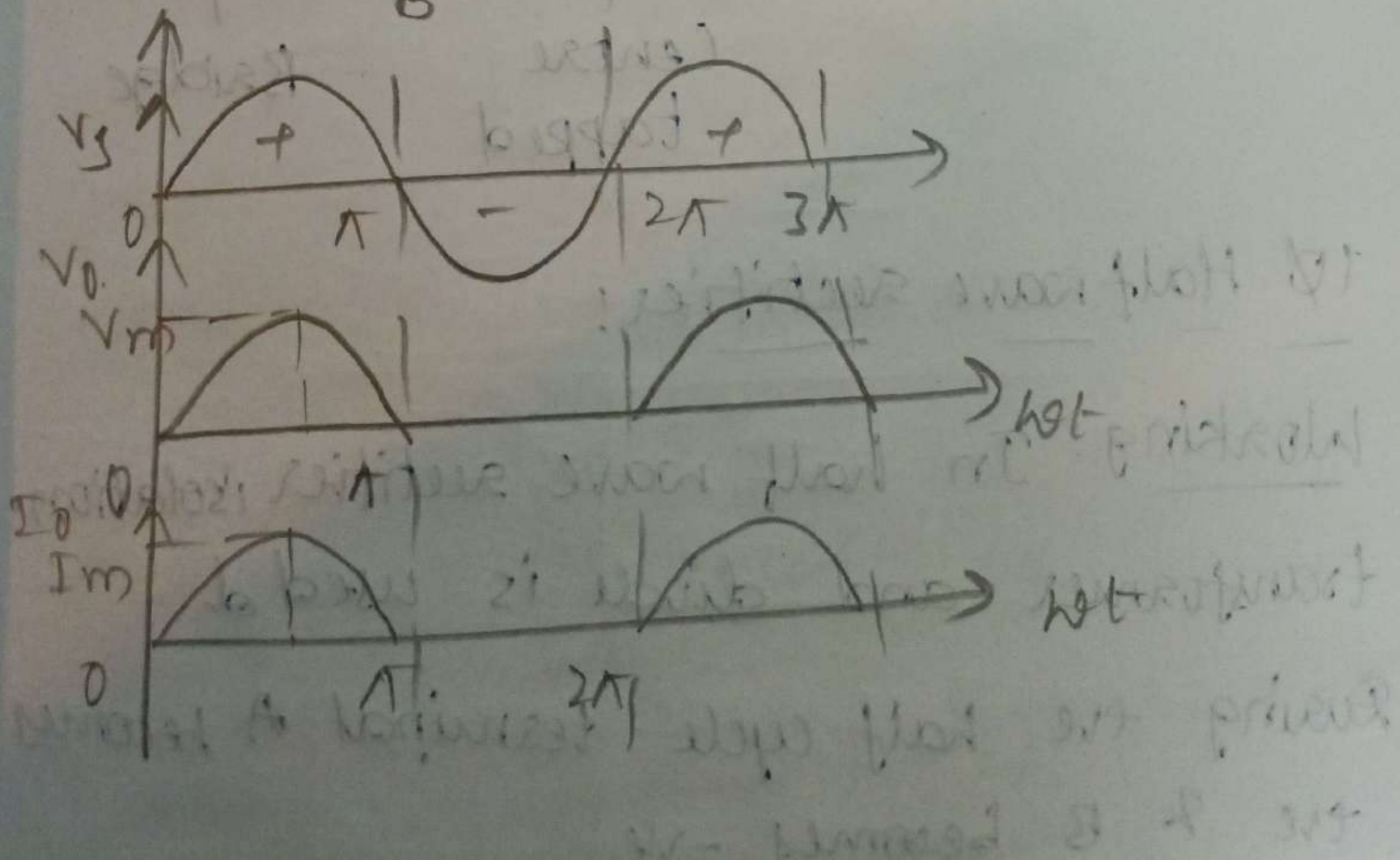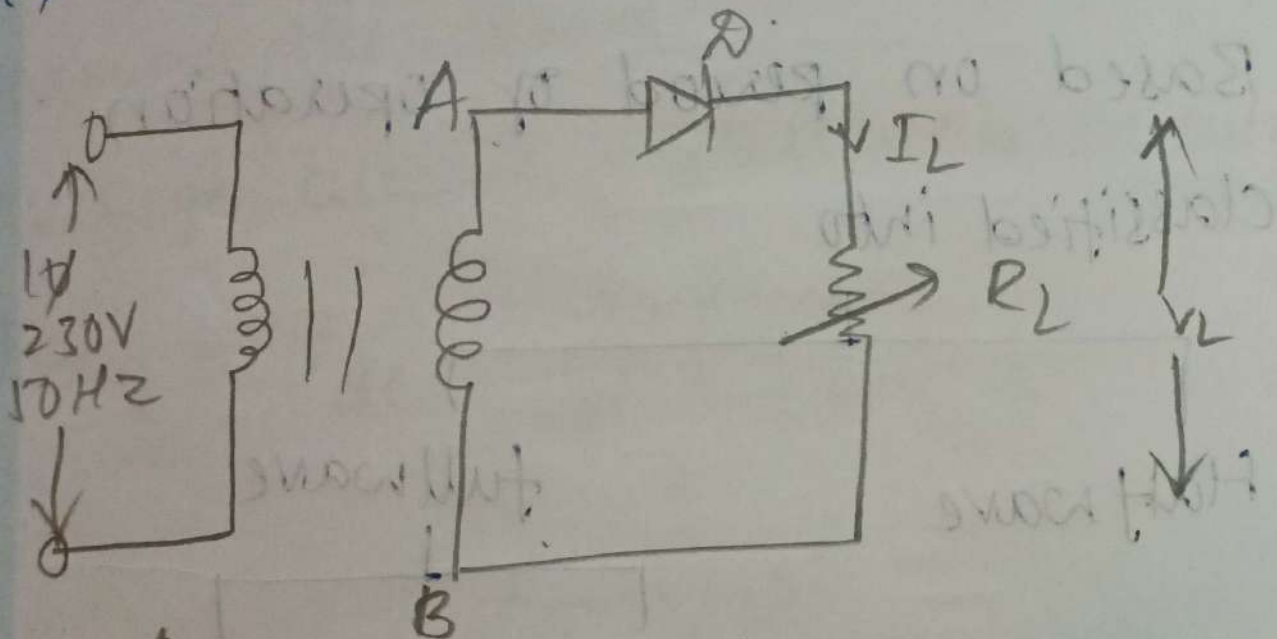


Rectifiers: Purpose of rectifiers:
It is an electronic device which converts fixed AC to variable DC.

Rectifiers are classified into two types:

1) Based on no of ~~for~~ phases 1ϕ , 3ϕ

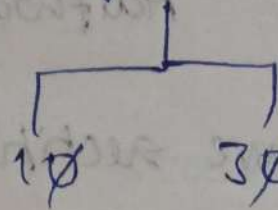

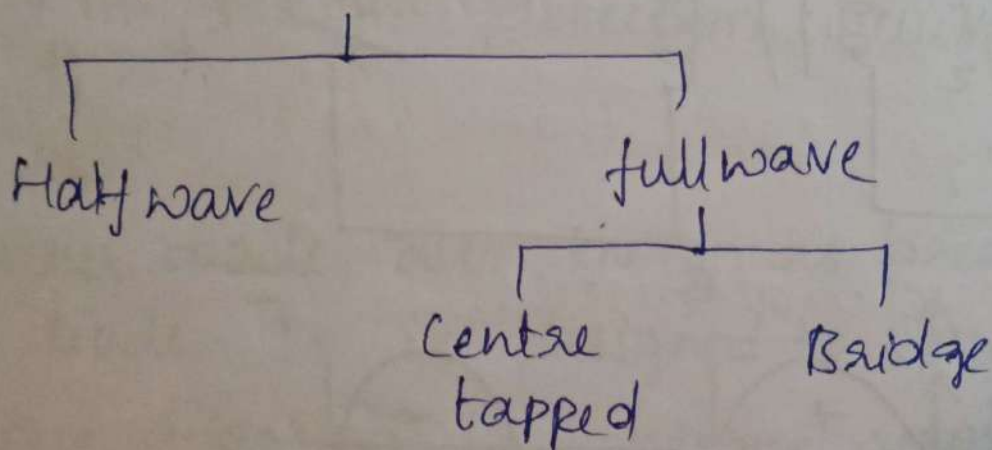2) Based on period of operation
classified into



1ϕ Half wave rectifier:

Working: In half wave rectifier isolation transformer and diode is used.

During the half cycle terminal A becomes +ve & B becomes -ve

Now diode is under forward biased mode and now current flows from anode to cathode and then to load.

During -ve half cycle terminal A becomes -ve & B becomes +ve due to this diode comes into reverse biased mode. Due to which it does not allow the current flow through the load.

Average current expression (or) DC output current:

$$I_{oavg} = I_{dc} = \frac{1}{T} \int_0^T I(\omega t) d\omega t$$

$$I = I_m \sin \omega t$$
$$= \frac{1}{2\pi} \int_0^\pi I_m \sin \omega t d\omega t$$

$$= \frac{I_m}{2\pi} \int_0^\pi \sin \omega t d\omega t$$

$$= \frac{I_m}{2\pi} (-\cos \omega t)_0^\pi$$

$$= \frac{I_m}{2\pi} (-(-1) + 1)$$

$$= \frac{2I_m}{2\pi} = \frac{I_m}{\pi}$$

$$I_{dc} = I_{oav} = \frac{I_m}{\pi}$$

Average Voltage Expression (or) Output dc voltage:

$$V_{oav} = V_{dc} = I_{dc} R_L$$

$$= \frac{I_m}{\pi} R_L \quad \left[\because I_m = \frac{V_m}{R_L} \right]$$

$$= \frac{V_m}{R_L \pi} R_L$$

$$V_{oav} = \frac{V_m}{\pi}$$

output power expression:

$$P_{dc} = I_{dc}^2 R_L$$

$$= \frac{I_m^2}{\pi^2} R_L$$

$$= \frac{V_m^2}{R_L \pi^2} R_L$$

$$P_{dc} = \frac{V_m^2}{R_L \pi^2}$$

Rms value of output current:

$$I_{\text{orms}} = I_{\text{ac}} = \left\{ \frac{1}{T} \int_0^T I^2(\omega t) d\omega t \right\}^{1/2}$$

$$I = I_m \sin \omega t$$

$$= \left\{ \frac{1}{2\pi} \int_0^{2\pi} I_m^2 \sin^2 \omega t d\omega t \right\}^{1/2}$$

$$= \left\{ \frac{I_m^2}{2\pi} \int_0^{2\pi} \left(\frac{1 - \cos 2\omega t}{2} \right) d\omega t \right\}^{1/2}$$

$$= \left\{ \frac{I_m^2}{4\pi} \left[(\omega t)_0^{2\pi} - \left(\frac{\sin 2\omega t}{2} \right)_0^{2\pi} \right] \right\}^{1/2}$$

$$= \left\{ \frac{I_m^2}{4\pi} \left[\pi - 0 - \frac{1}{2} (\sin 2\pi - \sin 0) \right] \right\}^{1/2}$$

$$= \left\{ \frac{I_m^2}{4} \right\}^{1/2}$$

$$\boxed{I_{\text{orms}} = \frac{I_m}{2} = I_{\text{ac}}}$$

$$V_{\text{orms}} = V_{\text{ac}} = I_{\text{ac}} R_L = \frac{I_m R_L}{2}$$

$$= \frac{V_m}{2 R_L} R_L$$

$$\boxed{V_{\text{orms}} = V_{\text{ac}} = \frac{V_m}{2}}$$

$$P_{ac} = I_{ac}^2 R_L$$

$$= \frac{I_m^2}{4} R_L$$

$$= \frac{V_m^2}{4 R_L} R_L$$

$$P_{ac} = \frac{V_m^2}{4 R_L}$$



$$\eta = \frac{P_{ac}}{P_{dc}} = \frac{\frac{V_m^2}{4 R_L}}{\frac{V_m^2}{R_L}} = \frac{1}{4} = 25\%$$

$$P.T. V = V_m$$

$$\text{ripple factor} = \sqrt{\left(\frac{I_{rms}}{I_{avg}}\right)^2 - 1}$$

$$\text{ripple factor} = 1.21$$


full wave centre tapped rectifier:

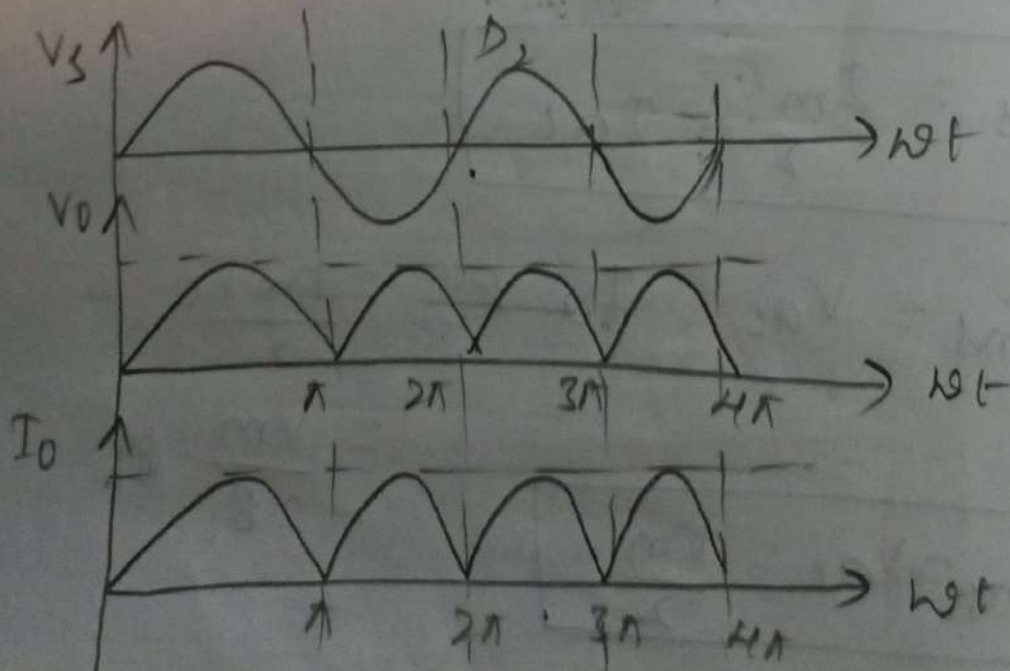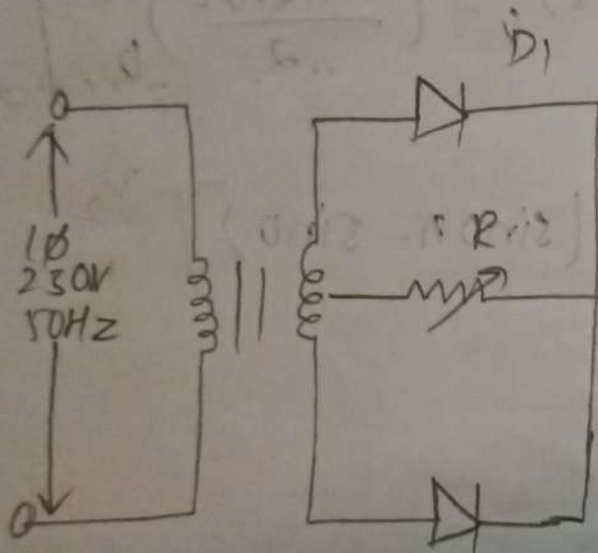

Circuit consisting of two diodes D_1 & D_2
 Circuit will be operated during both
 +ve half cycle as well as -ve half cycle

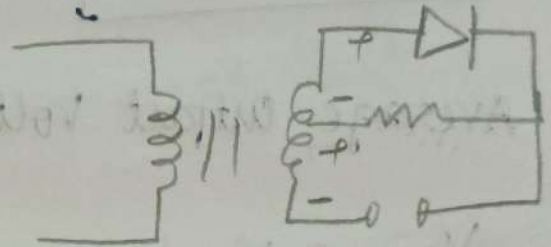
(i) Positive Halfcycle:

During +ve halfcycle diode D_1 gets forward
 biased and D_2 will be open circuited since
 it is reverse biased and now current
 flows through D_1 & then to load. And
 D_2 acts as open switch. since it is
 reverse biased.



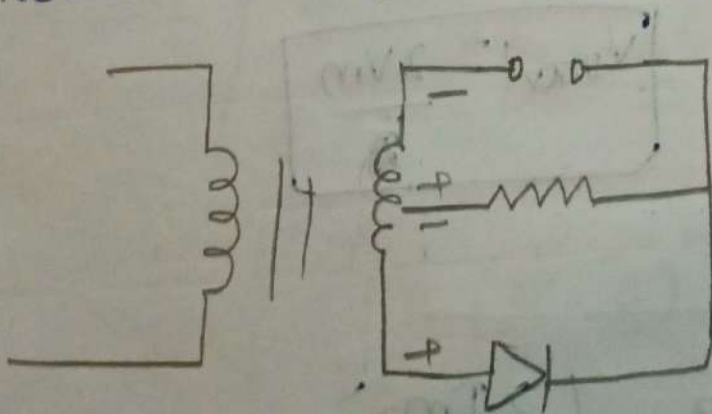(ii) Negative halfcycle:

During -ve halfcycle diode D_2 conducts current
 through the load & D_1 remains open
 circuited since it is reverse biased.



Avg output current expression:

$$I_{Oav} = I_{dc} = \frac{1}{T} \int_0^T I_m \sin \omega t d\omega t$$

$$= \frac{1}{\pi} \int_0^{\pi} I_m \sin \omega t \, dt$$

$$= \frac{1}{\pi} I_m \int_0^{\pi} \sin \omega t \, dt$$

$$= \frac{1}{\pi} I_m (-\cos \omega t) \Big|_0^{\pi}$$

$$= \frac{1}{\pi} I_m (2)$$

$$\boxed{I_{dc} = \frac{2I_m}{\pi}}$$

AC

I

Average output voltage (V_{oav}):

$$V_{oav} = V_{dc} = I_{dc} R_L = \frac{2I_m}{\pi} R_L$$

$$= \frac{2V_m}{\pi R_L} R_L$$

$$\boxed{V_{oav} = \frac{2V_m}{\pi}}$$

Output Power

$$P_{dc} = I_{dc}^2 R_L = \left(\frac{2I_m}{\pi} \right)^2 R_L$$

$$= \frac{4I_m^2}{\pi^2} R_L$$

$$= \frac{4V_m^2}{\pi^2 R_L} \times R_L$$

$$P_{dc} = \frac{4V_m^2}{\pi^2 R_L}$$

AC component (or) I_{rms} (or) I_{ac} :

$$I_{rms} = I_{ac} = \left\{ \frac{1}{T} \int_0^T I_m^2 \sin^2 \omega t \, d\omega t \right\}^{1/2}$$

$$= \left\{ \frac{1}{\pi} \int_0^{\pi} I_m^2 \sin^2 \omega t \, d\omega t \right\}^{1/2}$$

$$= \left[\frac{I_m^2}{\pi} \int_0^{\pi} \left(\frac{1 - \cos 2\omega t}{2} \right) d\omega t \right]^{1/2}$$

$$= \left[\frac{I_m^2}{2\pi} \left((\omega t)_0^{\pi} - \left(\frac{\sin 2\omega t}{2} \right)_0^{\pi} \right) \right]^{1/2}$$

$$= \left[\frac{I_m^2}{2\pi} (\pi - 0) \right]^{1/2}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}} = I_{ac}$$

$$V_{o\text{rms}} = V_{aL} = I_{aL} R_L$$

$$= \frac{I_m}{\sqrt{2}} R_L$$

$$= \frac{V_m}{\sqrt{2} R_L} R_L$$

$$V_{o\text{rms}} = V_{aL} = \frac{V_m}{\sqrt{2}}$$

$$P_{aL} = I_{aL}^2 R_L = \frac{I_m^2}{2} R_L = \frac{V_m^2}{2 R_L}$$

$$P_{aL} = \frac{V_m^2}{2 R_L}$$

$$\eta = \frac{P_{dc}}{P_{aL}} = \frac{4 V_m^2}{\pi^2 R_L} \div \frac{V_m^2}{2 R_L} = \frac{8}{\pi^2} = 81.05\%$$

$$\eta = 81.05\%$$

$$PIV = 2V_m$$

$$\text{ripple factor} = \sqrt{\left(\frac{\text{rms}}{\text{avg}}\right)^2 - 1}$$

Ripple
The u
output
Peak
It
diode
know

full



Ripple factor:
The unwanted AC component present in desired output is known as ripple factor.

Peak inverse voltage:


It is the maximum reverse voltage that diode can withstand without damage is known as Peak Inverse Voltage (PIV)

$$PIV = 2V_m$$

full wave Bridge rectifier:

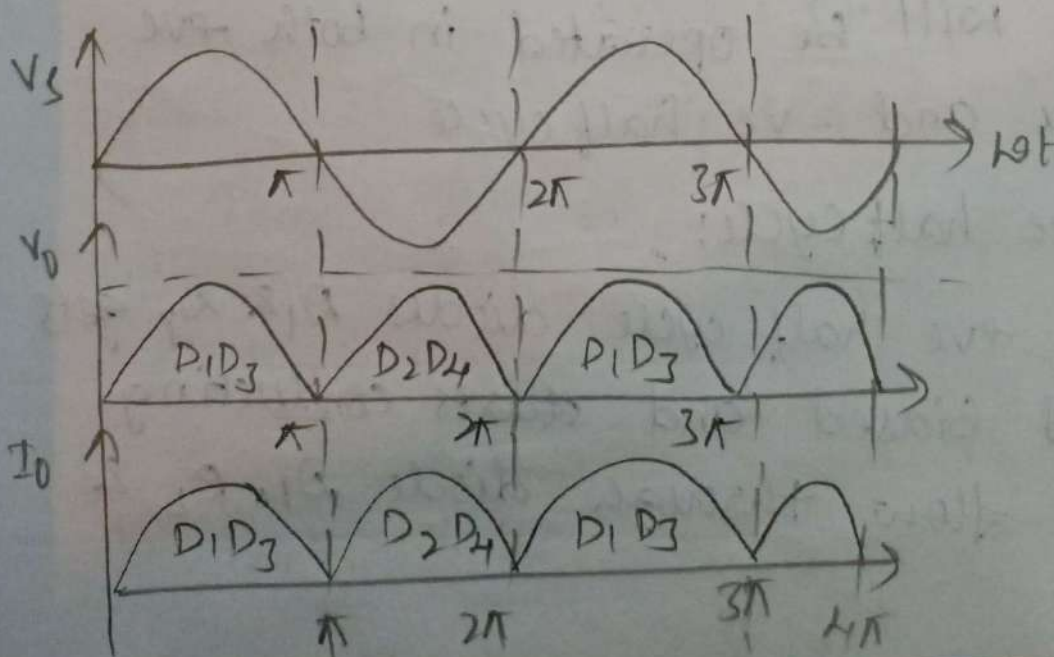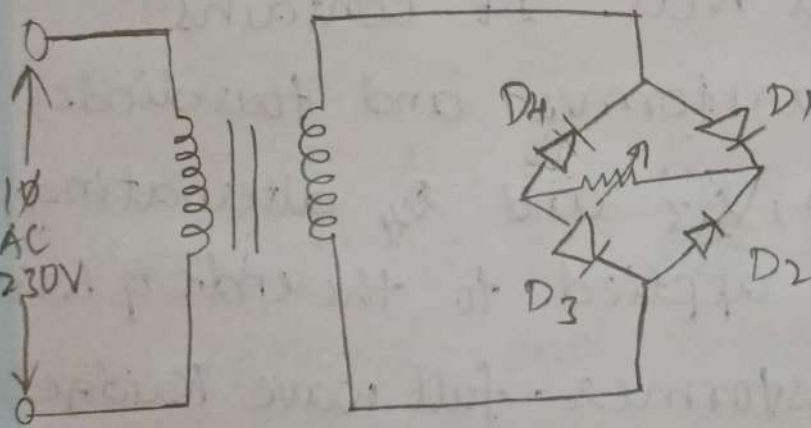

Case i) -ve

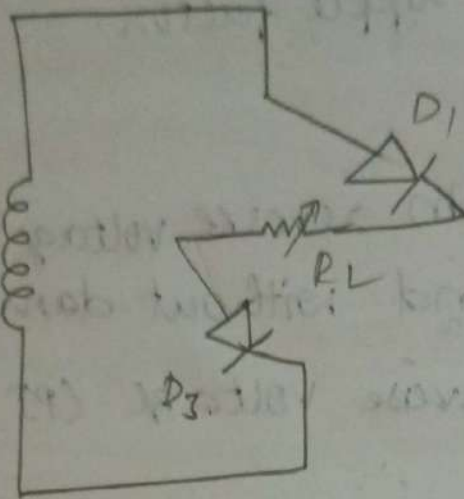


The full wave operation can be operation can be obtained without the bridge connection as well. It contains isolation transformer and four diodes that is D_1 , D_2 , D_3 and D_4 alternating voltage is applied to the ends of bridge through transformer. full wave Bridge rectifier will be operated in both +ve half cycle and -ve half cycle

(i) Positive half cycle:

During +ve half cycle diodes D_1 & D_3 gets forward biased and starts conducting current flow through diode D_1 , R_L & D_3 .

Whereas D_2 & D_4 are reverse biased there by open circuited.

Case(ii) Negative half cycle:

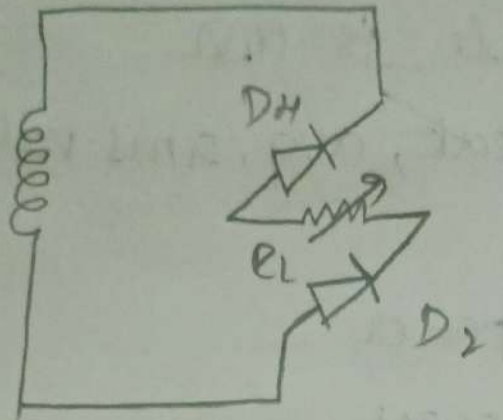

During -ve half cycle diodes D_2 & D_4 gets forward biased and there by it starts conducting current through load from diode D_2 , R_L , D_4

Whereas diode D_1 & D_3 remains reverse biased and there by open circuited.

$$V_{oav} = \frac{2 V_m}{\pi}$$

$$\eta = 81.05\%$$

$$I_{oav} = \frac{2 I_m}{\pi}$$

$$\text{ripple factor} = \sqrt{\left(\frac{V_{rms}}{V_{avg}}\right)^2 - 1}$$

$$P_{ac} = \frac{V_m^2}{2 R_L}$$

$$P_{IV} = V_m$$

$$V_{orms} = \frac{V_m}{\sqrt{2}}$$

$$P_{dc} = \frac{4 V_m^2}{\pi^2 R_L}$$

$$I_{orms} = \frac{I_m}{\sqrt{2}}$$

Q) A sinusoidal voltage of peak amplitude of 20 volts is applied to a half wave rectifier using P-n junction diode the load resistance is 1000Ω . The forward resistance of diode is 10Ω . Calculate (i) Peak, avg, rms values of load current.

(ii) DC output power

(iii) AC input power.

(iv) rectifier efficiency.

(v) PIV.

$$V_m = 20V, R_L = 1000\Omega, R_f = 10\Omega$$

$$I_m = \frac{V_m}{R_L + R_f} = \frac{20}{1000 + 10} = 0.0198$$

$$I_{rms} = \frac{I_m}{\sqrt{2}} = \frac{0.0198}{\sqrt{2}} = 9.5 \times 10^{-3}$$

$$I_{dc} = \frac{I_m}{\pi} = \frac{0.0198}{3.14} = 6.050 \times 10^{-3}$$

$$P_{dc} = (I_{dc})^2 (R_L + R_f)$$

$$= (6.050 \times 10^{-3})^2 (1010)$$

$$= 0.0369 \text{ W}$$

$$P_{ac} = (I_{ac})^2 (R_L + R_f)$$

$$= (9.5 \times 10^{-3})^2 (1000 + 10)$$

$$= 0.091 \text{ W}$$

$$\% \eta = \frac{P_{dc}}{P_{ac}} \times 100 = \frac{0.0369}{0.091} \times 100$$

$$= 40.6\%$$

$$PIV = V_m = 20V$$

- Q) A full wave rectifier uses load resistor of $1200\ \Omega$ a forward resistance of diode is $8\ \Omega$ sine wave of peak voltage is 30V applied to each diode calculate
- Max, DC, rms load currents.
 - DC output power
 - AC input power
 - Rectifier efficiency

$$R_L = 1200\ \Omega \quad R_f = 8\ \Omega$$

$$V_m = 30\text{V}$$

$$I_{dc} = \frac{2 I_m}{\pi}$$

$$I_{dc} = \frac{2 (0.0248)}{3.14}$$

$$= 0.0157$$

$$I_{rms} = \frac{I_m}{\sqrt{2}} = 0.0175\text{A}$$

$$I_{max} = \frac{V_{max}}{R_L + R_f}$$

$$= \frac{30}{1200 + 8}$$

$$= \frac{30}{1208}$$

$$I_{max} = 0.0248\text{A}$$

$$P_{dc} = (I_{dc})^2 (R_L + R_f)$$

$$= (0.0157)^2 (1208)$$

$$P_{dc} = 0.2977 \text{ W}$$

$$P_{ac} = (I_{ac})^2 (R_L + R_f)$$

$$= (0.0175)^2 (1208)$$

$$P_{ac} = 0.36995 \text{ W}$$

$$\eta = \frac{P_{dc}}{P_{ac}} \times 100$$

$$= \frac{0.2977}{0.36995} \times 100$$

$$= 80.4\%$$

Q) A sinusoidal peak voltage is 14.4 V which is applied to half wave rectifier with the load of 1000Ω & it has forward resistance of 10Ω determine (i) Peak, Rms, Avg values of current (ii) Dc & Ac power (iii) η of HWR

$$V_m = 14.4\text{ V} \quad R_L = 1000\Omega \quad R_f = 10\Omega$$

(iv) Ripple factor.

(i) Peak current.

$$I_m = \frac{V_m}{R_L + R_f} = \frac{14.4}{1010} = 0.0142\text{ A}$$

$$I_{rms} = \frac{I_m}{2} = 0.0071 = 7.1 \times 10^{-3}$$

$$I_{avg} = \frac{I_m}{\pi} = \frac{0.0142}{3.14} = 4.522 \times 10^{-3}$$

$$I_{dc} = 4.522 \times 10^{-3}$$

$$P_{dc} = I_{dc}^2 (R_L + R_f)$$

$$= 4.522 \times 10^{-3} \times 4.522 \times 10^{-3} (1010) = 0.0206\text{ W}$$

$$P_{ac} = (7.1 \times 10^{-3})^2 (1010)$$

$$= 0.0509 \Rightarrow \eta = \frac{0.0206}{0.0509} \times 100$$

$$\eta = 40.4$$

$$\text{Ripple factor} = \sqrt{\left(\frac{I_{rms}}{I_{avg}}\right)^2 - 1}$$

$$= \sqrt{\left(\frac{0.004}{0.0044}\right)^2 - 1}$$

$$\text{Ripple factor} = 1.21 = \sqrt{\left(\frac{7.1 \times 10^{-3}}{4.522 \times 10^{-3}}\right)^2 - 1}$$

- Q) A pure sinusoidal maximum voltage is 15.4V which is applied to a full wave rectifier with the load of $1.2 \text{ k}\Omega$ & it has forward resistance of 14Ω determine
- (i) max, rms, avg values of current.
 - (ii) DC & AC power.
 - (iii) η of FWR.

$$V_m = 15.4V, \quad R_L = 1.2 \times 10^3 = \frac{12}{10} \times 10^3$$

$$R_f = 14 \Omega \quad = 1200$$

$$I_m = \frac{V_m}{R_L + R_f} = \frac{15.4}{1214} = 0.0126$$

$$I_{dc} = \frac{2I_m}{\pi} = \frac{2 \times 0.0126}{3.14}$$

$$= 8.025 \times 10^{-3} A$$

$$I_{ac} = \frac{I_m}{\sqrt{2}} = 8.909 \times 10^{-3}$$

$$P_{dc} = I_{dc} (R_L + R_f)$$

$$= (8.025 \times 10^{-3}) (1214)$$

$$= 0.078 AW$$

$$P_{ac} = I_{ac}^2 (1214)$$

$$= 0.0963 W$$

$$\eta = \frac{0.078}{0.096} = 0.812 \times 100$$

$$= 81.2 \%$$

$$\text{ripple factor} = \sqrt{\left(\frac{8.909 \times 10^{-3}}{8.025 \times 10^{-3}} \right)^2 - 1}$$

$$= 0.48$$


8) An ac supply of 230V is applied to a half wave rectifier through a transformer find.

V_{DC} , η , PIV.

(i) DC output voltage.

(ii) Efficiency.

(iii) Peak inverse voltage.

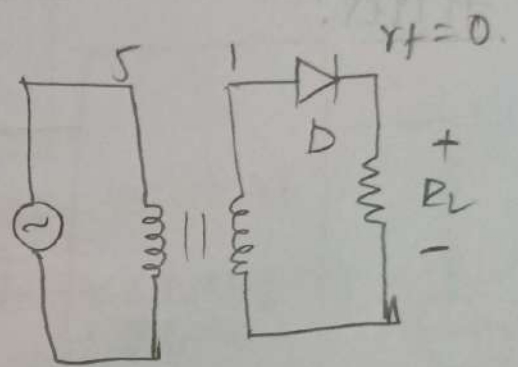

$$1.110$$

$$\text{DC Output voltage} = \sqrt{2} V_{ac}$$

$$1.2321$$

$$= \sqrt{2} \times 230$$

$$= 325.267V$$

$$\text{DC output voltage} = 325.267V$$

$$r_m =$$

$$R_f = 0$$


$$\eta = \frac{P_{dc}}{P_{ac}} = \frac{I_{dc}^2 (R_L + R_f)}{I_{ac}^2 (R_L + R_f)} = \frac{I_{dc}^2 (R_L + 0)}{I_{ac}^2 (R_L + 0)}$$

$$\therefore = \frac{I_{dc} R_L}{I_{ac} R_L} = \frac{\left(\frac{I_m}{\pi}\right)^2 R_L}{\left(\frac{I_m}{2}\right)^2 R_L} = \frac{\frac{V_m}{\pi^2 R_L} R_L}{\frac{V_m}{4 R_L} R_L} = \frac{4}{\pi^2} = 40.6\%$$

(iv) PIV = V_m

$$k \Rightarrow \frac{V_2}{V_1} = \frac{N_2}{N_1} \Rightarrow V_2 = V_1 \times \frac{N_2}{N_1} \Rightarrow 325.26 \times \frac{1}{5} \\ V_2 = 65.05V$$

filter:

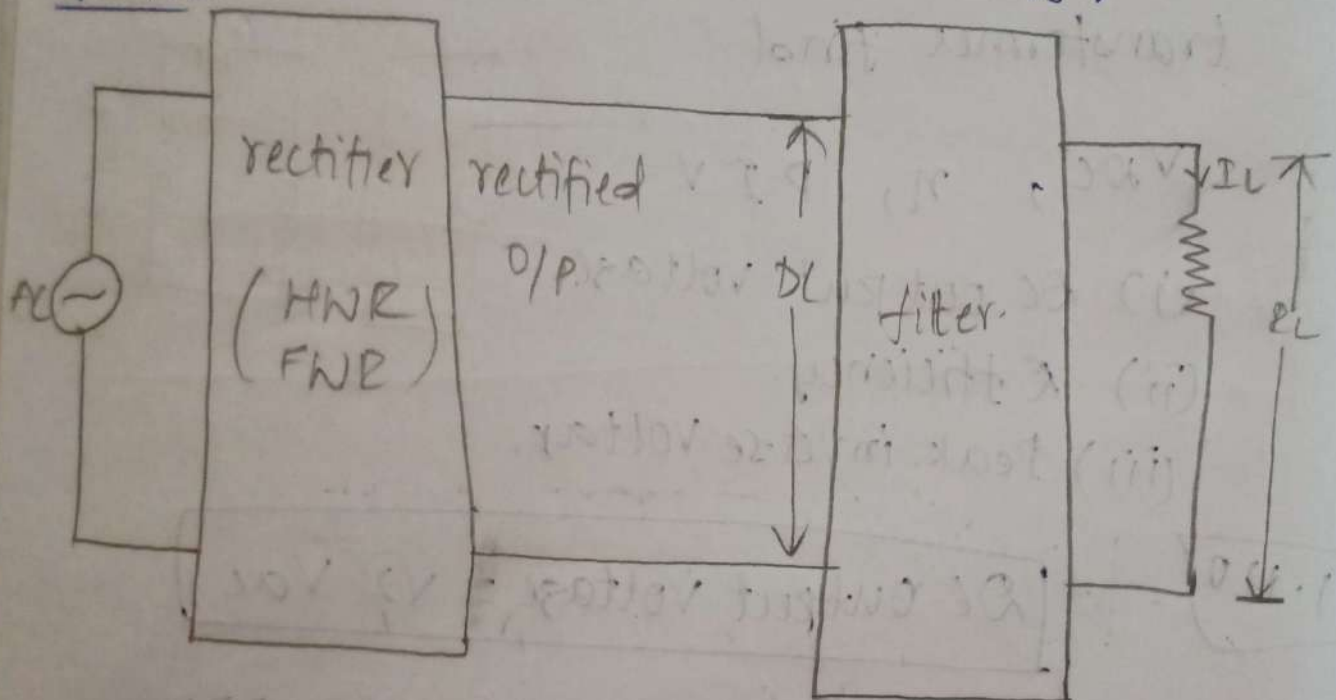


Filter is an electronic device which converts ripple content in rectifier output that is pulsating DC to pure DC it allows only DC component to reach the load. A filter circuit should be installed between rectifier & the load.

Filter circuit is classified into two types


- (i) Capacitor filter
- (ii) Inductor filter.

Capacitor filter: Blocks AC allows DC.

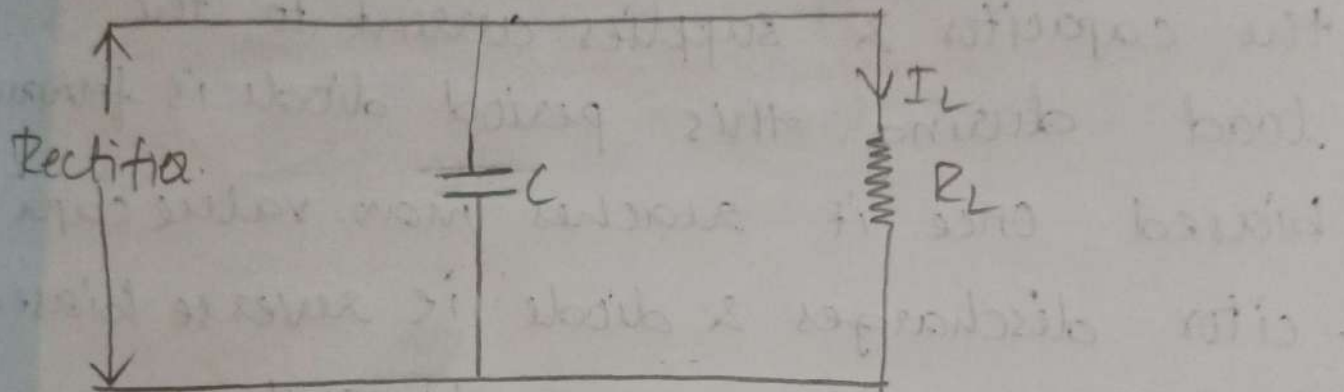


'D' \rightarrow f.B $\rightarrow V_2 > V_m \rightarrow$ 'C' \rightarrow charging

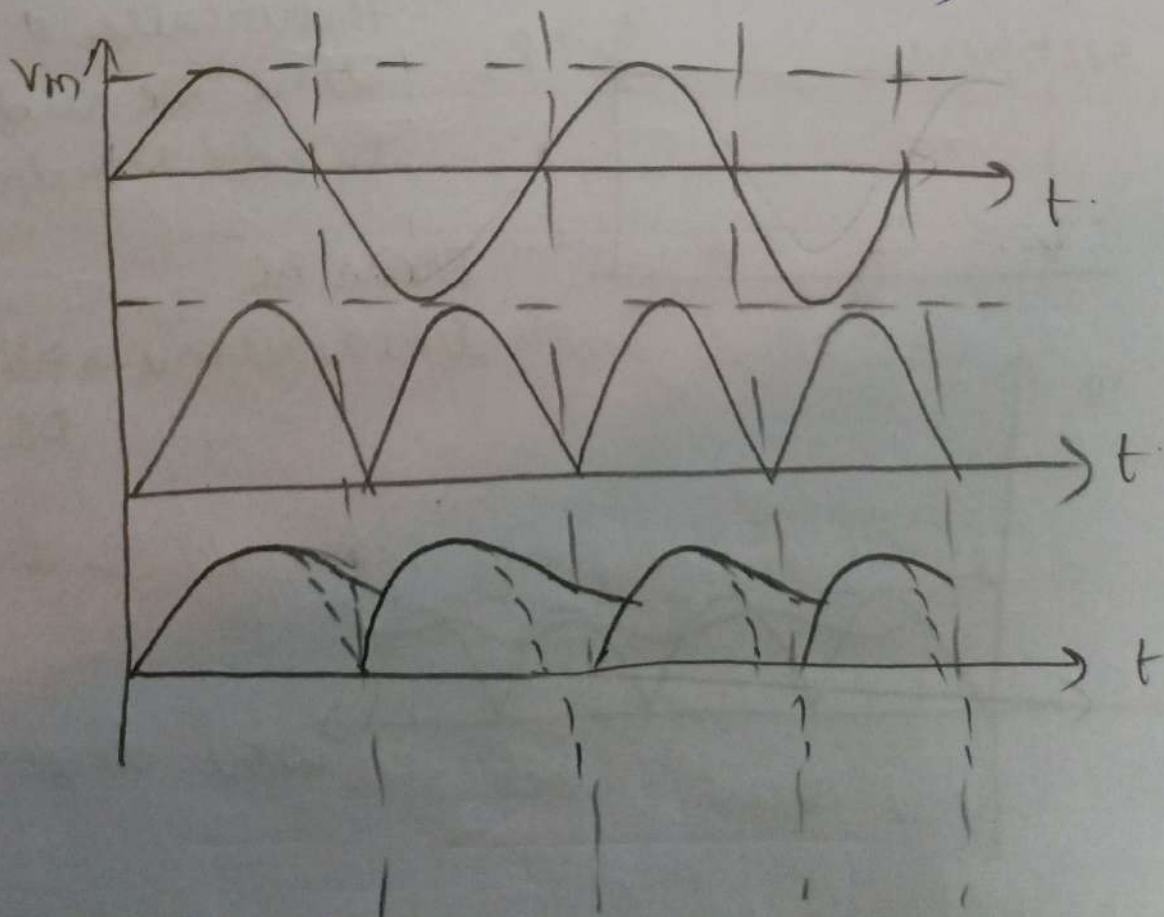'D' \rightarrow R.B $\rightarrow V_2 < V_m \rightarrow$ 'C' \rightarrow discharging




A capacitor filter consists of a capacitor placed across rectifier in parallel. With load resistance the voltage of rectifier applied across rectifier as the input voltage rises to maximum voltage (V_m) it charges the capacitor & supplies current to the load during this period diode is forward biased once it reaches max. value capacitor discharges & diode is reverse biased & this process repeats continuously.

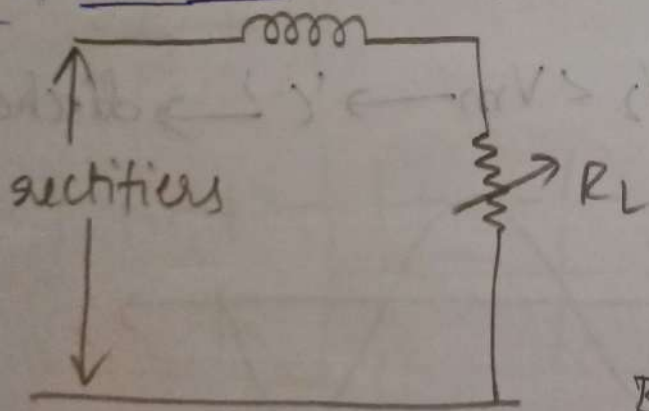Inductor filter (choke) \rightarrow high resistance \rightarrow Blocks AC



In order to get a theoretically st line we need to add regulator

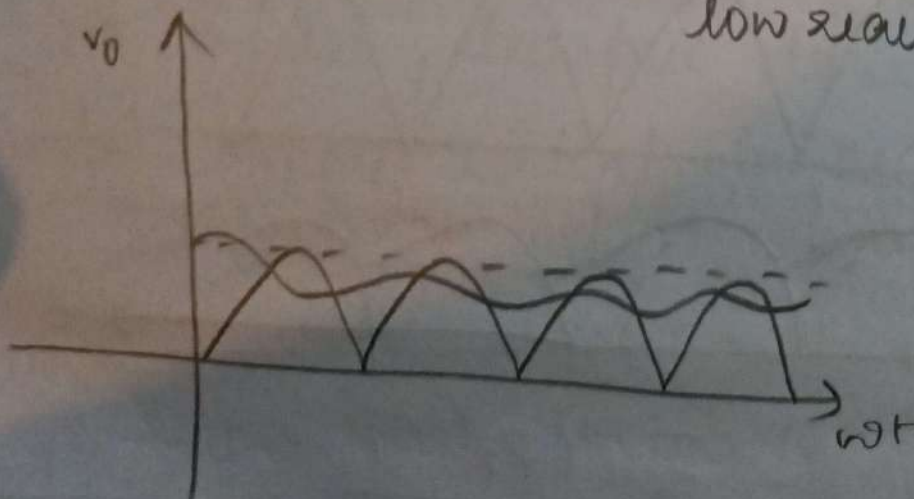Blocks AC
low reactance \rightarrow Allows DC.



Inductor filter also known as choke filter it consists of an inductor which is inserted b/w rectifier & load resistance. When the output current passes through inductor it offers high reactance to AC component & low reactance to DC component which while reaching to load resistor.


UNIT-V

Transistors


BJT:

Construction:

(i) NPN

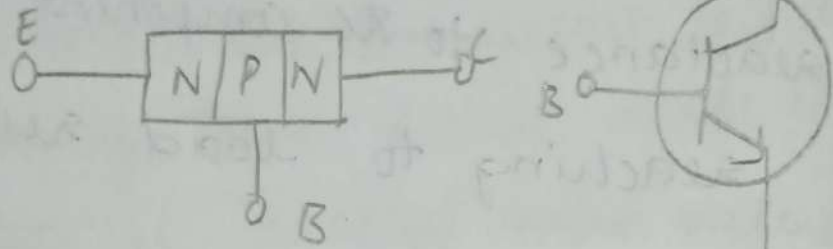

(ii) PNP

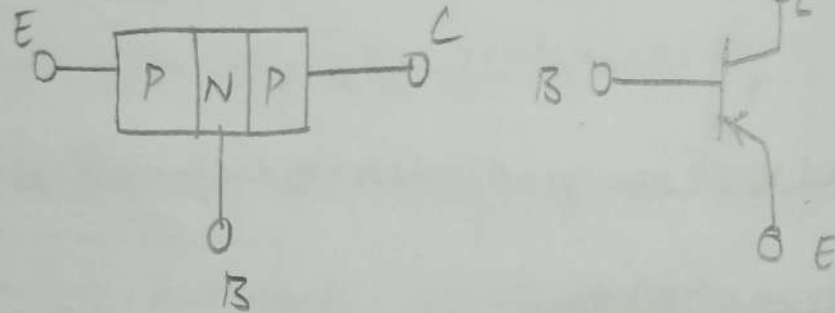

BJT:

Bipolar junction transistor (BJT).

Conduction of the current is due to both holes & electrons hence the name Bipolar device.

Purpose of transistor: it is used to strengthen a given weak signal.

Here Arrow mark indicates the direction of current.

Transistor has 3 different regions namely

- 1) Emitter
- 2) Base
- 3) Collector


1) Emitter: It is a highly doped region which emits or supplies majority charge carriers.

2) Collector: It is a moderately doped layer which accepts or collects charge carriers.

3) Base: It is a lightly doped layer located b/w emitter & collector due to narrow width it will not accept or emit charge carriers.

Working of Transistors:

(i) NPN Transistor:

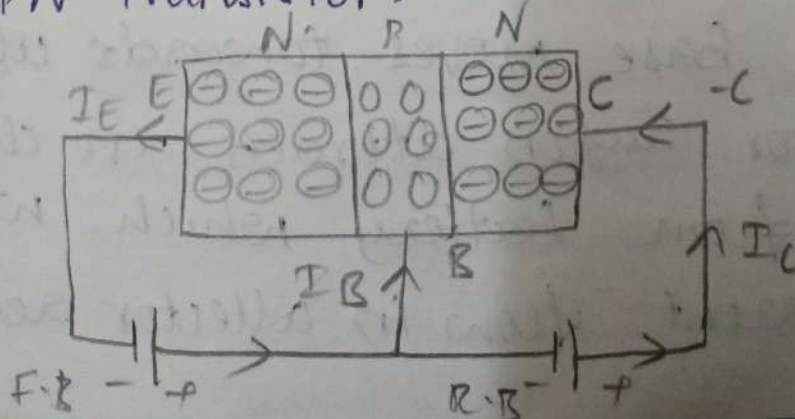

Emitter Base junction


In NPN transistor E-B Junction is forward biased & B-C Junction is reverse biased

In E-B Junction positive terminal is connected to base & -ve terminal connected to emitter making it F-B. & In B-C Junction +ve terminal connected to collector & -ve connected to base region making it reverse biased.

In forward biased mode of E-B junction electrons moves towards base region it will cause current flow in emitter. The electrons are recombined with holes in base causing current flow in base region.

Holes from base moves towards collector and collector region attracts +ve charge carriers from battery which will cause current flow in collector region.

(ii) PNP Transistor:

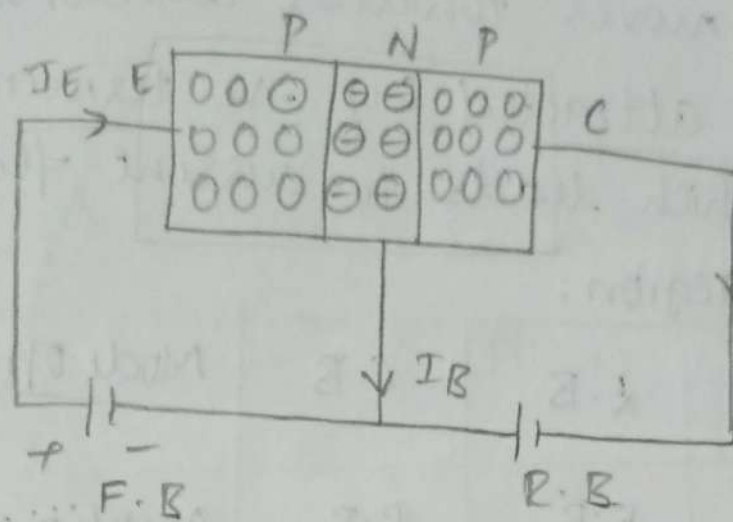

Emitter Base junction is forward biased
& B-C junction is reverse biased so that
transistor comes into active region

Positive terminal connected to emitter &
-ve terminal connected to base region.
Mk. making it forward biased & CB
junction +ve terminal connected to base
& -ve terminal connected to collector making
it reverse biased.

In forward biased mode of EB junction
holes moves towards base this
will cause current flow in emitter &
base region. Few electrons now gets
recombined with holes causing current
flow in base region.


Due to narrow width of base region, few electrons moves towards collector & also holes are attracted by -ve terminal of battery which leads to current flow in collector region.

Region	E-B	C-B	Mode of operation
Active region	F-B	R-B	Amplifier.
saturation	F-B	F-B	ON switch
Cut off	R-B	R-B	OFF switch


Types of configurations:

- (i) Common base
- (ii) Common emitter
- (iii) Common collector


(i) Common Base configuration

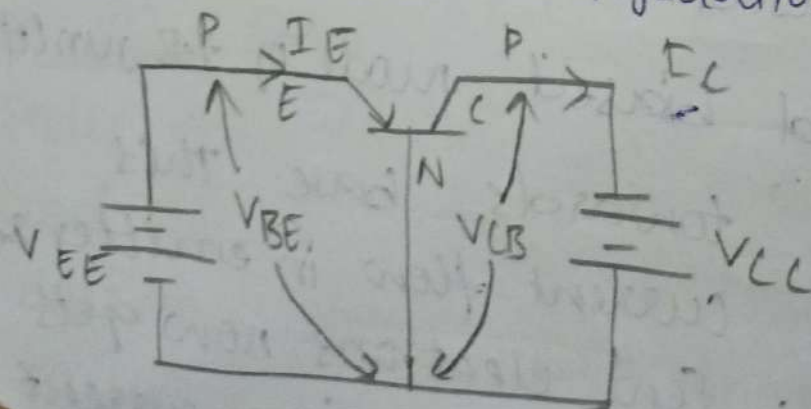

I/P characteristics:

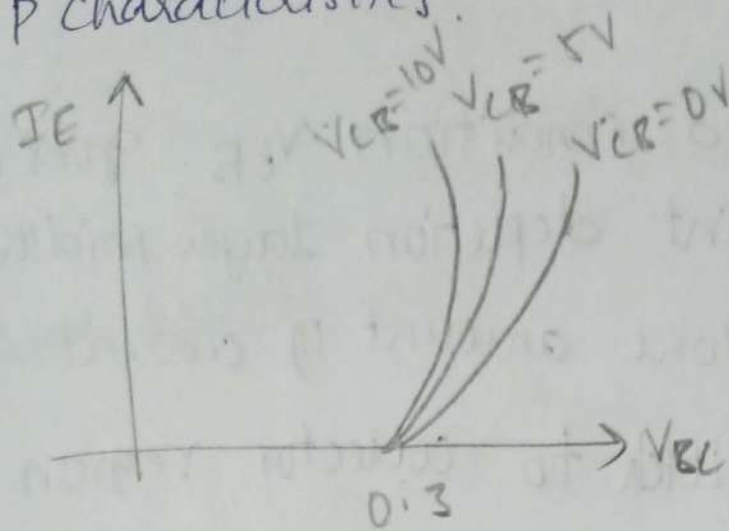

O/P characteristics

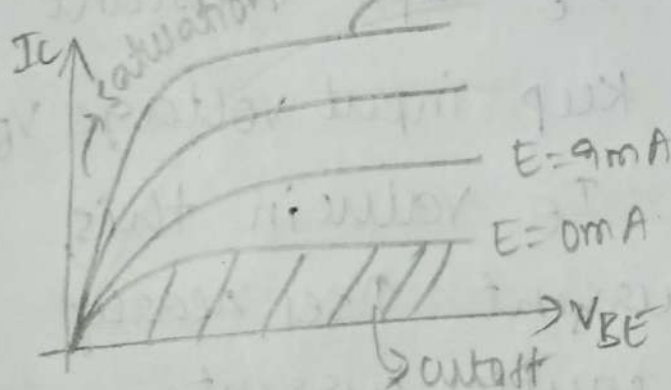

$$R_O = \frac{\Delta V_{BE}}{\Delta I_C}$$

In PNP transistor base terminal should be common between input and output known as CB configuration.

The input performance curve plot b/w I_E against V_{BE} at output voltage V_{CB} kept constant

In this mode emitter to base junction forward biased during graph between

I_E & V_{BE} output voltage kept constant & V_{CB} will be used in steps that is

0, 5V, 10V

In forward biased condition V_{EB} goes on rising at some point depletion layer width becomes zero. More amount of current flows from emitter to collector region.

→ Output characteristics graph plot b/w I_C (vs) V_{CB} where I_E kept constant

→ here, we need to keep input voltage V_{BE} constant then set I_E value in this process collector current rises nearly equal to that of emitter current.

	E.B	C.B
Saturation region	F.B	F.B
Active region	F.B	R.B
Cutoff region	R.B	R.B

current amplification factor :

$$\alpha = \frac{I_C}{I_E} \Rightarrow \frac{\Delta I_C}{\Delta I_E}$$

$$\boxed{I_C = \alpha I_E}$$


$$I_C = \alpha I_E + I_{CBO}$$

leakage current (A)


I_C units in μA

Common Emitter (CE):

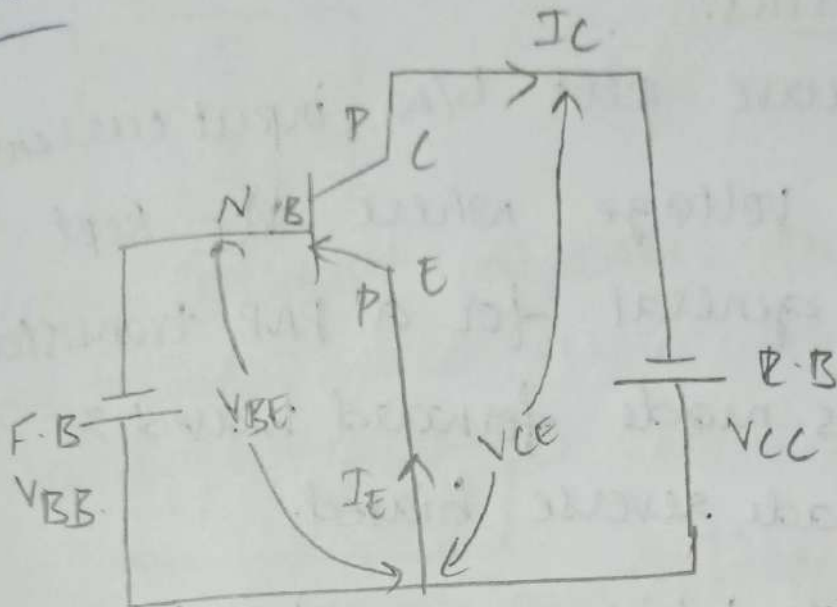leakage current is due to biasing provided.




Input characteristics:

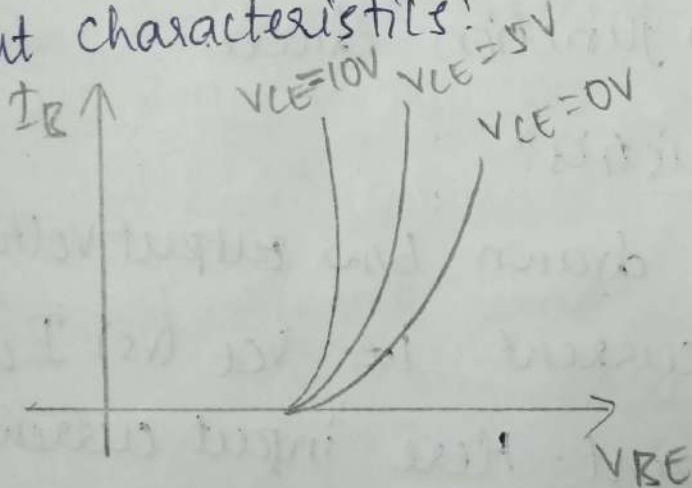

$$R_i = \frac{\Delta V_{BE}}{\Delta I_B}$$

Output characteristics:
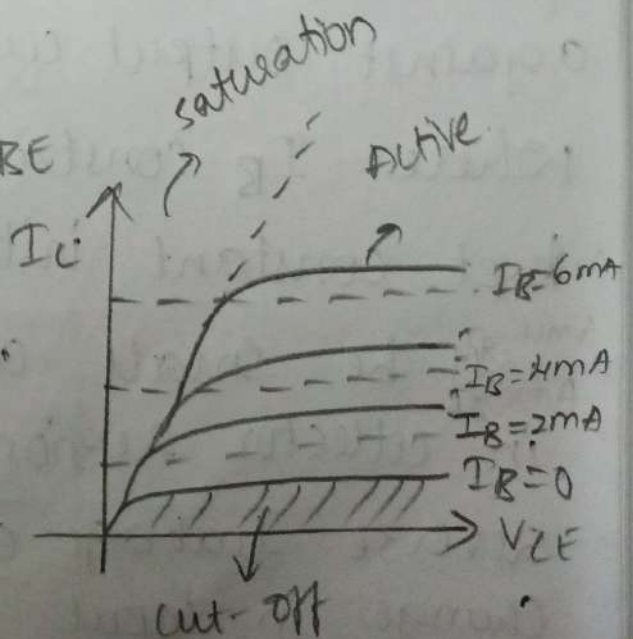
$$R_o = \frac{\Delta V_{CE}}{\Delta I_C}$$



In this PNP transistor emitter connected for both input & output known as CE configuration.

I/P characteristics:

Performance curve plot b/w input current against input voltage where V_{CE} kept constant in general for a PNP transistor EB junction is made forward biased & DC junction made reverse biased.

Input characteristics curve is similar to that of p-n junction diode.

Output characteristics:

Performance curve drawn b/w output voltage against output current i.e. V_{CE} (Vs) I_C where I_B constant. Here input current kept constant initially $I_B = 0$ there will be small amount of current flows in collector region i.e. I_{CBO} known as reverse leakage current for small change in input current there will be

large change in output current I_C
Base amplification factor:

It is defined as the ratio of change in collector current to base current

$$\beta = \frac{I_C}{I_B}$$


Collector current depends on base amplification factor

$$I_C = \beta I_B$$


Due to majority carriers there will be leakage current through device I_{CEO}

$$I_C = \beta I_B + I_{CEO}$$

common collector configuration:

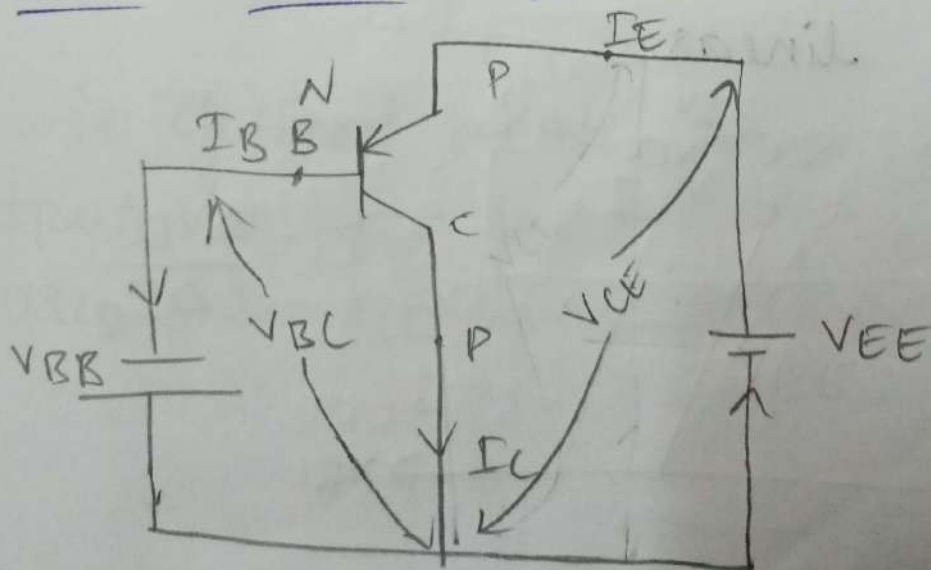


Input characteristics:

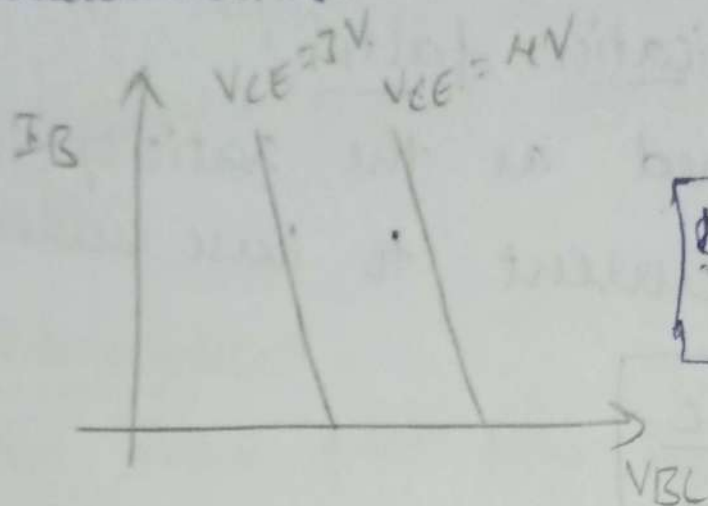

$$R_i = \frac{\Delta V_{BE}}{\Delta I_B}$$

In pnp transistor collector terminal is made common between both input & output known as cc configuration. Input characteristics

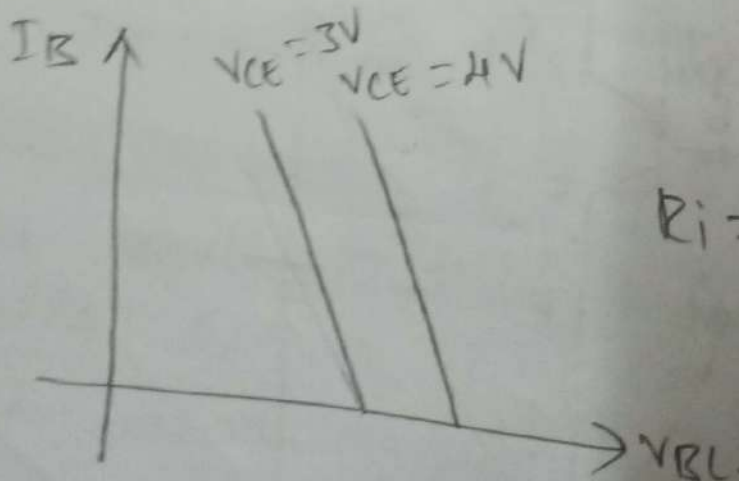Here performance curve is plot. & b/w input current I_B against input voltage V_{BE} keeping V_{CE} constant. And now for higher values V_{BE} the graph will be known linear



$$R_i = \frac{\Delta V_{BE}}{\Delta I_B}$$


output characteristics:

Performance curve - plot b/w output voltage V_{CE} against output current I_E keeping I_B constant. Here we need to keep V_{BC} constant and obtain input current I_B later it is also maintained constant and now output voltage V_{CE} is varied in steps so that for small change input current I_B there will be a large change in output current I_E and here the output characteristics will be same as that of CE configuration.

output resistance!

$$R_o = \frac{\Delta V_{CE}}{\Delta I_E}$$

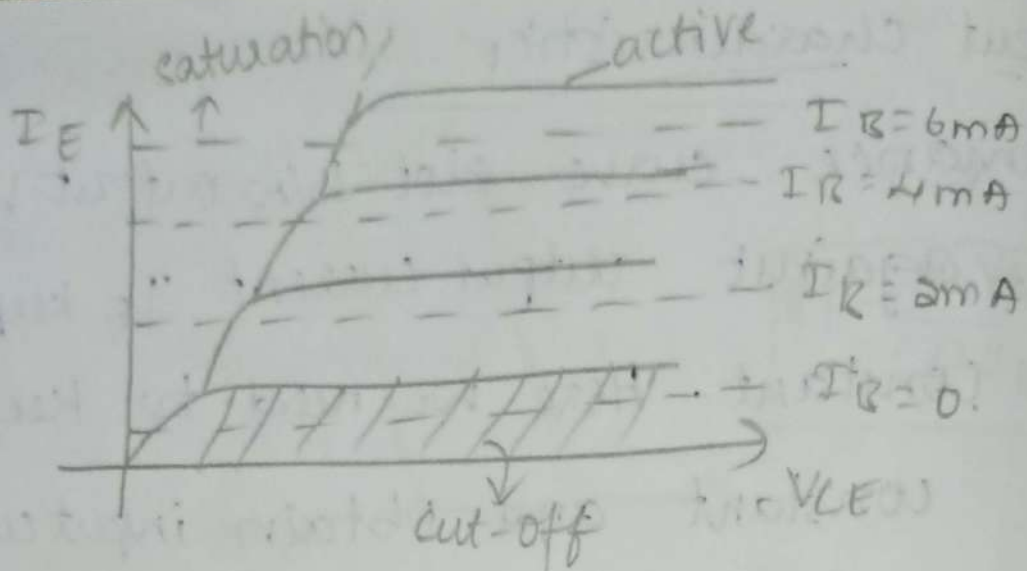It is defined as the ratio of change in output voltage V_{CE} to change in output current I_E keeping input current I_B constant.



Current amplification factor:

It is defined as the ratio of change in emitter current to change in base current known as current amplification factor.

In common base configuration the emitter

$$\gamma = \frac{I_E}{I_B} \Rightarrow \frac{\Delta I_E}{\Delta I_B}$$

$$I_E = \gamma I_B$$

$$I_E = \gamma I_B + I_{CEO}$$

Q) In common base configuration the emitter current I_E is 1mA & collector current I_C is 0.9mA calculate base current I_B ?

$$I_E = 1\text{mA}, \quad I_C = 0.9\text{mA}$$

$$I_E = I_B + I_C$$

$$1 = I_B + 0.9$$

$$\boxed{I_B = 0.1\text{mA}}$$

Q) In a common base configuration collector current is 0.95mA and the base current is 0.05mA calculate current amplification factor:

$$I_C = 0.95\text{mA}$$

$$I_B = 0.05\text{mA}$$

$$\alpha = \frac{I_C}{I_E}$$

$$\alpha = \frac{0.95}{1}$$

$$\boxed{\alpha = 0.95\text{mA}}$$

$$\begin{aligned} I_E &= I_B + I_C \\ &= 0.05 + 0.95 \\ &= 1\text{mA} \end{aligned}$$

Q) In a CB configuration the emitter current is 1 mA find collector current, when the value of α is 0.92

$$I_E = 1\text{ mA}$$

$$\alpha = 0.92$$

$$0.92 = \frac{I_C}{I_E}$$

$$I_C = 0.92\text{ mA}$$

Relation between α , β , γ :

(i) Relation between α , β :

$$\alpha = \frac{I_C}{I_E} \quad \text{--- (1)} \quad \beta = \frac{I_C}{I_B} \quad \text{--- (2)}$$

$$\Delta I_E = \Delta I_C + \Delta I_B$$

$$\Delta I_B = \Delta I_E - \Delta I_C \quad \text{--- (3)}$$

$$\beta = \frac{\Delta I_C}{\Delta I_B} = \frac{\Delta I_C}{\Delta I_E - \Delta I_C}$$

$$\beta = \frac{\frac{\Delta I_C}{\Delta I_E}}{\frac{\Delta I_E}{\Delta I_E} - \frac{\Delta I_C}{\Delta I_E}} = \frac{\alpha}{1 - \alpha}$$

$$\boxed{\beta = \frac{\alpha}{1-\alpha}}$$

$$\beta(1-\alpha) = \alpha$$

$$\alpha = \beta - \beta\alpha$$

$$\alpha + \beta\alpha = \beta$$

$$\beta = \alpha(1+\beta)$$

$$\boxed{\alpha = \frac{\beta}{1+\beta}}$$

Relation between α, β, γ :

(i) Relation between β, γ :

$$\beta = \frac{I_C}{I_B}, \quad \gamma = \frac{I_E}{I_B}$$

$$\Delta I_E = \Delta I_B + \Delta I_C$$

Dividing above equation with I_B , we get

$$\frac{\Delta I_E}{\Delta I_B} = \frac{\Delta I_B}{\Delta I_B} + \frac{\Delta I_C}{\Delta I_B}$$

$$\boxed{\gamma = 1 + \beta}$$

$$\boxed{\beta = \gamma - 1}$$

Relation b/w γ, α :

$$\gamma = \frac{I_E}{I_B}, \quad \alpha = \frac{I_C}{I_E}$$

$$\Delta I_E = \Delta I_B + \Delta I_C$$

$$\Delta I_B = \Delta I_E - \Delta I_C$$

$$\gamma = \frac{\Delta I_E}{\Delta I_E - \Delta I_C}$$

$$\Delta I_E - \Delta I_C$$

$$\gamma = \frac{\Delta I_E}{\Delta I_E - \Delta I_C}$$

$$\frac{\Delta I_E}{\Delta I_E} - \frac{\Delta I_C}{\Delta I_E}$$

$$\boxed{\gamma = \frac{1}{1 - \alpha}}$$

$$\gamma(1 - \alpha) = 1$$

$$1 - \alpha = \frac{1}{\gamma}$$

$$\alpha = 1 - \frac{1}{\beta}$$

$$\boxed{\alpha = \frac{\beta - 1}{\beta}}$$

Expression for CB configuration:-
from CB configuration

$$I_C = \alpha I_E + I_{CBO}$$

$$\boxed{I_C = \left(\frac{\beta}{1 + \beta} \right) I_E + I_{CBO}}$$

Expression for CE configuration:-
from CB configuration

$$I_C = \alpha I_E + I_{CBO}$$

$$I_E = I_B + I_C$$

$$I_C = \alpha (I_B + I_C) + I_{CBO}$$

$$I_C = \alpha I_B + \alpha I_C + I_{CBO}$$

$$I_C - \alpha I_C = \alpha I_B + I_{CBO}$$

$$I_C(1-\alpha) = \alpha I_B + I_{CBO}$$

$$I_C = \left(\frac{\alpha}{1-\alpha} \right) I_B + \left(\frac{1}{1-\alpha} \right) I_{CBO}$$

$$I_C = \beta I_B + \beta I_{CBO}$$

Expansion of CC configuration:
from CB configuration

$$I_C = \alpha I_E + I_{CBO}$$

$$I_E = I_B + I_C$$

$$I_E = I_B + \alpha I_E + I_{CBO}$$

$$I_E - \alpha I_E = I_B + I_{CBO}$$

$$I_E(1-\alpha) = I_B + I_{CBO}$$

$$I_E = \frac{1}{1-\alpha} I_B + \frac{1}{1-\alpha} I_{CBO}$$

$$= \beta I_B + \beta I_{CBO}$$

$$\beta = \frac{\alpha}{1-\alpha}$$

$$I_E = (\beta+1) I_B + (\beta+1) I_{CBO}$$

Q) find the value of β if $\alpha = 0.9$

$$\beta = \frac{\alpha}{1-\alpha} = \frac{0.9}{1-0.9} = \frac{0.9}{0.1} = 9.$$

Q) find the value of α if $\beta = 49$.

$$49 = \frac{\alpha}{1-\alpha}.$$

$$49 - 49\alpha = \alpha.$$

$$49 = 50\alpha.$$

$$\alpha = \frac{49}{50}.$$

$$\alpha = 0.98.$$

Q) find the value of I_C where $\beta = 50$ &
 $I_B = 20\text{mA}$ & take I_{CBO} is 10mA

$$= 50 \times 20 +$$

$$\gamma = 1 + \beta$$

$$I_C = \beta I_B + \gamma I_{CBO}$$

$$= 51$$

$$= (50)(20) + (51)(10)$$

$$= 1000 + 510$$

$$I_C = 1510\text{mA}$$

8) find the value of β of a transistor when α is 0.98 calculate the values of β & γ .

$$\beta = \frac{\alpha}{1 - \alpha}$$

$$= \frac{0.98}{1 - 0.98} = \frac{0.98}{0.02} = 49$$

$$\gamma = 1 + \beta = 50$$

$$= 49$$

9) collector current of transistor is 9.945mA emitter current is 10mA & leakage current is 5 μ A. when it is connected in CB configuration α, β, γ .

$$I_C = 9.945 \text{ mA}, I_E = 10 \text{ mA}$$

$$I_{CBO} = 5 \mu \text{ A}$$

$$I_C = \left(\frac{\beta}{1 + \beta} \right) I_E + I_{CBO}$$

$$9.945 = \left(\frac{\beta}{1 + \beta} \right) 10 + 5 \times 10^{-3}$$

$$9.945 = \frac{10\beta}{1 + \beta} + 0.005$$

$$9.940 = \frac{10\beta}{1 + \beta}$$

Q) find the value of β of a transistor when α is 0.98 calculate the values of β & γ .

$$\beta = \frac{\alpha}{1 - \alpha}$$

$$= \frac{0.98}{1 - 0.98} = \frac{0.98}{0.02} = 49$$

$$\gamma = 1 + \beta = 50$$

$$= 49$$

Q) collector current of transistor is 9.945mA emitter current is 10mA & leakage current is 5 μ A. When it is connected in CB configuration α , β , γ .

$$I_C = 9.945$$

$$I_C = 9.945 \text{ mA}, I_E = 10 \text{ mA}$$

$$I_{CBO} = 5 \mu\text{A}$$

$$I_C = \left(\frac{\beta}{1 + \beta} \right) I_E + I_{CBO}$$

$$9.945 = \left(\frac{\beta}{1 + \beta} \right) 10 + 5 \times 10^{-3}$$

$$9.945 = \frac{10\beta}{1 + \beta} + 0.005$$

$$9.940 = \frac{10\beta}{1 + \beta}$$

$$10\beta = 9.940 + 9.940\beta$$

$$0.06\beta = 9.940$$

$$\beta = 165.6$$

$$\beta = \frac{\alpha}{1-\alpha}$$

$$165.6 = \frac{\alpha}{1-\alpha}$$

$$165.6 - 165.6\alpha = \alpha$$

$$166.6\alpha = 165.6$$

$$\alpha = 0.994$$

$$V = 1 + \beta = 165.6 + 1$$

$$= 166.$$

Comparison of Transistor:

Configuration	CB	CE	CC
S/p R	less 100Ω	less 750Ω	very high $750 k\Omega$
O/p R	very high $450 k\Omega$	high $45 k\Omega$	low 50Ω
volt gain	100	500	< 1
Applications	radio frequency	Audio frequency	Impedance matching

V_{CE0} : This is the maximum voltage which may be applied across the collector emitter terminal with base open

V_{CB0} (collector to base voltage): The maximum voltage which may be applied to the collector base terminal with emitter open